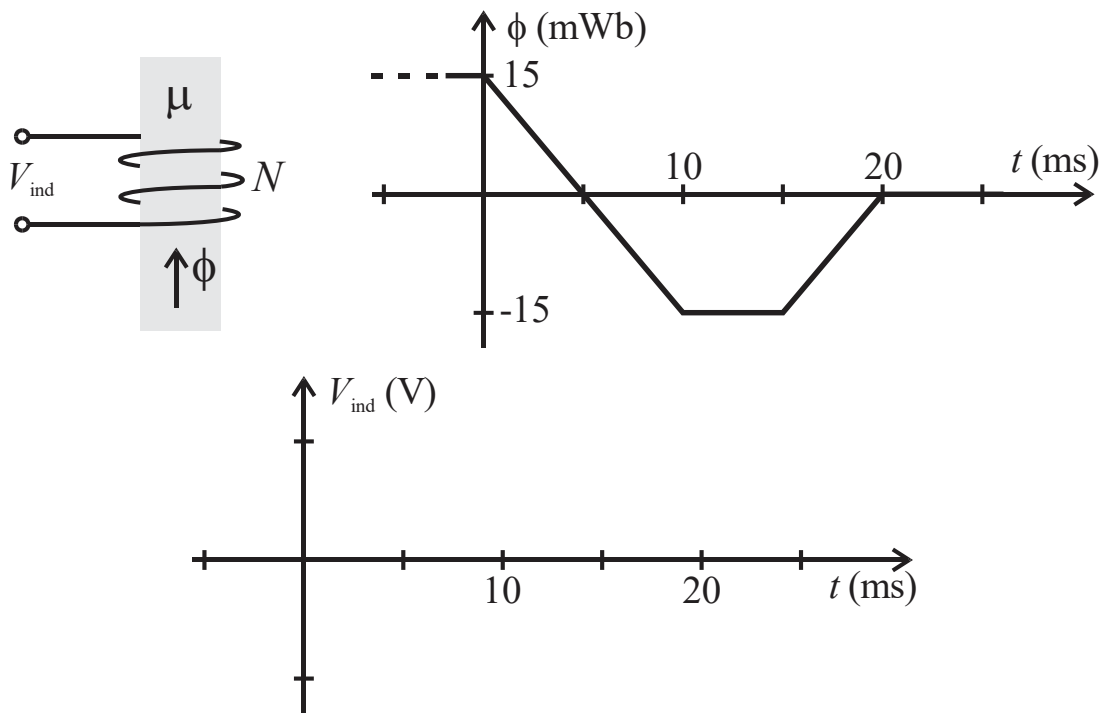


EE 330 Energy Systems (Fall 2026)


Homework 2

Wednesday, September 9, 2026

- 1) 1-10 Show voltage polarity on the figure.
- 2) A 40-turn coil of copper magnetic wire is tightly-wound about a magnetic core as shown. If the core carries the magnetic flux ϕ shown, determine the polarity of the voltage induced V_{ind} at the wire terminals (show polarity on figure) and sketch on the provided axes.



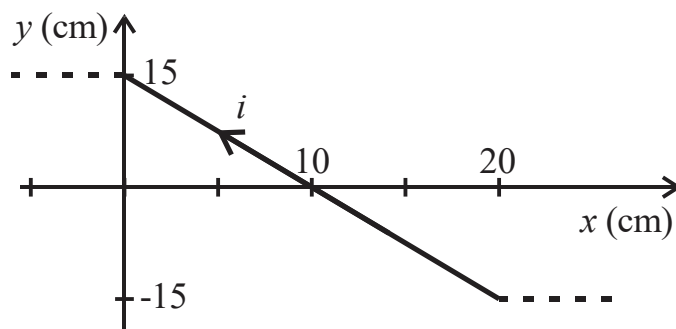- 3) The wire section shown (solid line) is exposed to a magnetic field of $19.1 \hat{a}_x$ (kA/m) in air. If the wire carries a current of 12 A, find: a) the magnetic flux density vector, b) length vector of the wire section, and c) the vector magnetic force on the wire.



- 4) A 60 Hz, 208 V_{rms} single-phase source (assume 0 degree phase angle) initially supplies two loads ($\bar{Z}_1 = 16\angle 60^\circ \Omega$ & $\bar{Z}_2 = 16 + j8 \Omega$) connected in parallel.
 - a) Find the phasor current (rms) and real, reactive, & apparent powers as well as the power factor for load 1.
 - b) Repeat for load 2.
 - c) Find the phasor line current (rms) as well as the real, reactive, & apparent powers supplied by the source. Also, find the power factor 'seen' by the source.
 - d) We desire to achieve a $PF \geq 0.9$ by connecting a capacitive load in parallel. What range of capacitance values will work?
- 5) A 60 Hz, 120 V_{rms} single-phase source (assume 0° phase angle) is connected to three loads connected in parallel. Load 1 consumes 12 kW of power and has a power factor $pf_1 = 0.866$ leading. Load 2 draws 156 A_{rms} of current and has $pf_2 = 0.85$ lagging. Load 3 uses 20 kvar of reactive power and has a power factor $pf_3 = 0.6$ lagging. Determine:
 - a) the complex power consumed, phasor current (rms) drawn by, and impedance of load 1,
 - b) repeat for load 2,
 - c) repeat for load 3,
 - d) the total complex power and phasor current (rms) supplied by the source, and
 - e) the overall power factor 'seen' by the source.
- 6) It is desired to correct the overall power factor of the prior problem to unity by connecting a reactive load in parallel with loads 1 – 3.
 - a) Will the reactive load need to be an inductor or capacitor? Explain.
 - b) Determine the value of the reactive load (i.e., L or C) required, reactive power used, and phasor current (rms) supplied to the reactive load.
 - c) Determine the new complex power and phasor current (rms) supplied by the source. By what percent was the source current magnitude reduced (e.g., $|I_{old} - I_{new}| / I_{old} * 100\%$)?

Due Monday, September 14, 2026.