

## EE 330 (Spring 2012) Examination 2

Name Key

**Instructions:** Show all work for full credit. Write answers in indicated places. Attach equation sheet to exam.

- 1) A 3-phase, 6-pole, Y-connected AC generator outputs an open circuit terminal voltage of 500 V<sub>rms</sub> at 50 Hz. There are 66 turns per coil and the coils are installed in 18 slots around the stator. For each phase, the coils are connected in series. Determine the necessary shaft rotation speed  $\omega_m$  (rad/s) and  $n_m$  (RPM). Find the open circuit phase voltage  $V_\phi$  and required magnetic flux. For an electrical load of 25 kVA with a 0.8 lagging power factor at the rated voltage, the electrical losses are 800 W, mechanical losses are 1.4 kW, and stray/core losses are 600 W. Determine the input power  $P_{in}$ , applied torque  $\tau_{app}$ , and efficiency  $\eta$ . Use MKS units.

$$\text{Per (3-34)} \quad f_{se} = \frac{N_{sm} P}{120} \Rightarrow n_m = \frac{120(50)}{6} = \underline{1000 \text{ RPM}}$$

$$\omega_m = (1000 \frac{\text{rev}}{\text{min}}) \left( \frac{1 \text{ min}}{60 \text{ sec}} \right) \left( \frac{2\pi \text{ rad}}{1 \text{ rev}} \right) = 33.3\pi = \underline{104.72 \text{ rad/s}}$$

$$\text{Y-connected, per (A-11)} \quad V_{LL} = \sqrt{3} V_\phi \Rightarrow V_\phi = \frac{500}{\sqrt{3}} = \underline{288.675 \text{ V}_{rms}}$$

Per (3-50), the induced RMS voltage for a coil (2-slots per coil)

is  $E_A = \sqrt{2} \pi N_c \phi f$ . With 18 slots, we have

$\frac{18 \text{ slots}}{3 \text{ phases}} = 6 \frac{\text{slots}}{\text{phase}}$ . So, w/ open circuit conditions -

$$E_A = V_\phi = \frac{\sqrt{2} \pi N_c \phi f}{2 \text{ slots}} (6 \text{ slots}) = 3\sqrt{2} \pi N_c \phi f$$

$$\hookrightarrow \phi = \frac{288.675}{3\sqrt{2} \pi (66) 50} = \underline{0.0065631 \text{ Wb}}$$

$$P_{in} = P_{out} + \text{losses} = 25 \text{ kVA} (0.8) + 0.8 \text{ kW} + 1.4 \text{ kW} + 0.6 \text{ kW} = \underline{22.8 \text{ kW}}$$

$$P_{in} = P_{mech} = \tau_{app} \omega_m \Rightarrow \tau_{app} = \frac{22,800}{104.72} = \underline{217.72 \text{ N}\cdot\text{m}}$$


$$\eta = \frac{P_{out}}{P_{in}} \times 100\% = \frac{25(0.8)}{22.8} \times 100\% = \underline{87.72\%}$$

$$\omega_m = \underline{104.72 \frac{\text{rad}}{\text{s}}} \quad n_m = \underline{1000 \text{ RPM}} \quad V_\phi = \underline{288.675 \text{ V}_{rms}} \quad \phi = \underline{6.563 \text{ mWb}}$$

$$P_{in} = \underline{22.8 \text{ kW}} \quad \tau_{app} = \underline{217.72 \text{ N}\cdot\text{m}} \quad \eta = \underline{87.72\%}$$

2) A Y-connected 3-phase, synchronous generator has the OCC and SCC shown. The rated field current is 6 A. A 6 V<sub>dc</sub> voltage applied across two terminals results in a current of 4 A<sub>dc</sub>. Find the per-phase armature resistance R<sub>A</sub> and rated synchronous reactance X<sub>S</sub>. Sketch, with labels, the per-phase equivalent armature circuit. At the rated field current, a load draws a line current of 12 A<sub>rms</sub> with a lagging power factor of 0.82. Find the phasor armature voltage  $\bar{E}_A$ , armature current  $\bar{I}_A$ , and phase voltage  $\bar{V}_\phi$  (assume at angle 0°).

Y-connection

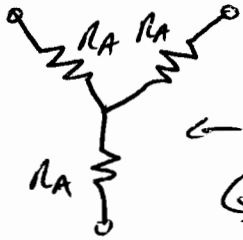

$$R_T = 2R_A = \frac{V_{dc}}{I_{dc}}$$

$$R_A = \frac{6}{2(4)} = 0.75 \Omega$$

From OCC,  $V_{T,oc} = 600 V_{rms}$

Per (A-11)  $V_{LL} = \sqrt{3} V_\phi$

$$V_{\phi,oc} = E_{A,oc} = \frac{600}{\sqrt{3}} = 346.41 V_{rms}$$

From SCC,  $I_{L,sc} = I_{A,sc} = 30 A_{rms}$

Per (4-25),  $\sqrt{R_A^2 + X_S^2} = \frac{E_{A,oc}}{I_{A,sc}}$



$$X_S = \sqrt{\left(\frac{346.41}{30}\right)^2 - 0.75^2}$$

$$= \sqrt{11.547^2 - 0.75^2}$$

$$= 11.5226227 \Omega$$

$R_A = 0.75 \Omega$


$X_S = 11.523 \Omega$

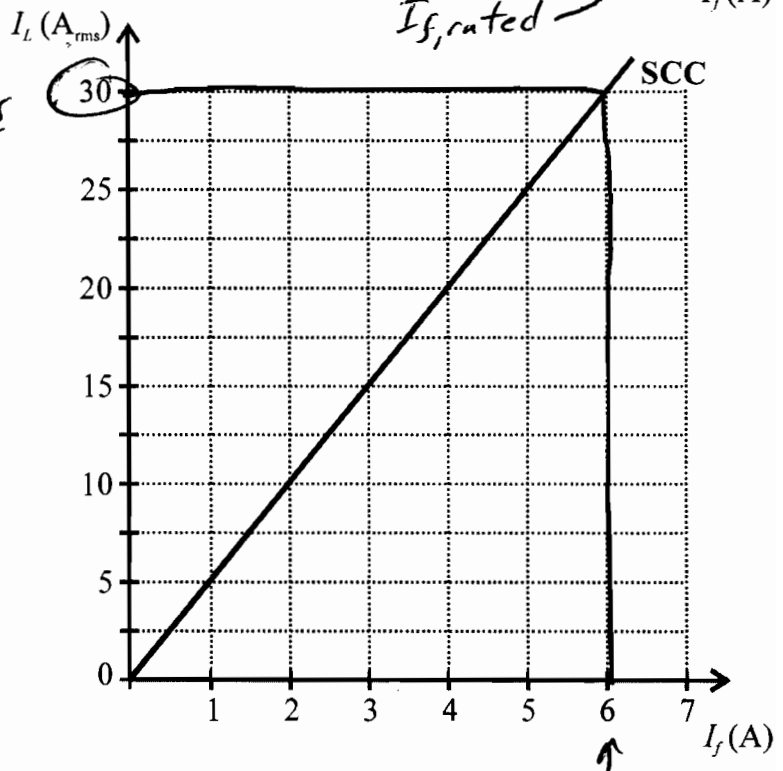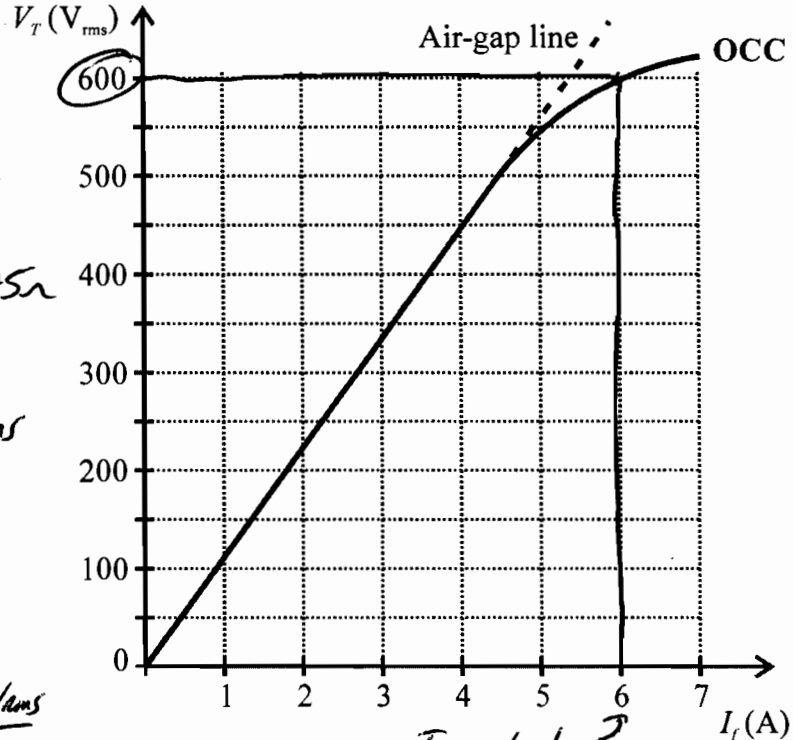

$I_{f,rated}$

2) cont.

Per-phase equivalent armature circuit

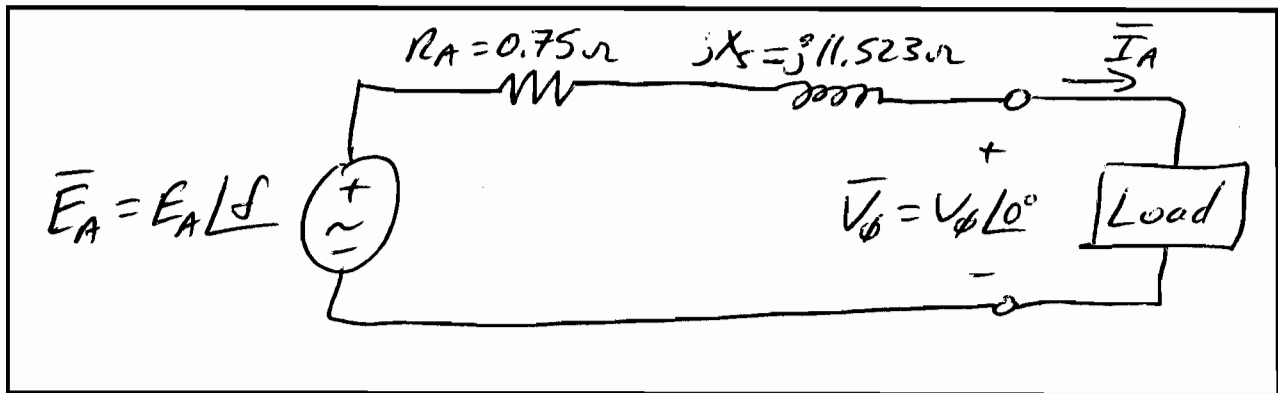

We are given  $\bar{I}_A = \bar{I}_L = 12 \text{ A rms}$ . For a  $\text{pf} = 0.82$  lagging,

$$\theta = \phi_{V_\phi} - \theta_{\bar{I}_A} = \cos^{-1}(0.82) = 34.9152^\circ \Rightarrow \theta_{\bar{I}_A} = -34.9152^\circ$$

$$\hookrightarrow \bar{I}_A = 12 \angle -34.915^\circ \text{ A rms}$$

By KVL,  $\bar{E}_A = \bar{I}_A (R_A + jX_S) + \bar{V}_\phi$  @ rated  $I_f$ ,  $E_A = \frac{600}{\sqrt{3}} \text{ V rms}$

$$\frac{600}{\sqrt{3}} \angle \delta = (12 \angle -34.915^\circ)(0.75 + j11.523) + V_\phi \angle 0^\circ$$

$$\frac{600}{\sqrt{3}} \cos \delta + j \frac{600}{\sqrt{3}} \sin \delta = 86.52154658 + j108.2313354 + V_\phi$$

$$\text{Equate imaginary parts} \rightarrow \frac{600}{\sqrt{3}} \sin \delta = 108.2313354$$


$$\hookrightarrow \delta = 18.206154^\circ$$

$$\text{Equate real parts} \rightarrow \frac{600}{\sqrt{3}} \cos(18.206154^\circ) = 86.52155 + V_\phi$$

$$\hookrightarrow V_\phi = 242.5468 \text{ V rms}$$

$$\bar{I}_A = 12 \angle -34.915^\circ \text{ A rms} \quad \bar{E}_A = 346.41 \angle 18.206^\circ \text{ V rms} \quad \bar{V}_\phi = 242.55 \angle 0^\circ \text{ V rms}$$

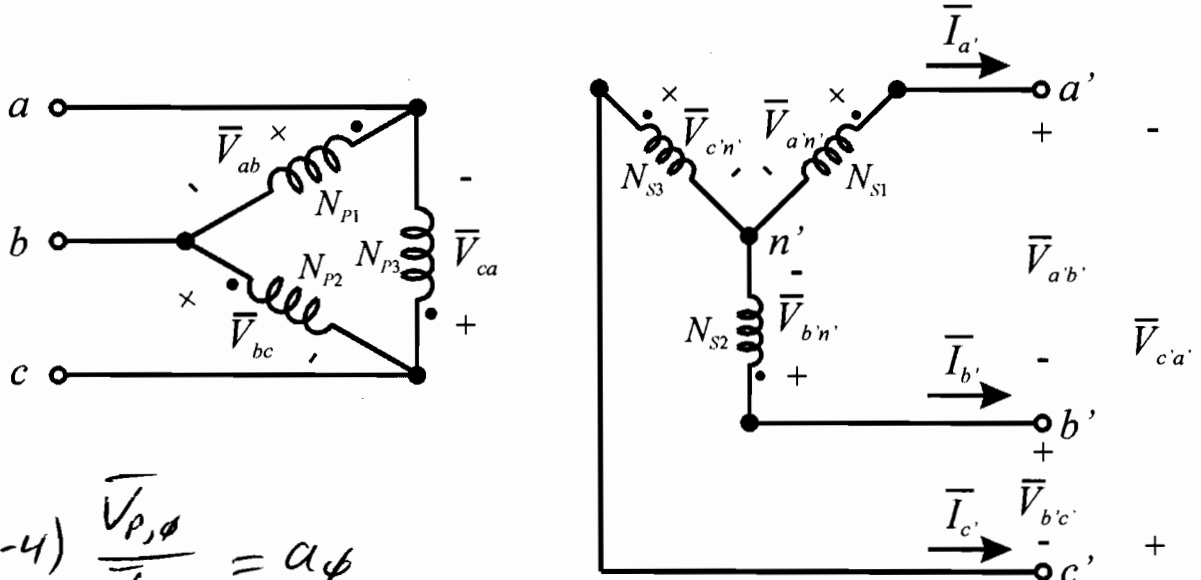3) A 200 kVA, 480/2,400 V<sub>rms</sub>, Δ-Y connected three-phase transformer is connected as shown. Given  $\vec{V}_{ab} = V_{LL,P} \angle 0^\circ$ ,  $\vec{V}_{bc} = V_{LL,P} \angle 120^\circ$ , and  $\vec{V}_{ca} = V_{LL,P} \angle 240^\circ$ , determine the secondary line voltages  $\vec{V}_{a'b'}$ ,  $\vec{V}_{b'c'}$ , &  $\vec{V}_{c'a'}$ , phase voltages  $\vec{V}_{a'n'}$ ,  $\vec{V}_{b'n'}$ , &  $\vec{V}_{c'n'}$ , and phase turns ratio  $a_\phi$ . **Bonus-** If the rated load with a power factor of 0.7 lagging is connected, find the line currents  $\vec{I}_{a'}$ ,  $\vec{I}_{b'}$ , &  $\vec{I}_{c'}$ .



Per (2-4)  $\frac{\vec{V}_{P,\phi}}{\vec{V}_{S,\phi}} = a_\phi$

So  $\frac{\vec{V}_{ab}}{\vec{V}_{a'n'}} = a_\phi \Rightarrow \vec{V}_{a'n'} = \frac{\vec{V}_{ab}}{a_\phi} = \frac{480}{a_\phi} \angle 0^\circ \text{ Vrms}$  ← given

Similarly  $\vec{V}_{b'n'} = \frac{\vec{V}_{bc}}{a_\phi} = \frac{480}{a_\phi} \angle 120^\circ \text{ Vrms}$

$\vec{V}_{c'n'} = \frac{\vec{V}_{ca}}{a_\phi} = \frac{480}{a_\phi} \angle 240^\circ \text{ Vrms}$

By KVL,  $\vec{V}_{a'b'} = \vec{V}_{a'n'} - \vec{V}_{b'n'} = \frac{480}{a_\phi} [1 \angle 0^\circ - 1 \angle 120^\circ]$

given  $\Rightarrow 2400 \angle \theta_{a'b'} = \frac{480\sqrt{3}}{a_\phi} \angle -30^\circ$

$\Rightarrow \theta_{a'b'} = -30^\circ$   $\Rightarrow \vec{V}_{a'b'} = 2400 \angle -30^\circ \text{ Vrms}$

and

$a_\phi = \frac{480\sqrt{3}}{2400} = 0.34641$

Note:  $a_{\Delta-Y} = \frac{480}{2400} = 0.2 = \sqrt{3} a_\phi$

3) cont.

$$\text{Then } \bar{V}_{a'n'} = \frac{480}{a_\phi} \angle 0^\circ = \frac{480}{0.3464} \angle 0^\circ = \underline{1385.64 \angle 0^\circ \text{ V}_{rms}}$$

$$\underline{\bar{V}_{b'n'} = 1385.64 \angle 120^\circ \text{ V}_{rms}} \quad \& \quad \underline{\bar{V}_{c'n'} = 1385.64 \angle 240^\circ \text{ V}_{rms}}$$

$$\bar{V}_{b'c'} = \bar{V}_{b'n'} - \bar{V}_{c'n'} = 1385.64 \angle 120^\circ - 1385.64 \angle 240^\circ = \underline{2400 \angle 90^\circ \text{ V}_{rms}}$$

$$\bar{V}_{c'a'} = \bar{V}_{c'n'} - \bar{V}_{a'n'} = 1385.64 \angle 240^\circ - 1385.64 \angle 0^\circ = 2400 \angle -150^\circ \text{ V}_{rms}$$

OR  
2400 \angle 210^\circ \text{ V}\_{rms}

$$\text{Bonus: Per (A-31)} \quad \bar{I}_L = \bar{I}_{rated} = \frac{S_{rated}}{\sqrt{3} V_{L,rated}} = \frac{200 \times 10^3}{\sqrt{3} \cdot 2400} = \underline{48.1125 \text{ A}_{rms}}$$

$$\theta = \theta_V - \theta_I = \cos^{-1} 0.7 = 45.573^\circ \Rightarrow \theta_I = \theta_V - 45.573^\circ$$

$$\text{So } \theta_{I_{a'}} = \theta_{V_{a'n'}} - 45.573^\circ = 0 - 45.573^\circ = -45.573^\circ$$

$$\theta_{I_{b'}} = \theta_{V_{b'n'}} - 45.573^\circ = 120^\circ - 45.573^\circ = 74.427^\circ$$

$$\theta_{I_{c'}} = \theta_{V_{c'n'}} - 45.573^\circ = 240^\circ - 45.573^\circ = 194.427^\circ$$

= +165.573^\circ

where

$$\bar{I}_{a'} = \bar{I}_{b'} = \bar{I}_{c'} = 48.1125 \text{ A}_{rms}$$

$$\bar{V}_{a'b'} = \underline{2400 \angle -30^\circ \text{ V}_{rms}} \quad \bar{V}_{b'c'} = \underline{2400 \angle 90^\circ \text{ V}_{rms}} \quad \bar{V}_{c'a'} = \underline{2400 \angle 210^\circ \text{ V}_{rms}} \quad a_\phi = \underline{0.34641}$$

$\sim \text{OR } -150^\circ$

$$\bar{V}_{a'n'} = \underline{1385.64 \angle 0^\circ \text{ V}_{rms}} \quad \bar{V}_{b'n'} = \underline{1385.64 \angle 120^\circ \text{ V}_{rms}} \quad \bar{V}_{c'n'} = \underline{1385.64 \angle 240^\circ \text{ V}_{rms}}$$

$$\text{Bonus: } \bar{I}_{a'} = \underline{48.11 \angle -45.57^\circ \text{ A}_{rms}} \quad \bar{I}_{b'} = \underline{48.11 \angle 74.43^\circ \text{ A}_{rms}} \quad \bar{I}_{c'} = \underline{48.11 \angle 194.43^\circ \text{ A}_{rms}}$$