

## EE 330 (Spring 2012) Examination 3

Name Key

**Instructions:** Show all work for full credit. Write answers in indicated places. Attach equation sheet to exam.

- 1) A 120 V<sub>rms</sub>, 1.5 hp, 60 Hz, Y-connected, 4-pole, three-phase induction motor has a rated slip of 4%, 56 W of mechanical losses, 32 W of copper losses, 20 W of stray losses, and 44 W of core losses. Determine the synchronous, slip, and rated speeds (in RPM) as well as the frequency of the current on the rotor for this motor under rated conditions. Also, find the input power (W), output torque, induced torque, and efficiency (%) under rated conditions.

$$(6-1) \quad n_{sync} = \frac{120 f_{sc}}{p} = \frac{120(60)}{4} = 1800 \text{ RPM}$$

$$(6-3) \quad n_{slip} = s n_{sync} = 0.04(1800) = 72 \text{ RPM}$$

$$(6-6) \quad n_{rated} = (1-s) n_{sync} = (1-0.04)1800 = 1728 \text{ RPM}$$

$$(6-8) \quad f_{re} = s f_{se} = 0.04(60) = 2.4 \text{ Hz}$$

$$P_{in} = P_{out} + \text{losses} = (1.5 \text{ hp}) \left( \frac{746 \text{ W}}{1 \text{ hp}} \right) + 56 + 32 + 20 + 44 \\ = 1119 + 152 = 1271 \text{ W}$$

$$P_{out} = \tau_{out} \omega_m \Rightarrow \tau_{out} = \frac{(1.5)(746)}{1728 \left( \frac{\pi}{30} \right)} = 6.18383 \text{ N}\cdot\text{m}$$

$$P_{conv} = \tau_{ind} \omega_m = P_{out} + P_{stray} + P_{Fhw} = 1.5(746) + 20 + 56$$

$$\tau_{ind} = \frac{1119 + 20 + 56}{1728 \left( \frac{\pi}{30} \right)} = 6.6038 \text{ N}\cdot\text{m}$$

$$\eta = \frac{P_{out}}{P_{in}} \times 100 \% = \frac{1.5(746)}{1271} \times 100 \% = 88.0409 \%$$

$$n_{sync} = \underline{1800 \text{ RPM}}$$

$$n_{slip} = \underline{72 \text{ RPM}}$$

$$n_{rated} = \underline{1728 \text{ RPM}}$$

$$f_{rotor} = \underline{2.4 \text{ Hz}}$$

$$P_{in} = \underline{1271 \text{ W}}$$

$$\tau_{out} = \underline{6.1838 \text{ N}\cdot\text{m}}$$

$$\tau_{ind} = \underline{6.6038 \text{ N}\cdot\text{m}}$$



$$\eta = \underline{88.04 \%}$$

2) A simple rotating loop (see below) has:  $B = 0.15 \text{ T}$ ,  $l = 100 \text{ cm}$ ,  $r = 35 \text{ cm}$ ,  $R = 1.5 \Omega$ ,  $V_B = 25 \text{ V}$ , and brush voltage drops of  $0.8 \text{ V/ea}$ . Sketch a labeled equivalent electrical circuit in the box provided. Given that the loop is initially at rest, determine the no-load starting induced emf, induced torque, and current. Show the initial direction of loop rotation with a curved arrow on the drawing by  $o'$ .

*in direction of  $i$*

$$\vec{F} = i(\vec{l} \times \vec{B})$$

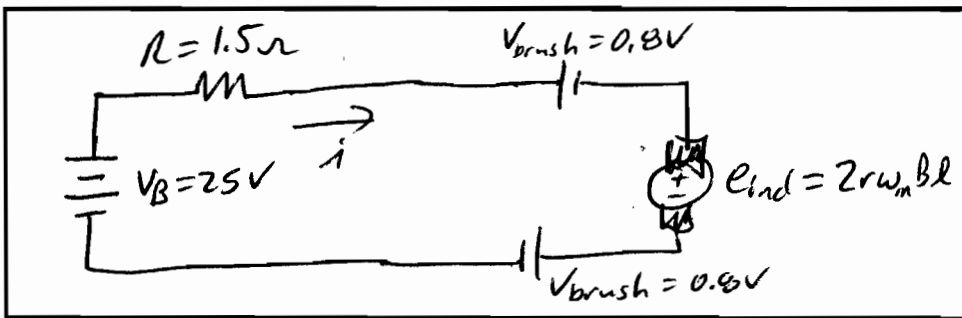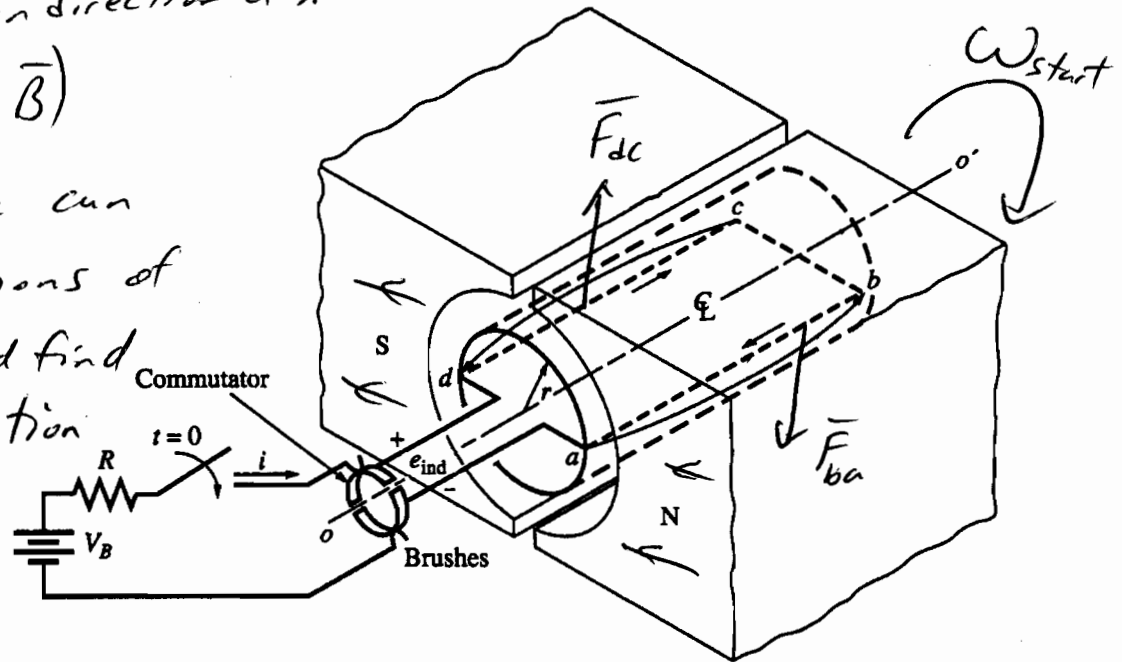wt this, we can find directions of  $\vec{F}_{dc}$  &  $\vec{F}_{ba}$  and find  $\omega_{start}$  direction



← (7-5) to (7-6)

@  $t = 0^+$ ,  $\omega_m = 0 \Rightarrow e_{ind} = 0$   
(@ rest)

By KVL,  $V_B = i_{start}(1.5) + 0.8 + e_{ind,start} + 0.8$

$$i_{start} = \frac{25 - 0.8 - 0.8}{1.5} = 15.6 \text{ A}$$

Per (8-15)  $\tau_{ind,start} = 2 r i_{start} l B = 2(0.35)(15.6)(1)(0.15)$   
 $= 1.638 \text{ N}\cdot\text{m}$

$\tau_{ind,start} = \underline{1.638 \text{ N}\cdot\text{m}}$

$i_{start} = \underline{15.6 \text{ A}}$

$e_{ind,start} = \underline{0}$

2) cont. Later, this loop is rotating clockwise (defined with right thumb pointing toward  $o'$ ) at a steady 1600 RPM. Is the loop acting as a generator or motor? Why? Find the steady-state induced emf, torque, current (base sign on arrow drawn on figure), electrical power into/out of battery, mechanical power into/out of the loop, and efficiency (%). Neglect mechanical losses.

$$e_{ind,ss} = 2r\omega Bl = 2(0.35)\left[1600\left(\frac{\pi}{30}\right)\right]0.15(1)$$

$$= 17.59292V < V_B \Rightarrow \underline{\text{Motor!}}$$

By KVL,  $25 = i_{ss}(1.5) + 0.8 + 17.5929 + 0.8$

$$\hookrightarrow i_{ss} = \frac{25 - 0.8 - 17.5929 - 0.8}{1.5} = 3.87138743A$$

Per (8-15)  $\tau_{ind,ss} = 2r i_{ss} l B = 2(0.35)(3.8714)(1)(0.15)$

$$= 0.4064956 \text{ N}\cdot\text{m}$$

$$P_B = -25(3.87) = -96.784686 \text{ W}$$

$$P_{mech} = \tau_{ind,ss} \omega_{ss} = (0.4065)1600\left(\frac{\pi}{30}\right) = 68.109 \text{ W}$$

$$\eta = \frac{P_{out}}{P_{in}} \times 100\% = \frac{P_{mech}}{P_B} \times 100\% = \frac{68.109}{96.785} \times 100\%$$

$$= 70.4\%$$

generator / motor? Why?  $e_{ind,ss} < V_B$

$$e_{ind,ss} = \underline{17.5929V} \quad \tau_{ind,ss} = \underline{0.4065 \text{ N}\cdot\text{m}} \quad i_{ss} = \underline{3.8714A}$$

$$|P_B| = \underline{96.785W} \text{ (into / out of battery?)} \quad P_{mech} = \underline{68.109W} \text{ (into / out of loop?)}$$

(For questions, **circle** correct answers)

+2 Extra credit  $\rightarrow$   $\eta = 70.4\%$  motor delivers power

- 3) A 480 V<sub>rms</sub>, 110 hp, 50 Hz, six-pole, Y-connected, three-phase induction motor has per-phase equivalent circuit parameters:  $R_1 = R_2 = 0.09 \Omega$ ,  $X_1 = X_2 = 0.3 \Omega$ ,  $X_M = 9 \Omega$ , and  $R_C = 75 \Omega$ . With a slip of 4.5%, sketch a fully-labeled per-phase equivalent circuit (assume line voltage at  $0^\circ$ ). Then, find the magnitude of the line current, input power, and input power factor.


$$\bar{V}_\phi = \frac{480}{\sqrt{3}} \angle 0^\circ \text{ V}_{rms} = 277.13 \angle 0^\circ \text{ V}_{rms}$$

$$n_{sync} = \frac{120 f_{sc}}{p} = \frac{120(50)}{6} = 1000 \text{ RPM} \quad \omega_{sync} = n_{sync} \left( \frac{\pi}{30} \right) = 104.719755 \frac{\text{rad}}{\text{s}}$$

$$R_{z/s} = \frac{0.09}{0.045} = 2 \Omega, \quad R_2 = 0.09 \Omega, \quad R_{conv} = R_2 \left( \frac{1-s}{s} \right) = 0.09 \left( \frac{1-0.045}{0.045} \right) = 1.91 \Omega$$

$$\omega_m = (1-s)\omega_{sync} = (1-0.045)104.72 = 100.007 \frac{\text{rad}}{\text{s}}$$

Per-phase equivalent circuit

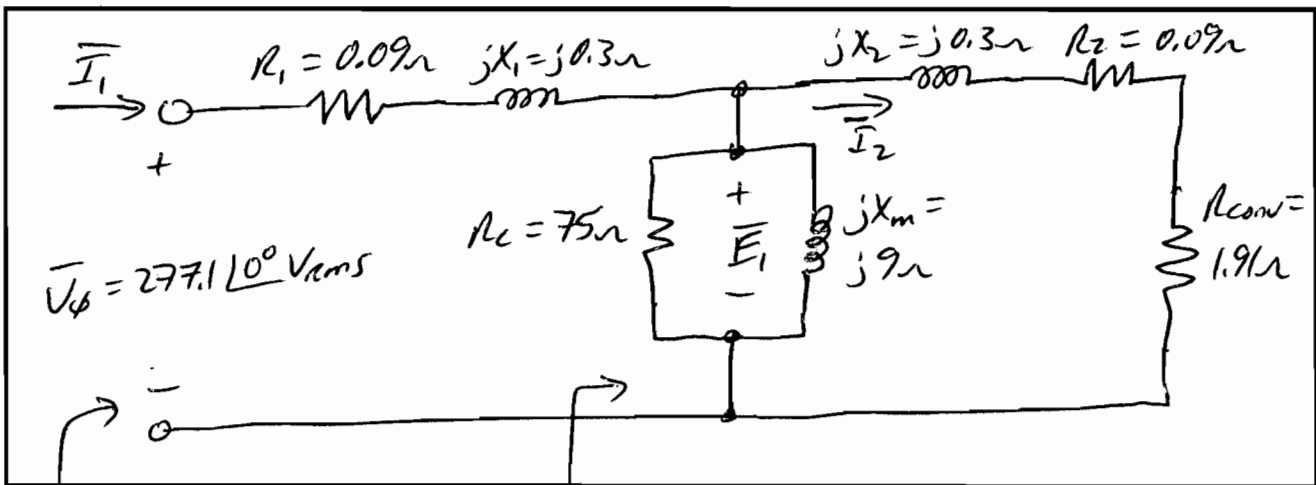

$$\bar{Z}_{eq,p} = 75 \parallel j9 \parallel (2 + j0.3) = 1.75418 + j0.64415 \Omega$$

$$\bar{Z}_{in} = (R_1 + jX_1) + \bar{Z}_{eq,p} = (0.09 + j0.3) + (1.75418 + j0.64415) = 1.84418 + j0.94415 \Omega$$

$$\bar{I}_1 = \frac{480}{\sqrt{3}} \angle 0^\circ}{1.844 + j0.944} = 133.7609029 \angle -27.1107608^\circ \text{ A}$$

$$I_L = |\bar{I}_1| = 133.761 \text{ A}_{rms} \quad (\text{R-L impedance})$$

$$pf_{in} = \cos \theta_{Z_{in}} = \cos(0 + 27.11076^\circ) = 0.890127 \text{ lagging}$$

$$P_{in} = \sqrt{3} V_{LL} I_L \cos \theta = \sqrt{3} (480) 133.761 \cos(27.11076^\circ) = 98,988.13555 \text{ W}$$

$$I_L = 133.761 \text{ A}_{rms} \quad P_{in} = 98.988 \text{ kW} \quad pf_{in} = 0.8901 \text{ lagging}$$

- 3) cont. Next, determine the stator copper losses, core losses, air gap power, & rotor copper losses, **Extra credit:** Find the converted power (from electrical to mechanical), and induced torque. If the friction & windage losses are 3.3 kW, determine the stray losses and efficiency (%) of the motor.

$$(6-25) P_{SCL} = 3|\bar{I}_1|^2 R_1 = 3(133.761)^2 0.09 = \underline{4830.834 \text{ W}}$$

$$\text{By voltage division, } \bar{E}_1 = \bar{V}_\phi \frac{\bar{Z}_{2,P}}{\bar{Z}_{in}} = \left(\frac{480}{\sqrt{3}} \angle 0^\circ\right) \frac{1.754 + j0.644}{1.844 + j0.944}$$

$$= 249.960527 \angle -6.947039^\circ \text{ V}_{rms}$$

$$(6-26) P_{core} = \frac{3|\bar{E}_1|^2}{R_c} = \frac{3(249.96)^2}{75} = \underline{2499.211 \text{ W}}$$

$$\text{By Ohm's Law, } \bar{I}_2 = \frac{\bar{E}_1}{2 + j0.3} = \frac{249.96 \angle -6.95^\circ}{2 + j0.3} = 123.59753 \angle -15.4778^\circ \text{ A}_{rms}$$

$$(6-27) \& (6-28) P_{AG} = P_{in} - P_{SCL} - P_{core} = 91,658.09 \text{ W} \quad \swarrow \text{ same!}$$

$$= 3|\bar{I}_2|^2 \frac{R_2}{s} = 3(123.6)^2 \frac{0.09}{0.045} = \underline{91,658.1 \text{ W}}$$

$$(6-30) P_{RCL} = 3|\bar{I}_2|^2 R_2 = 3(123.6)^2 0.09 = \underline{4124.61 \text{ W}}$$

$$\text{Extra Credit: } (6-33) P_{conv} = (1-s)P_{AG} = (1-0.045)91,658.09 = \underline{87,533.5 \text{ W}}$$

$$(6-35) P_{conv} = \tau_{ind} \omega_m \Rightarrow \tau_{ind} = \frac{87533.5}{100.0074} = \underline{875.27 \text{ Nm}}$$

$$P_{stray} = P_{in} - P_{SCL} - P_{core} - P_{RCL} - P_{mech} - P_{out}$$

$$= 98,988.136 - 4830.834 - 2499.211 - 4124.61 - 110 \text{ hp} \left(\frac{746 \text{ W}}{\text{hp}}\right) = \underline{5473.48 \text{ W}}$$

$$\eta = \frac{P_{out}}{P_{in}} \times 100\% = \frac{110(746)}{98988} \times 100\% = \frac{82060}{98988} \times 100\% = \underline{82.9\%}$$

$$P_{SCL} = \underline{4.831 \text{ kW}} \quad P_{core} = \underline{2.499 \text{ kW}} \quad P_{AG} = \underline{91.658 \text{ kW}} \quad P_{RCL} = \underline{4.125 \text{ kW}}$$

$$\text{Extra credit: } P_{conv} = \underline{87.533 \text{ kW}}$$

$$\tau_{ind} = \underline{875.27 \text{ N}\cdot\text{m}}$$

+2/ea

$$P_{stray} = \underline{5473.5 \text{ W}}$$

$$\eta = \underline{82.9\%}$$

+ P<sub>mech</sub> (actually)