

EE 330/330L Energy Systems (Spring 2012) Laboratory 1 Three-Phase Loads

Introduction/Background

In this laboratory, you will measure and study the voltages, currents, impedances, phase angles, power factors, and real & reactive power in balanced three-phase systems. In particular, balanced Y-Y (Fig. 1a) and Δ - Δ (Fig. 1b) three-phase systems will be studied. Also, an unbalanced Y-Y system is examined.

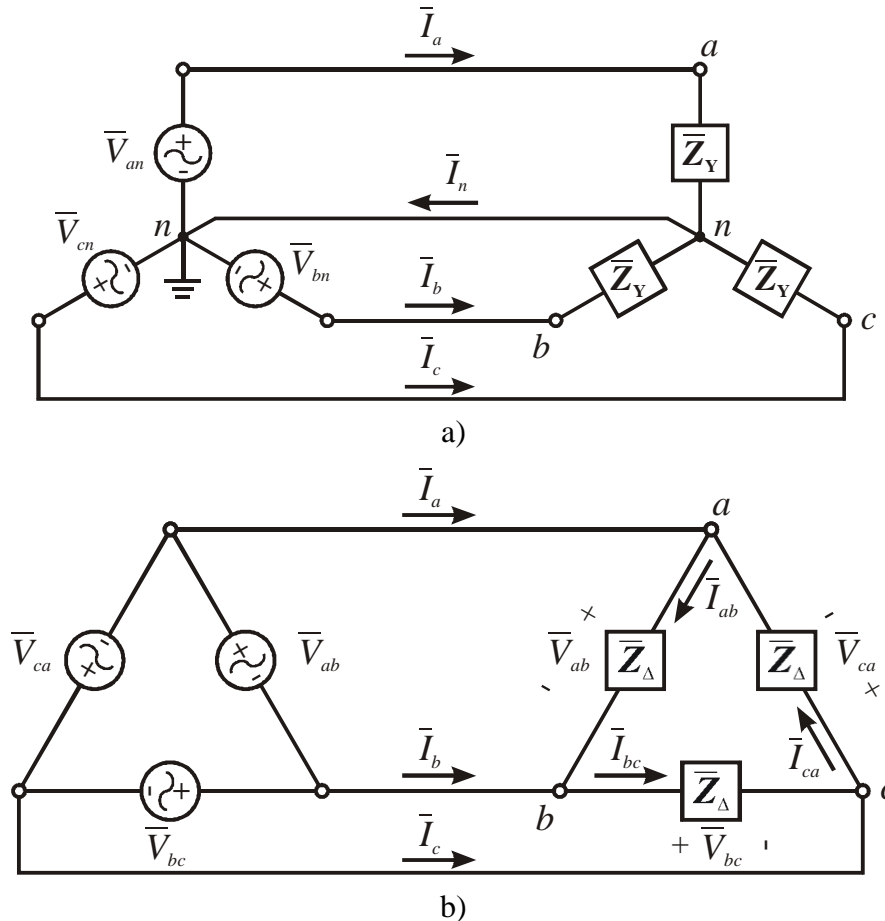


Figure 1 Balanced a) Y-Y (4-wire) and b) Δ - Δ three-phase systems.

Preliminary

- 1) For the balanced Y-Y three-phase circuit shown in Fig. 1a, the phase voltages V_{an} , V_{bn} , & V_{cn} are $63.5 \text{ V}_{\text{rms}}$. For a load impedance $\bar{Z}_Y = 100 \Omega$, determine the line/phase currents $I_L = I_a = I_b = I_c$, neutral current I_n , line-to-line voltages $V_{LL} = V_{ab} = V_{bc} = V_{ca}$, phase apparent powers $S_a = S_b = S_c$, total apparent power S , phase powers $P_a = P_b = P_c$, total power P , phase reactive powers $Q_a = Q_b = Q_c$, total reactive power Q , phase power factors $pf_a = pf_b = pf_c$, and overall power factor pf .
- 2) Assuming a frequency of 60 Hz, repeat part 1 when inductors with a wire resistance of 15Ω and inductance of 0.175 H are placed in series with the loads of part 1. What is the new load impedance \bar{Z}_Y ? Tabulate answers from parts 1 & 2 (e.g., column 1 quantity name, column 2 part 1 answer, and column 3 part 2 answer).
- 3) For the balanced Δ - Δ three-phase circuit shown in Fig. 1b, the line-to-line/phase voltages V_{ab} , V_{bc} , & V_{ca} are $90 \text{ V}_{\text{rms}}$. The load impedance \bar{Z}_Δ is 100Ω in series with inductors with a wire resistance of 15Ω and inductance of 0.175 H . Assuming a frequency of 60 Hz, determine the phase currents $I_\phi =$

$I_{ab} = I_{bc} = I_{ca}$, line currents $I_L = I_a = I_b = I_c$, phase apparent powers $S_{ab} = S_{bc} = S_{ca}$, total apparent power S , phase powers $P_{ab} = P_{bc} = P_{ca}$, total power P , phase reactive powers $Q_{ab} = Q_{bc} = Q_{ca}$, total reactive power Q , phase power factors $pf_{ab} = pf_{bc} = pf_{ca}$, and overall power factor pf . Tabulate answers.

- Read through the following experiments and determine which equations will be needed for the calculations.

Experiment 1

- Connect a balanced Y-Y three-phase circuit with load impedances of $\bar{Z}_Y \approx 100\Omega$ (use rheostats). A block diagram of the necessary connections, including wattmeters and ammeter, is shown in Fig. 2. Do **NOT** plug in the power cord at this point. Using an ohmmeter (multimeter), measure and record the dc resistances $R_a, R_b,$ and R_c of the loads.

Three-phase Wall Outlet

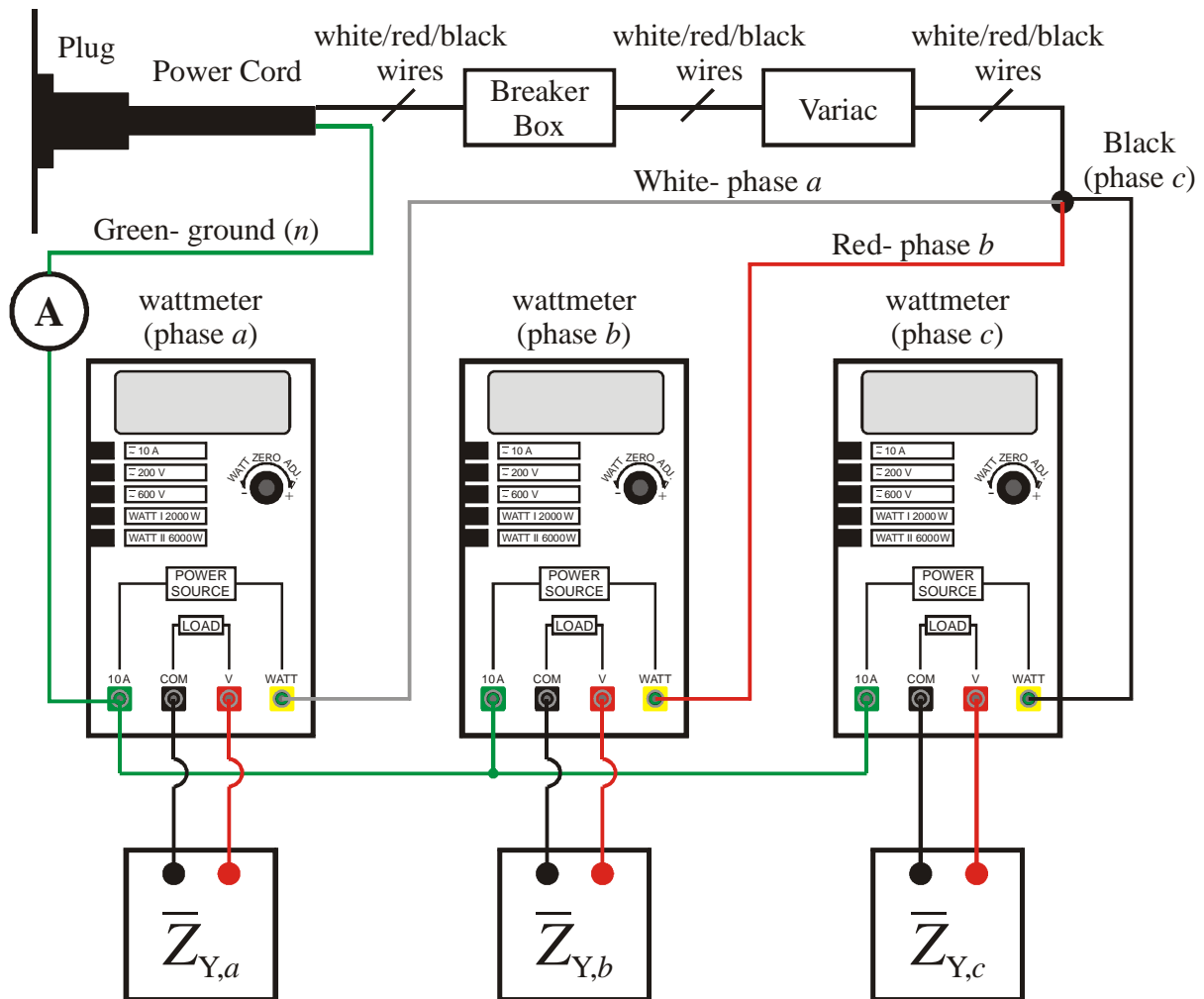


Figure 2 Balanced Y-Y three-phase circuit for Experiment 1.

- After ensuring the breaker box is 'off' and that the variac is set to 0 (all the way CCW), plug in the power cord. Designate the white wire as phase a , red wire as phase b , and black wire as phase c (totally arbitrary). Use a voltmeter (multimeter) to measure the wall outlet line-to-line voltages $V_{ab}, V_{bc},$ & V_{ca} and phase voltages $V_{an}, V_{bn},$ & V_{cn} at the breaker box input jacks. Use the frequency measurement capability of the multimeter to verify that the frequency is ~ 60 Hz.

- 3) Turn on and zero the wattmeters in **WATT I** mode. Then, put the wattmeters in **200 V** mode to measure the phase voltages. Turn on and ensure the ammeter (multimeter) is properly connected and set for ac current. Turn the breaker box 'on' and **slowly** increase the variac setting until phase voltages of $\sim 63.5 V_{\text{rms}}$ are achieved.
- 4) Measure and record the actual phase voltages V_{an} , V_{bn} , and V_{cn} . Put the wattmeters in **10 A** mode. Measure and record the phase currents I_a , I_b , and I_c . Put the wattmeters in **2000 W** mode. Measure and record the phase powers P_a , P_b , and P_c .
- 5) Using the ammeter, measure and record the neutral current I_n .
- 6) Using a voltmeter (multimeter), measure and record the line-to-line voltages V_{ab} , V_{bc} , and V_{ca} .
- 7) Set the variac to 0 (i.e., rotate dial/knob all the way CCW), turn breaker box off, and unplug the power cord. Do **NOT** disassemble circuit.
- 8) Using the preceding measurements, determine the total power P , apparent powers S_a , S_b , & S_c , total apparent power S , power factors pf_a , pf_b , & pf_c , overall power factor pf , impedance phase angles θ_a , θ_b , & θ_c , load impedance magnitudes Z_a , Z_b , & Z_c , complex impedances \bar{Z}_a , \bar{Z}_b , & \bar{Z}_c (put in rectangular form), reactive phase powers Q_a , Q_b , & Q_c , and total reactive power Q .
- 9) Tabulate nominal values and calculated answers from part 1 of the preliminary and experiment 1 (e.g., column 1- quantity name, column 2- part 1 answer, column 3- experiment 1 answer, & column 4- % difference, except for complex numbers). List in order measured/calculated in experiment 1. How do the calculated and measured quantities compare? Discuss discrepancies.

Experiment 2

- 1) Obtain three inductors from the instructor or teaching assistant (TA). Record the labeled inductance values of L_a , L_b , and L_c .
- 2) Modify the circuit of Experiment 1 by inserting the inductors in series with the $\sim 100 \Omega$ load impedances (rheostats). Then, measure and record the DC resistances of the inductors in series with the 100Ω loads, i.e., $R_a + R_{w,a}$, $R_b + R_{w,b}$, and $R_c + R_{w,c}$.
- 3) After ensuring the breaker box is 'off' and that the variac is set to 0, plug in the power cord. If necessary, turn on and zero the wattmeters in **WATT I** mode. Then, put the wattmeters in **200 V** mode to measure the phase voltages. Turn on and ensure the ammeter is properly connected and set for ac current. Turn the breaker box 'on' and **slowly** increase the variac setting until phase voltages of $\sim 63.5 V_{\text{rms}}$ are achieved.
- 4) Measure and record V_{an} , V_{bn} , V_{cn} , I_a , I_b , I_c , P_a , P_b , P_c , I_n , V_{ab} , V_{bc} , and V_{ca} .
- 5) Set the variac to 0 (i.e., rotate dial/knob all the way CCW), turn breaker box off, and unplug the power cord. Do **NOT** disassemble circuit.
- 6) Using the preceding measurements, determine P , S_a , S_b , S_c , S , pf_a , pf_b , pf_c , pf , θ_a , θ_b , θ_c , Z_a , Z_b , Z_c , \bar{Z}_a , \bar{Z}_b , \bar{Z}_c (put in rectangular form), Q_a , Q_b , Q_c , and Q .
- 7) Using \bar{Z}_a , \bar{Z}_b , and \bar{Z}_c , determine the measured values of L_a , L_b , and L_c . How do they compare with the labeled values? Does $\text{Re}(\bar{Z}_a) = R_a + R_{w,a}$, $\text{Re}(\bar{Z}_b) = R_b + R_{w,b}$, and $\text{Re}(\bar{Z}_c) = R_c + R_{w,c}$?
- 8) Tabulate nominal values and calculated answers from part 2 of the preliminary and experiment 2 (e.g., column 1- quantity name, column 2- part 2 answer, column 3- experiment 2 answer, & column 4- % difference, except for complex numbers). List in order measured/calculated in experiment 2. How do the calculated and measured quantities compare? Discuss discrepancies.

Experiment 3

- 1) Connect a balanced Δ - Δ three-phase circuit with load impedances \bar{Z}_{Δ} each consisting of $\sim 100\ \Omega$ load impedances in series with an inductor. Record the labeled values of L_{ab} , L_{bc} , and L_{ca} . Measure and record the dc resistances of the $\sim 100\ \Omega$ loads in series with the inductors, i.e., $R_{ab} + R_{w,ab}$, $R_{bc} + R_{w,bc}$, and $R_{ca} + R_{w,ca}$. A block diagram of the necessary connections, including wattmeters and ammeters, is shown in Fig. 3. Do **NOT** plug in the power cord.

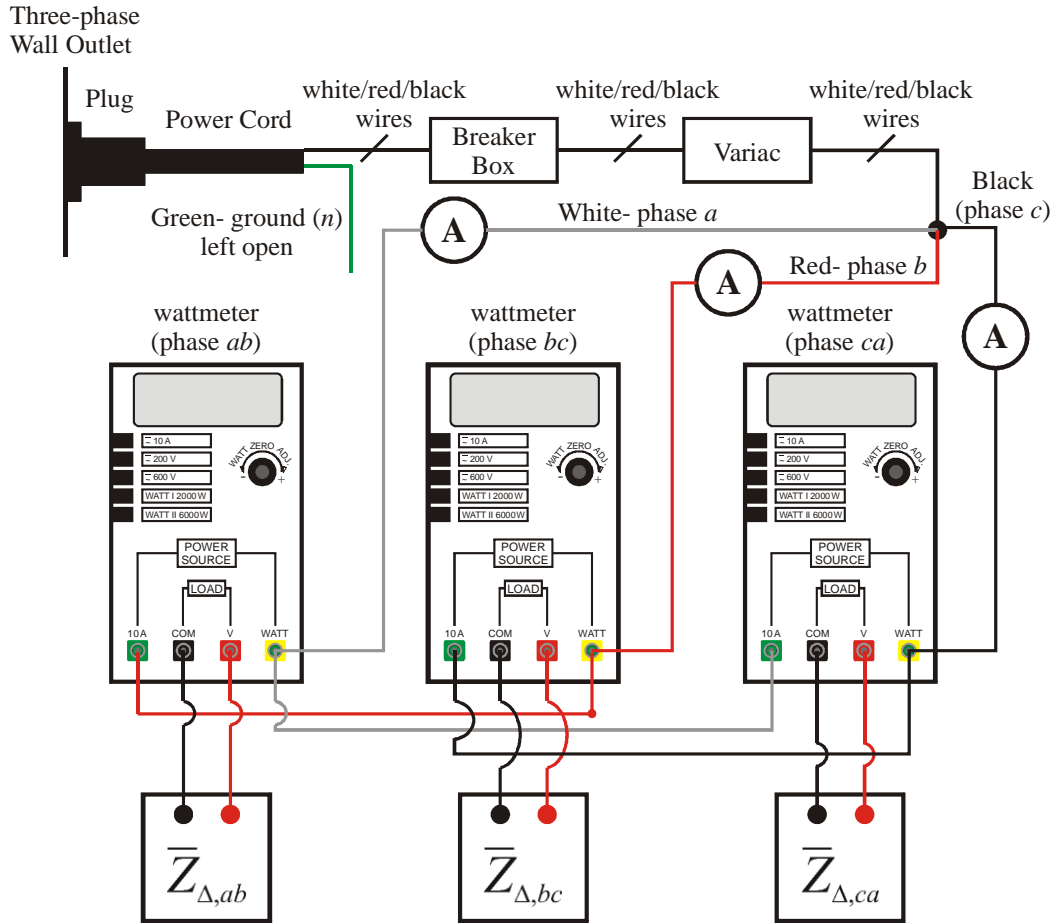


Figure 3 Balanced Δ - Δ three-phase circuit for experiment 4.

- 2) After ensuring the breaker box is 'off' and that the variac is set to 0 (all the way CCW), plug in the power cord. If necessary, turn on and zero the wattmeters in **WATT I** mode. Then, put the wattmeters in **200 V** mode to measure the line-to-line/phase voltages. Turn on and ensure each ammeter (multimeter) is properly connected and set for ac current. Turn the breaker box 'on' and **slowly** increase the variac setting until line-to-line voltages of $\sim 90\ V_{rms}$ are achieved.
- 3) Measure and record the actual line-to-line/phase voltages V_{ab} , V_{bc} , & V_{ca} . Put the wattmeters in **10 A** mode. Measure and record the phase currents I_{ab} , I_{bc} , & I_{ca} . Put the wattmeters in **2000 W** mode. Measure and record the phase powers P_{ab} , P_{bc} , & P_{ca} .
- 4) Using the ammeters, measure and record the line currents I_a , I_b , and I_c .
- 5) Set the variac to 0 (i.e., rotate dial/knob all the way CCW), turn breaker box off, and unplug the power cord. Do **NOT** disassemble circuit.
- 6) Using the preceding measurements, determine the total power P , apparent powers S_{ab} , S_{bc} , & S_{ca} , total apparent power S , power factors pf_{ab} , pf_{bc} , & pf_{ca} , overall power factor pf , impedance phase

angles θ_{ab} , θ_{bc} , & θ_{ca} , load impedance magnitudes Z_{ab} , Z_{bc} , & Z_{ca} , complex impedances \bar{Z}_{ab} , \bar{Z}_{bc} , & \bar{Z}_{ca} (put in rectangular form), reactive phase powers Q_{ab} , Q_{bc} , & Q_{ca} , and total reactive power Q .

- 7) Using \bar{Z}_{ab} , \bar{Z}_{bc} , & \bar{Z}_{ca} , determine the measured values of L_{ab} , L_{bc} , and L_{ca} . Compare with the labeled values. Does $\text{Re}(\bar{Z}_{ab}) = R_{ab} + R_{w,ab}$, $\text{Re}(\bar{Z}_{bc}) = R_{bc} + R_{w,bc}$, and $\text{Re}(\bar{Z}_{ca}) = R_{ca} + R_{w,ca}$?
- 8) Tabulate nominal values and calculated answers from part 3 of the preliminary and experiment 3 (e.g., column 1- quantity name, column 2- part 3 answer, column 3- experiment 3 answer, & column 4- % difference, except for complex numbers). List in order measured/calculated in experiment 3. How do the calculated and measured quantities compare? Discuss discrepancies.

Summary and Conclusions

Summarize and discuss significant findings. Are your results consistent with theory? Why/why not?

Lab Report

- The results should be organized into a typed short report consisting of a Cover Page, Introduction, a Body broken down into subsections/paragraphs based on the steps in the laboratory, and a Summary & Conclusions. Where possible tabulate results.
- Unless otherwise specified, follow format guidelines contained in course syllabus.
- Put the calculations, results, and plots/figures in the body of the report in the order specified. Appendices are **NOT** to be used as a “dumping ground” for the calculations, results, and figures. However, long mathematical derivations may be attached as Appendices **if referenced in the text** of the report. Your logbook is definitely a reference item.

Due Monday, February 6, 2012 by 3 pm.

Deliver lab report and logbook at class, to my office (EP325), or mailbox in ECE office.