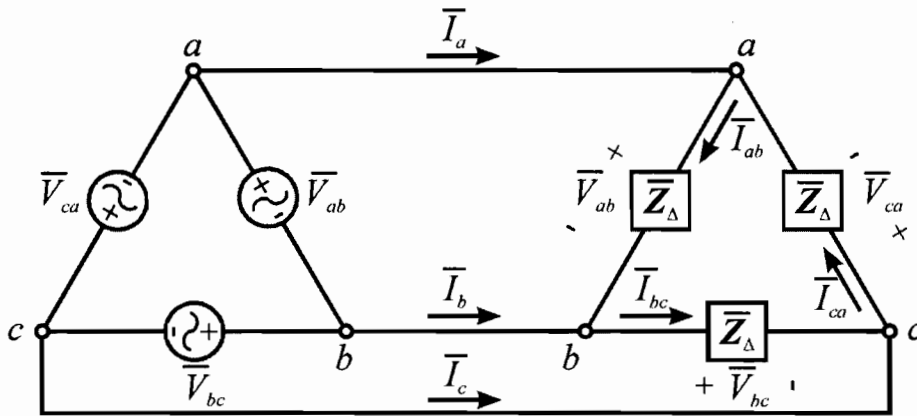


EE 330/330L Energy Systems (Spring 2012) Quiz #1

Name Key A

Instructions: Open notes & homework. Place answers in indicated spaces & show all work for credit.

For the balanced three-phase circuit shown, the phase voltage is measured to be 240 V_{rms} and the load impedance is 16 + j4 Ω. Determine the phase I_φ & line I_L currents and line-to-line voltage V_{LL}. Then, find the real power P, reactive power Q, and apparent power S supplied by the source as well as the power factor pf.



For Δ-source → $V_{LL} = V_{\phi} = 240 \text{ V}_{rms}$ $\bar{Z}_{\phi} = \bar{Z}_{\Delta} = 16 + j4 \Omega$
 (A-14) → $I_{\phi} = \frac{V_{\phi}}{Z_{\phi}} = \frac{240}{16.4924} = 14.55214 \text{ A}_{rms}$
 (A-15) → $I_L = \sqrt{3} I_{\phi} = \sqrt{3} (14.552) = 25.205 \text{ A}_{rms}$

$pf = \cos \theta_2 = \cos 14.036^\circ = 0.9701$ lagging (R-L load)

(A-23) $P = 3 V_{\phi} I_{\phi} \cos \theta = 3(240)(14.55214) 0.9701 = 10,164.3 \text{ W}$

(A-24) $Q = 3 V_{\phi} I_{\phi} \sin \theta = 3(240)(14.55214) \sin 14.03624^\circ = 2541.2 \text{ VAR}$

(A-25) $S = 3 V_{\phi} I_{\phi} = 3(240) 14.55214 = 10,477.5 \text{ VA}$

$I_{\phi} = 14.552 \text{ A}_{rms}$ $I_L = 25.205 \text{ A}_{rms}$ $V_{LL} = 240 \text{ V}_{rms}$ $pf = 0.9701$ lagging

$P = 10.164 \text{ kW}$ $Q = 2.541 \text{ KVAR}$ $S = 10.478 \text{ KVA}$