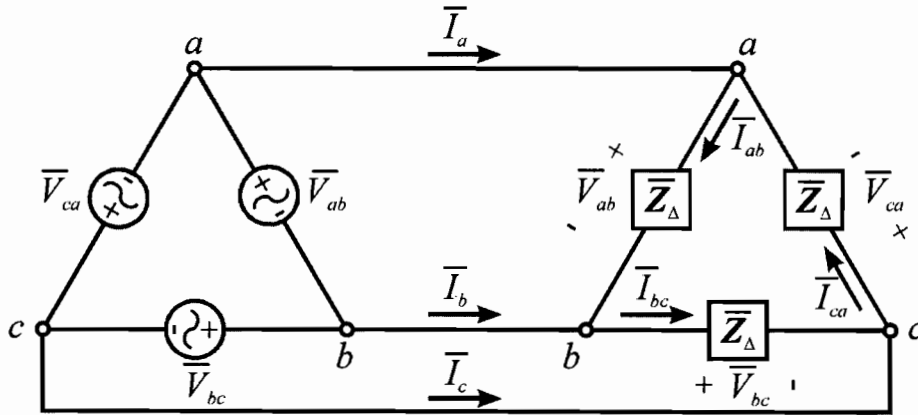


EE 330/330L Energy Systems (Spring 2012) Quiz #1

Name Key B

Instructions: Open notes & homework. Place answers in indicated spaces & show all work for credit.

For the balanced three-phase circuit shown, the phase voltage is measured to be 220 V<sub>rms</sub> and the load impedance is 12 + j3 Ω. Determine the phase I<sub>φ</sub> & line I<sub>L</sub> currents and line-to-line voltage V<sub>LL</sub>. Then, find the real power P, reactive power Q, and apparent power S supplied by the source as well as the power factor pf.



For  $\Delta$ -source (A-14)  $V_{LL} = V_{\phi} = 220 V_{rms}$   
 $\bar{Z}_{\phi} = \bar{Z}_{\Delta} = 12 + j3 \Omega = 12.36932 \angle 14.03624^{\circ} \Omega$   
 $I_{\phi} = \frac{V_{\phi}}{Z_{\phi}} = \frac{220}{12.36932} = 17.785946 A_{rms}$

(A-15)  $I_L = \sqrt{3} I_{\phi} = 30.8061618 A_{rms}$

$pf = \cos \theta_z = \cos 14.03624^{\circ} = 0.97014$  lagging (R-L Load)

(A-23)  $P = 3 V_{\phi} I_{\phi} \cos \theta = 3(220)(17.786) 0.97014 = 11,388.2 W$

(A-24)  $Q = 3 V_{\phi} I_{\phi} \sin \theta = 3(220)(17.786) \sin 14.036^{\circ} = 2847.06 VAR$

(A-25)  $S = 3 V_{\phi} I_{\phi} = 3(220)(17.786) = 11,738.7 VA$

$I_{\phi} = 17.786 A_{rms}$     $I_L = 30.806 A_{rms}$     $V_{LL} = 220 V_{rms}$     $pf = 0.9701$  lagging

$P = 11.388 kW$     $Q = 2.847 kVAR$     $S = 11.739 kVA$