

EE 330/330L Energy Systems (Spring 2012) Quiz #3

Name Key A

Instructions: Open book. Place answers in indicated spaces & show all work for credit.

A 220 KVA, 8000/240 V, 60 Hz single-phase transformer has a per-unit resistance of 1.1%, per-unit reactance of 4%, per-unit core loss resistance of 85, and per-unit magnetizing reactance of 22. Determine the turns ratio, base impedance, and approximate transformer circuit model referred to the secondary side. A load is supplied the rated voltage and load at a pf of 0.825 lagging. Determine the RMS phasor load current and load power. Use load voltage as phase reference.


$$V_{base} = 240 V_{rms}, \quad (2-57) \quad Z_{base} = \frac{V_{base}^2}{S_{base}} = \frac{240^2}{220 \times 10^3} = \underline{\underline{0.2618 \Omega}}$$

$$R_{eq,s} = R_{eq,pu} Z_{base} = 0.011(0.2618) = 0.00288 \Omega$$

$$X_{eq,s} = X_{eq,pu} Z_{base} = 0.04(0.2618) = 0.010472 \Omega$$

$$R_{c,s} = R_{c,pu} Z_{base} = 85(0.2618) = 22.254 \Omega \quad X_{m,s} = X_{m,pu} Z_{base} = 22(0.2618) = 5.76 \Omega$$

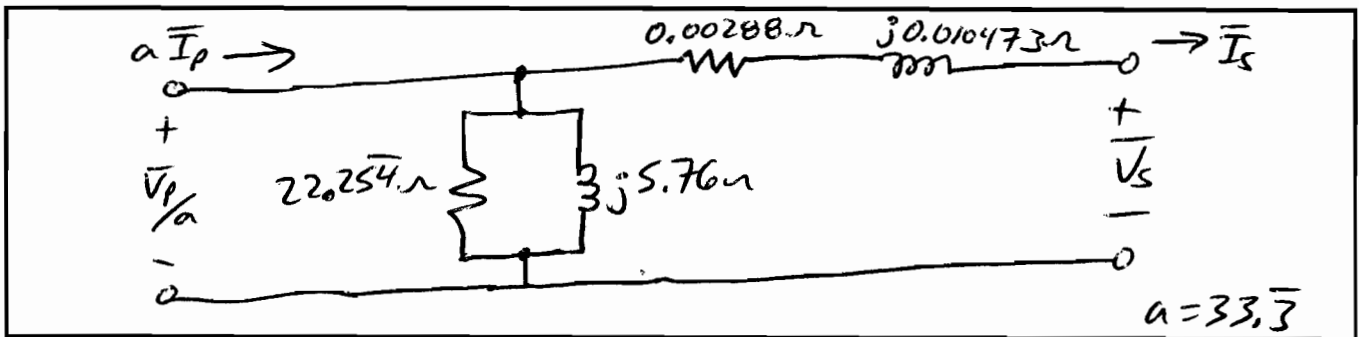Secondary side approximate transformer circuit model



$$a = \frac{V_p}{V_s} = \frac{8000}{240} = \underline{\underline{33.3}}$$

$$I_L = \frac{S_{rated}}{V_{rated}} = \frac{220 \times 10^3}{240} = 916.6 A_{rms}$$

$$\theta = \cos^{-1} pf = \cos^{-1} 0.825 = 34.4115^\circ = \phi - \theta_I \Rightarrow \theta_I = -34.4115^\circ$$

$$P_L = S_L (pf) = V_L I_L \cos \theta = 220 \times 10^3 (0.825) = \underline{\underline{181.5 kW}}$$

turns ratio = 33.3 base impedance = 0.2618 Ω  $I_L = 916.6 \angle -34.4^\circ A_{rms}$   $P_L = 181.5 kW$