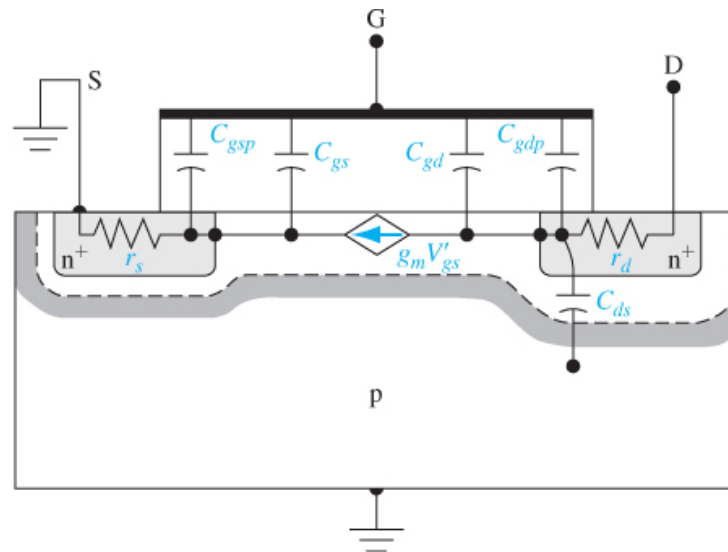


From *Semiconductor Physics and Devices: Basic Principles* (4th Edition), Donald A. Neamen, McGraw Hill, 2012, ISBN 978-0-07-352958-5.


## n-channel MOSFET



**Figure 10.52** | Inherent resistances and capacitances in the n-channel MOSFET structure.

- Note that the body (B) and source (S) are both grounded (common-source).
- There are gate-source  $C_{gs}$  and gate-drain  $C_{gd}$  capacitances to represent the interaction between the gate and the channel charges on each end (D & S).
- In addition, there are parasitic gate-source  $C_{gsp}$  and gate-drain  $C_{gdp}$  capacitances due to manufacturing issues which cause gate oxide and the drain & source regions to overlap.  $C_{gsp} = C_{ox}$  (gate-source overlap area) and  $C_{gdp} = C_{ox}$  (gate-drain overlap area).
- There is a drain-to-substrate  $C_{ds}$  capacitance to represent the pn junction capacitance. [Not needed for source-to-substrate as they are both grounded.]
- The drain and source will have some series resistances,  $r_d$  and  $r_s$ .
- Lastly, we have the voltage-controlled current-source (VCCS) element,  $g_m V'_{gs}$ , to represent the I-V relation of the MOSFET.
- The transconductance  $g_m$  was defined earlier.
- The internal gate-to-source voltage is  $V'_{gs}$  is what controls the current through the channel. It is the gate-to-source voltage less the voltage drop across the source resistance  $r_s$ .

## Small-signal circuit model for common-source n-channel MOSFET

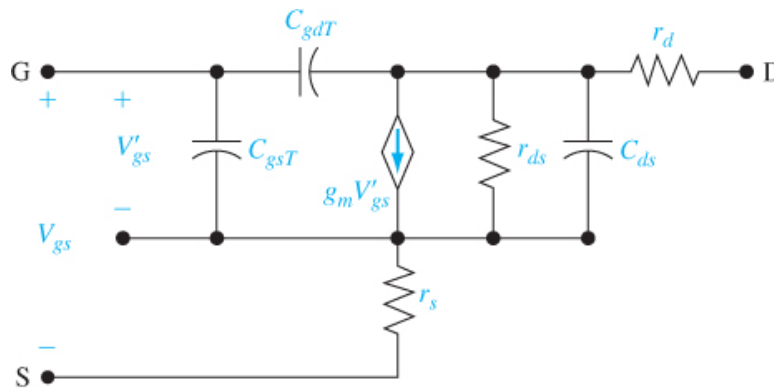

**Figure 10.53** | Small-signal equivalent circuit of a common-source n-channel MOSFET.


- This small-signal model uses total gate-source  $C_{gsT} = C_{gs} + C_{gsp}$  and total gate-drain  $C_{gdT} = C_{gd} + C_{gdp}$  capacitances, i.e., combine regular and parasitic capacitances.
- Model adds a resistance  $r_{ds}$  to account for slope of MOSFET I-V curve. In saturation,  $r_{ds} \rightarrow \infty$ .
- For p-channel model, reverse voltage polarities and current directions.

### Low frequency small-signal circuit models

- At low frequencies, the capacitors act like open circuits.
- Note that the impedance looking into the gate is infinite in both models.

#### **Model 1**


- Neglect  $r_s$  and  $r_d$ , but keep  $r_{ds}$ .

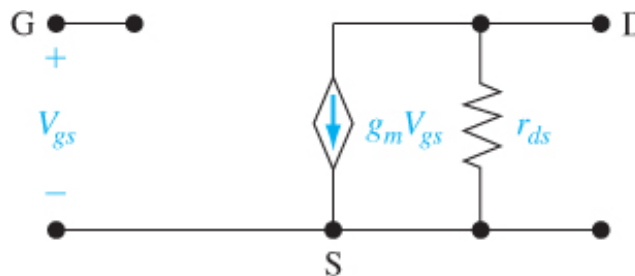

**Figure 10.54** | Simplified, low-frequency small-signal equivalent circuit of a common-source n-channel MOSFET.

**Model 2**

➤ Neglect  $r_{ds}$  and  $r_d$ , but keep  $r_s$ .

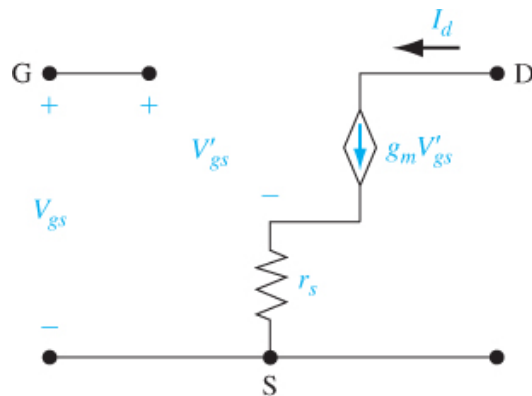

**Figure 10.55** | Simplified, low-frequency small-signal equivalent circuit of common-source n-channel MOSFET including source resistance  $r_s$ .

➤ Here,  $I_d = g_m V'_{gs}$ .

➤ By KVL,  $V_{gs} = V'_{gs} + I_d r_s = V'_{gs} + g_m V'_{gs} r_s = (1 + g_m r_s) V'_{gs}$ .

➤ Combining these two equations, we get  $I_d = \left( \frac{g_m}{1 + g_m r_s} \right) V_{gs} = g'_m V_{gs}$  where

$g'_m = \frac{g_m}{1 + g_m r_s}$  is the effective transconductance which is less than  $g_m$ .