
 


From *Semiconductor Physics and Devices: Basic Principles* (4th Edition), Donald A. Neamen, McGraw Hill, 2012, ISBN 978-0-07-352958-5.

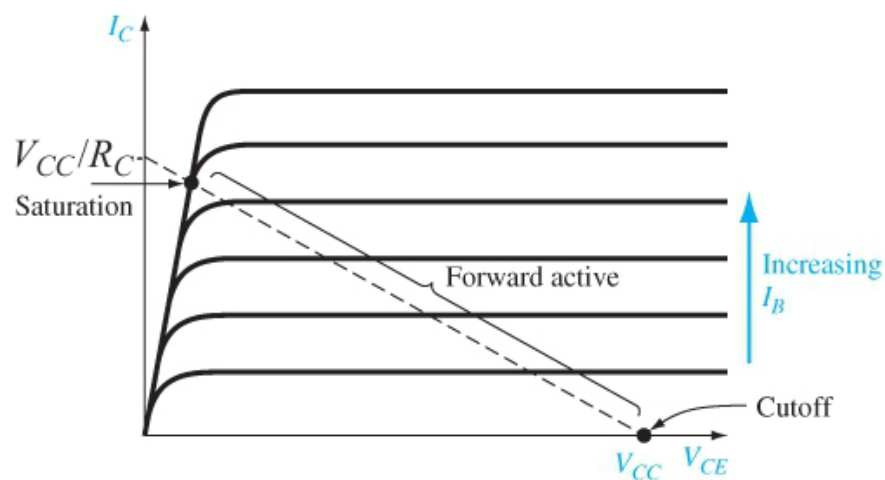

**Figure 12.8** | An npn bipolar transistor in a common-emitter circuit configuration.

- BY KVL around the RH loop  $V_{CC} = I_C R_C + V_{CB} + V_{BE} = V_R + V_{CE}$
- For  $V_{BE} > 0$  (forward biased) with  $V_{CC}$  large enough and  $V_R$  small enough  $V_{CB} > 0 \Rightarrow BC$  pn junction is reverse biased (active mode).
- As  $V_{BE}$  increases,  $I_C = I_S e^{v_{BE}/V_t}$  increases. In turn,  $V_R = I_C R_C$  increases enough that  $V_{CB} \leq 0 \Rightarrow BC$  pn junction is forward biased (**saturation** mode).  $I_C$  does NOT depend on  $V_{BE}$  at this point and is essentially limited only by  $R_C$ ,  $I_C \rightarrow V_{CC} / R_C$ .



**Figure 12.9** | Bipolar transistor common-emitter current–voltage characteristics with load line superimposed.

- BY KVL,  $V_{CE} = V_{CC} - I_C R_C$ . This is called the load line equation (dashed line in Figure 12.9).