

**10.56** An n-channel MOSFET has the following parameters:

$$\begin{aligned}\mu_n &= 400 \text{ cm}^2/\text{V-s} & t_{ox} &= 500 \text{ \AA} \\ L &= 2 \mu\text{m} & W &= 20 \mu\text{m} \\ V_T &= +0.75 \text{ V}\end{aligned}$$

Assume the transistor is biased in the saturation region at  $V_{GS} = 4 \text{ V}$ . (a) Calculate the ideal cutoff frequency. (b) Assume that the gate oxide overlaps both the source and drain contacts by  $0.75 \mu\text{m}$ . If a load resistance of  $R_L = 10 \text{ k}\Omega$  is connected to the output, calculate the cutoff frequency.

a) Per (10.96),  $f_T = \frac{\mu_n(V_{GS} - V_T)}{2\pi L^2}$

using MICS units

$$f_T = \frac{400 \times 10^{-4} (4 - 0.75)}{2\pi (2 \times 10^{-6})^2}$$

$$\underline{\underline{f_T = 5.172536 \times 10^9 \text{ Hz} = 5.1725 \text{ GHz}}}$$

b) Per Table B.6,  $\epsilon_r = 3.9$  for  $\text{SiO}_2$  @ 300K

$$\text{Per (10.35), } C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{3.9(8.8541878 \times 10^{-12})}{500 \times 10^{-10}} \\ = 6.906266 \times 10^{-14} \text{ F/m}^2$$

$$\begin{aligned}\text{Overlap area } A_{overlap} &= W_{overlap} \\ &= 20 \times 10^{-6} (0.75 \times 10^{-6}) \\ &= 1.5 \times 10^{-11} \text{ m}^2\end{aligned}$$

Parasitic capacitances

$$\begin{aligned}C_{sd\beta} &= C_{ss\beta} = C_{ox} A_{overlap} = 6.906 \times 10^{-14} (1.5 \times 10^{-11}) \\ &= 1.03594 \times 10^{-14} \text{ F}\end{aligned}$$

b) cont. With transistor in saturation, per page 426 of text,

$$C_{gs} = C_{ox} WL = 6.906 \times 10^{-4} (20 \times 10^{-6}) / (2 \times 10^{-6}) \\ = 2.76251 \times 10^{-14} F$$

$$C_{gd} = 0$$

$$C_{gdt} = C_{sd} + C_{sdp} = 0 + 1.03594 \times 10^{-14} F$$

$$C_{gst} = C_{gs} + C_{sdp} = 2.76251 \times 10^{-14} + 1.03594 \times 10^{-14} \\ = 3.79845 \times 10^{-14} F$$

$$\text{Per (10.77), } g_{ms} = \frac{W M_n C_{ox}}{L} (V_{bs} - V_T) \\ = \frac{20 \times 10^{-6} (400 \times 10^{-4}) 6.906 \times 10^{-4}}{2 \times 10^{-6}} (4 - 0.75) \\ = 8.97815 \times 10^{-4} S$$

$$\text{Per (10.91), } C_m = C_{gdt} (1 + g_{ms} R_L) \\ = 1.03594 \times 10^{-14} (1 + 8.978 \times 10^{-4} (10 \times 10^3)) \\ = 1.033676 \times 10^{-13} F$$

$$\text{Per (10.95), } f_T = \frac{g_{ms}}{2\pi(C_{gst} + C_m)} \\ = \frac{8.97815 \times 10^{-4}}{2\pi (3.79845 \times 10^{-14} + 1.033676 \times 10^{-13})}$$

$$\underline{\underline{f_T = 1.0109 \times 10^9 Hz = 1.0109 GHz}}$$