

Ex. Check to see if the Belden 9085 twin-lead transmission line is distortionless and/or low loss at 100 MHz.

***** From earlier example *****

Quantities that we looked up or were given:

$$\epsilon_0 := 8.85419 \cdot 10^{-12} \text{ F/m} \quad \mu_0 := 4 \cdot \pi \cdot 10^{-7} \text{ H/m} \quad f := 100 \cdot 10^6 \text{ Hz}$$

$$a := 0.5 \cdot (0.644 \cdot 10^{-3}) \quad a = 3.22 \times 10^{-4} \text{ m} \quad d := 7.4 \cdot 10^{-3} \text{ m}$$

$$\sigma_{\text{ccs}} := 1 \cdot 10^7 \text{ S/m} \quad \epsilon_{\text{ccs}} := \epsilon_0 \quad \mu_{\text{ccs}} := \mu_0$$

$$\sigma_{\text{poly}} := 3 \cdot 10^{-5} \text{ S/m} \quad \epsilon_{\text{poly}} := 2.26 \cdot \epsilon_0 \quad \mu_{\text{poly}} := \mu_0$$

$$\sigma_{\text{eff}} := 0.45 \cdot \sigma_{\text{poly}} \quad \epsilon_{\text{eff}} := 0.55 \cdot \epsilon_0 + 0.45 \cdot \epsilon_{\text{poly}} \quad \mu_{\text{eff}} := \mu_0$$

Use Table 11.1 equations to find per-unit-length parameters

$$\delta := \frac{1}{\sqrt{\pi \cdot f \cdot \mu_{\text{ccs}} \cdot \sigma_{\text{ccs}}}} \quad \delta = 1.592 \times 10^{-5} \text{ m}$$

$$\frac{\delta}{a} = 0.049$$

Check if $\delta \ll a$ to ensure equations are valid.

$$R := \frac{1}{\pi \cdot a \cdot \delta \cdot \sigma_{\text{ccs}}} \quad R = 6.21118 \text{ } \Omega/\text{m}$$

$$L := \frac{\mu_{\text{eff}}}{\pi} \cdot \text{acosh}\left(\frac{d}{2 \cdot a}\right) \quad L = 1.25311 \times 10^{-6} \text{ H/m}$$

$$G := \frac{\pi \cdot \sigma_{\text{eff}}}{\text{acosh}\left(\frac{d}{2 \cdot a}\right)} \quad G = 1.3538 \times 10^{-5} \text{ S/m}$$

$$C := \frac{\pi \cdot \epsilon_{\text{eff}}}{\text{acosh}\left(\frac{d}{2 \cdot a}\right)} \quad C = 1.39135 \times 10^{-11} \text{ F/m}$$

Check if Belden 9085 is distortionless per (11.22)-

$$\frac{R}{L} = 4.9566 \times 10^6$$

$$\frac{G}{C} = 9.7301 \times 10^5$$

Since R/L is NOT equal to G/C , Belden 9085 has distortion.

Check if Belden 9085 is low loss at 100 MHz-

$$\omega := 2 \cdot \pi \cdot f$$

Is $R \ll \omega L$ (i.e., $R/\omega L \ll 1$)?

$$\frac{R}{\omega \cdot L} = 0.00789 \quad \text{Yes}$$

Is $G \ll \omega C$ (i.e., $G/\omega C \ll 1$)?

$$\frac{G}{\omega \cdot C} = 0.00155 \quad \text{Yes}$$

Belden 9085 is low loss at 100 MHz!

How good are the low loss approximations?

Propagation constant

$$(11.11) \quad \gamma := \sqrt{(R + j \cdot \omega \cdot L) \cdot (G + j \cdot \omega \cdot C)} \quad \boxed{\gamma = 0.01238 + 2.62359i} \quad 1/m$$

$$\gamma_{LL} := j \cdot \omega \cdot \sqrt{L \cdot C} \cdot \left[1 + \frac{1}{2 \cdot j \cdot \omega} \cdot \left(\frac{R}{L} + \frac{G}{C} \right) \right] \quad \boxed{\gamma_{LL} = 0.01238 + 2.62358i} \quad 1/m$$

Attenuation constant $\alpha := \text{Re}(\gamma)$ $\boxed{\alpha = 0.01238}$ Np/m

$$\alpha_{LL} := 0.5 \cdot \left(R \cdot \sqrt{\frac{C}{L}} + G \cdot \sqrt{\frac{L}{C}} \right) \quad \boxed{\alpha_{LL} = 0.01238} \quad \text{Np/m}$$

Phase constant $\beta := \text{Im}(\gamma)$ $\boxed{\beta = 2.62359}$ rad/m

$$\beta_{LL} := \omega \cdot \sqrt{L \cdot C} \quad \boxed{\beta_{LL} = 2.62358} \quad \text{rad/m}$$

Phase velocity (11.14) $u := \frac{\omega}{\beta}$ $\boxed{u = 2.39488 \times 10^8}$ m/s

$$u_{LL} := \frac{1}{\sqrt{L \cdot C}} \quad \boxed{u_{LL} = 2.39489 \times 10^8} \quad \text{m/s}$$

Characteristic Impedance (11.19) $Z_0 := \sqrt{\frac{R + j \cdot \omega \cdot L}{G + j \cdot \omega \cdot C}}$ $\boxed{Z_0 = 300.11039 - 0.95134i}$ Ω

$$Z_{0LL} := \sqrt{\frac{L}{C}} \cdot \left[1 + \frac{1}{2 \cdot j \cdot \omega} \cdot \left(\frac{R}{L} - \frac{G}{C} \right) \right] \quad \boxed{Z_{0LL} = 300.10741 - 0.95135i} \quad \Omega$$

The low loss approximations are excellent for Belden 9085 at 100 MHz.