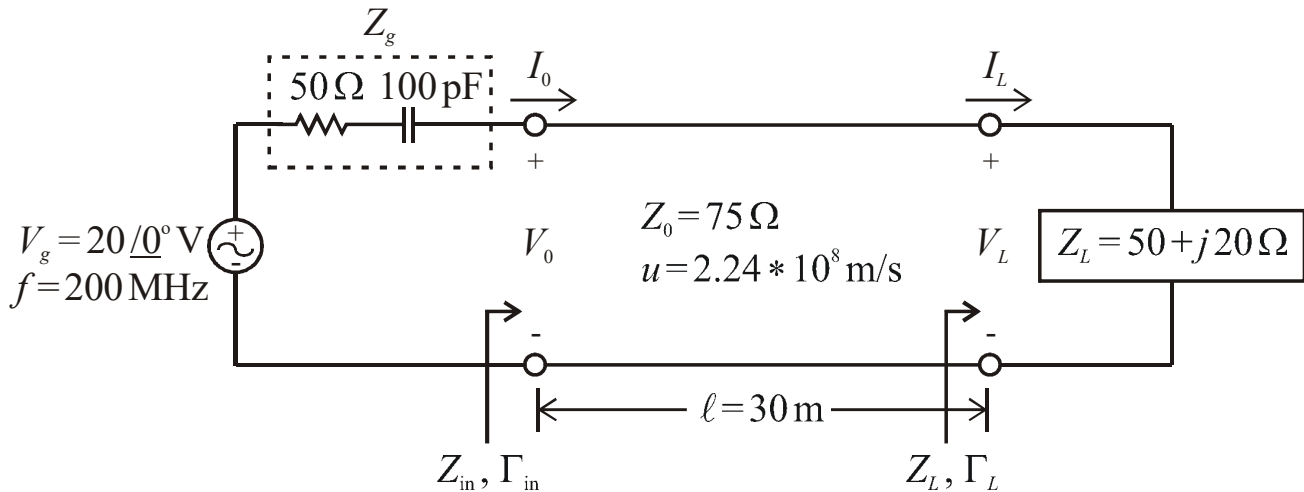


## EE 381 Lossless Transmission Line example with power

For the circuit shown below, calculate the standing wave ratio as well as input & load currents, voltages, powers, reflection coefficients, and impedances. Also, plot the magnitude of the current and voltage as a function of position near generator.



### Enter given information

$$V_g := 20 \cdot e^{j \cdot 0 \cdot \frac{\pi}{180}} \text{ V} \quad f := 200 \cdot 10^6 \text{ Hz} \quad R_g := 50 \text{ } \Omega \quad C_g := 100 \cdot 10^{-12} \text{ F}$$

$$\underline{L} := 30 \text{ m} \quad u := 2.24 \cdot 10^8 \text{ m/s} \quad Z_0 := 75 \text{ } \Omega \quad Z_L := 50 + j \cdot 20 \text{ } \Omega$$

### Calculate variables related to generator and transmission line

$$\omega := 2 \cdot \pi \cdot f \quad \omega = 1.257 \times 10^9 \text{ rad/s} \quad \beta := \frac{\omega}{u} \quad \beta = 5.61 \text{ rad/m}$$

$$Z_g := R_g - \frac{j}{2 \cdot \pi \cdot f \cdot C_g} \quad Z_g = 50 - 7.9577i \text{ } \Omega \quad \lambda := \frac{u}{f} \quad \lambda = 1.12 \text{ m}$$

### Calculate reflection coefficients and SWR


$$\Gamma_L := \frac{Z_L - Z_0}{Z_L + Z_0} \quad |\Gamma_L| = 0.2529 \quad \arg(\Gamma_L) \cdot \frac{180}{\pi} = 132.25 \text{ deg}$$

$$\Gamma_{in} := \Gamma_L \cdot e^{-j \cdot 2 \cdot \beta \cdot L} \quad |\Gamma_{in}| = 0.2529 \quad \arg(\Gamma_{in}) \cdot \frac{180}{\pi} = -73.464 \text{ deg}$$

$$\text{SWR} := \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} \quad \text{SWR} = 1.677$$

**Calculate input impedance**

$$Z_{in} := Z_0 \cdot \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} \quad \boxed{Z_{in} = 76.3073 - 39.5296i} \quad \Omega$$

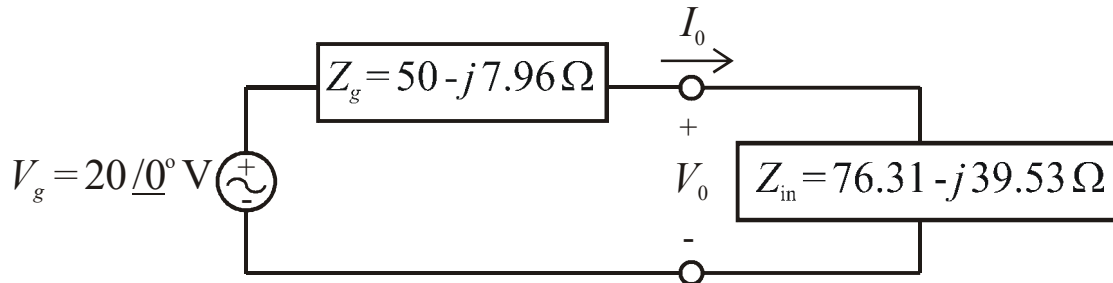**Calculate input current, voltage, and power using equivalent circuit**

$$I_0 := \frac{V_g}{Z_g + Z_{in}} \quad \boxed{|I_0| = 0.1482} \quad \text{A} \quad \boxed{\arg(I_0) \cdot \frac{180}{\pi} = 20.605} \quad \text{deg}$$

$$V_0 := V_g \cdot \frac{Z_{in}}{Z_g + Z_{in}} \quad \boxed{|V_0| = 12.7373} \quad \text{V} \quad \boxed{\arg(V_0) \cdot \frac{180}{\pi} = -6.781} \quad \text{deg}$$

$$P_{ave\_in} := 0.5 \cdot \text{Re}(V_0 \cdot \bar{I}_0) \quad \boxed{P_{ave\_in} = 0.8381} \quad \text{W}$$

**Calculate phasor forward traveling voltage wave amplitude  $V_0^+$** 

$$V_{fwd} := \frac{V_0}{1 + \Gamma_{in}} \quad |V_{fwd}| = 11.5893 \quad \text{V} \quad \arg(V_{fwd}) \cdot \frac{180}{\pi} = 5.963 \quad \text{deg}$$

**Define reflection coefficient, phasor current & voltage in terms of position**

$$\Gamma(z) := \Gamma_L \cdot e^{-j \cdot 2 \cdot \beta \cdot (L-z)}$$

$$I_s(z) := \frac{V_{fwd}}{Z_0} \cdot e^{-j \cdot \beta \cdot z} \cdot (1 - \Gamma(z)) \quad V_s(z) := V_{fwd} \cdot e^{-j \cdot \beta \cdot z} \cdot (1 + \Gamma(z))$$

**Calculate the load current, voltage, and power**



$$I_L := I_s(L) \quad \boxed{|I_L| = 0.1831} \quad \text{A} \quad \boxed{\arg(I_L) \cdot \frac{180}{\pi} = 74.016} \quad \text{deg}$$

$$V_L := V_s(L) \quad \boxed{|V_L| = 9.8603} \quad \text{V} \quad \boxed{\arg(V_L) \cdot \frac{180}{\pi} = 95.817} \quad \text{deg}$$

$$P_{ave\_L} := 0.5 \cdot \text{Re}(V_L \cdot \bar{I}_L) \quad \boxed{P_{ave\_L} = 0.83815} \quad \text{W} \quad \text{Same as input power!}$$

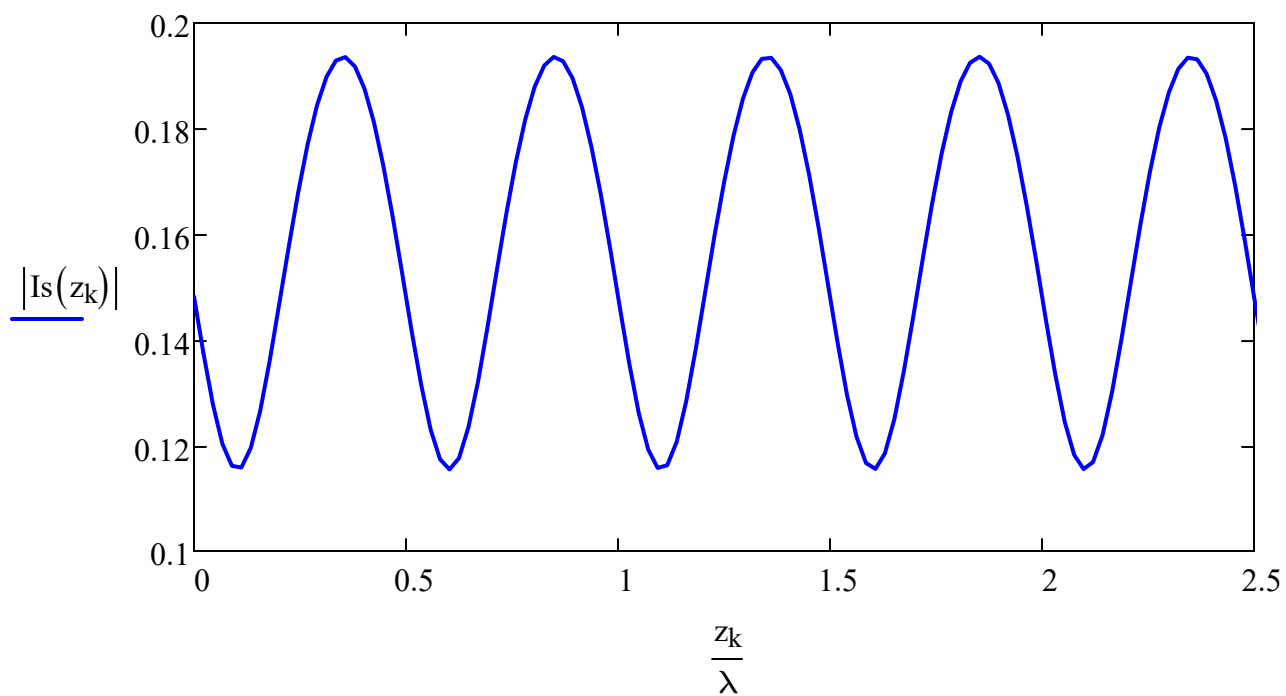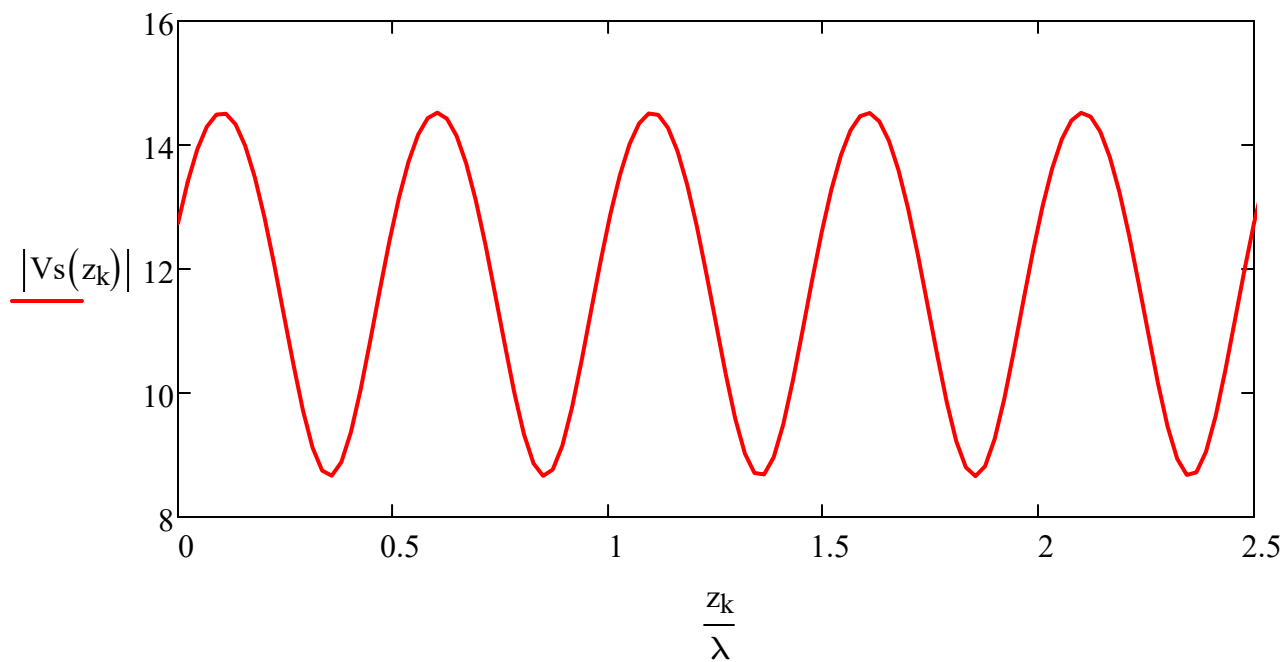**Plot the magnitude of the current & voltage as functions of position**

$$k := 0..1200 \quad z_k := \frac{k}{1200} \cdot L$$





**Everything repeats at  $\lambda/2$  intervals!**
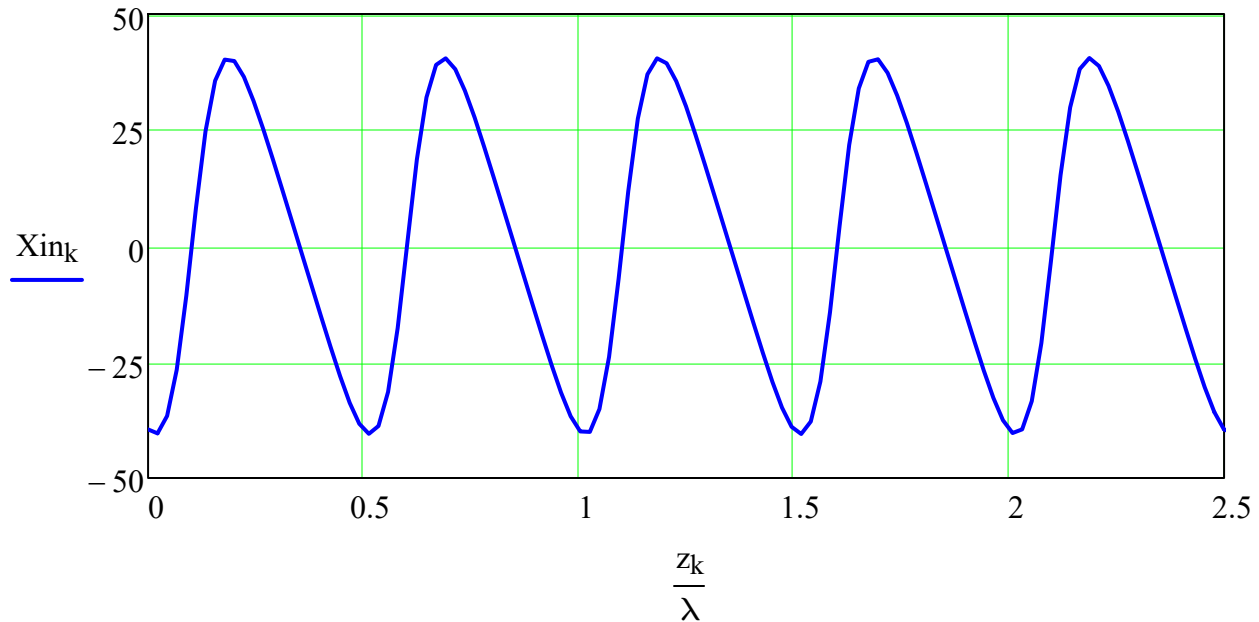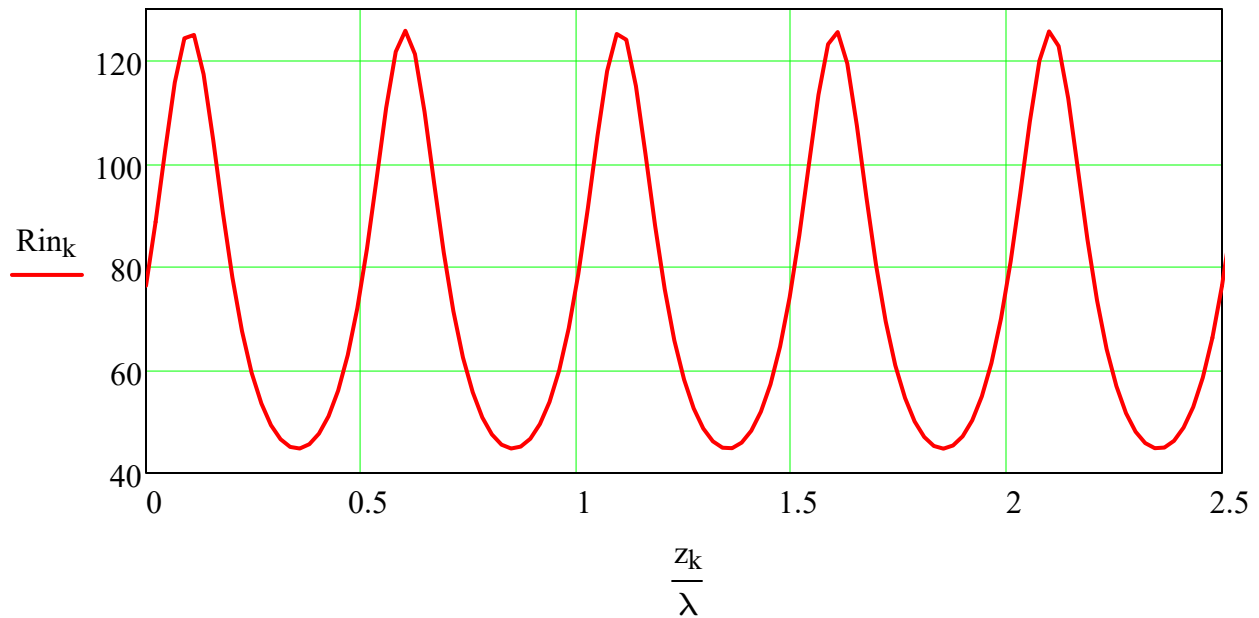
## Plot the input impedance as a function of position near the generator

$$\underline{Z}_{in_k} := Z_0 \cdot \left( \frac{1 + \Gamma(z_k)}{1 - \Gamma(z_k)} \right) \quad R_{in_k} := \text{Re}(Z_{in_k}) \quad X_{in_k} := \text{Im}(Z_{in_k})$$

Remember  $Z_{in}$  is complex, separate the real & imaginary parts for plotting.



**Everything repeats at  $\lambda/2$  intervals!**