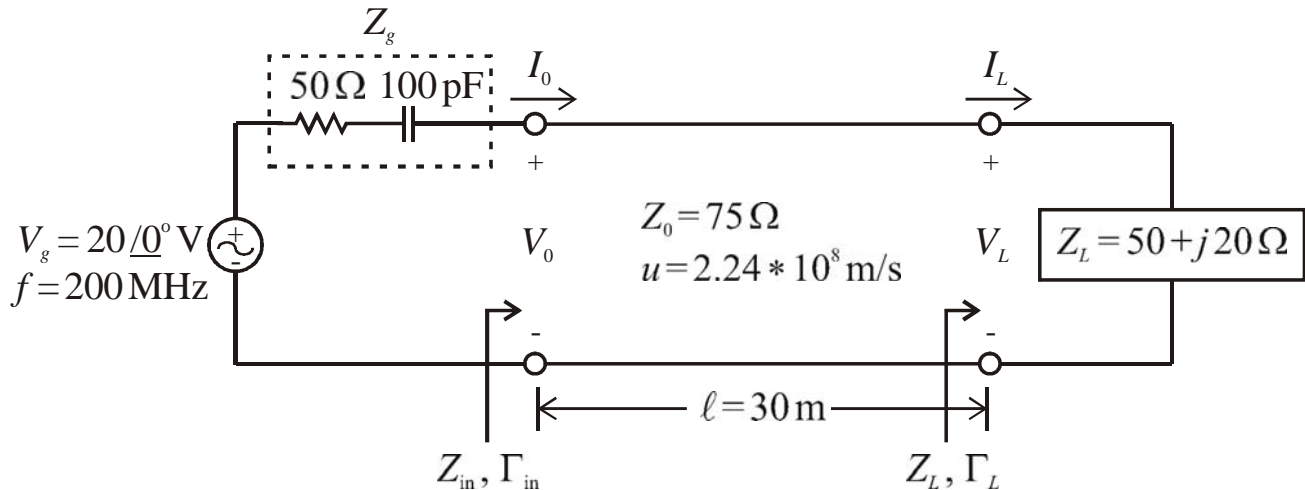


EE381 Lossless Transmission Line example with power

For the circuit shown below, calculate the standing wave ratio as well as input & load currents, voltages, powers, reflection coefficients, and impedances. Also, plot the magnitude of the current and voltage as a function of position.



Enter given information

$$V_g := 20 \cdot e^{j \cdot 0 \cdot \frac{\pi}{180}} \text{ V} \quad f := 200 \cdot 10^6 \text{ Hz} \quad L := 30 \text{ m} \quad u := 2.24 \cdot 10^8 \text{ m/s}$$

$$R_g := 50 \text{ } \Omega \quad C_g := 100 \cdot 10^{-12} \text{ F} \quad Z_0 := 75 \text{ } \Omega \quad Z_L := 50 + j \cdot 20 \text{ } \Omega$$

Calculate variables related to generator and transmission line

$$\omega := 2 \cdot \pi \cdot f \quad \omega = 1.257 \times 10^9 \text{ rad/s} \quad \beta := \frac{\omega}{u} \quad \beta = 5.61 \text{ rad/m}$$

$$Z_g := R_g - \frac{j}{2 \cdot \pi \cdot f \cdot C_g} \quad Z_g = 50 - 7.9577i \text{ } \Omega \quad \lambda := \frac{u}{f} \quad \lambda = 1.12 \text{ m}$$

Ex. cont.**Calculate reflection coefficients and SWR**


$$\Gamma_L := \frac{Z_L - Z_0}{Z_L + Z_0} \quad \boxed{|\Gamma_L| = 0.2529} \quad \boxed{\arg(\Gamma_L) \cdot \frac{180}{\pi} = 132.25} \text{ deg}$$

$$\Gamma_0 := \Gamma_L \cdot e^{-j \cdot 2 \cdot \beta \cdot L} \quad \boxed{|\Gamma_0| = 0.2529} \quad \boxed{\arg(\Gamma_0) \cdot \frac{180}{\pi} = -73.464} \text{ deg}$$

$$\text{SWR} := \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} \quad \boxed{\text{SWR} = 1.677}$$

Calculate input impedance

$$Z_{in} := Z_0 \cdot \frac{(1 + \Gamma_0)}{1 - \Gamma_0} \quad \boxed{Z_{in} = 76.3073 - 39.5296i} \quad \Omega$$

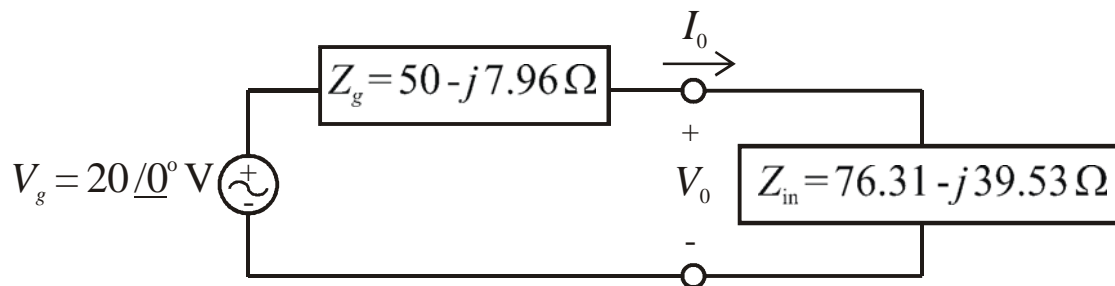Calculate input current, voltage, and power using equivalent circuit

$$I_0 := \frac{V_g}{Z_g + Z_{in}} \quad \boxed{|I_0| = 0.1482} \text{ A} \quad \boxed{\arg(I_0) \cdot \frac{180}{\pi} = 20.605} \text{ deg}$$

$$V_0 := V_g \cdot \frac{Z_{in}}{Z_g + Z_{in}} \quad \boxed{|V_0| = 12.7373} \text{ V} \quad \boxed{\arg(V_0) \cdot \frac{180}{\pi} = -6.781} \text{ deg}$$

$$P_{ave_0} := 0.5 \cdot \text{Re}(V_0 \cdot \bar{I}_0) \quad \boxed{P_{ave_0} = 0.8381} \text{ W}$$

Ex. cont.**Calculate phasor forward traveling voltage wave**

$$V_{\text{fwd}} := \frac{V_0}{1 + \Gamma_0} \quad |V_{\text{fwd}}| = 11.5893 \quad \text{V} \quad \arg(V_{\text{fwd}}) \cdot \frac{180}{\pi} = 5.963 \quad \text{deg}$$

Define refl. coeff., phasor current & voltage in terms of position

$$\Gamma(z) := \Gamma_L \cdot e^{-j \cdot 2 \cdot \beta \cdot (L-z)}$$

$$I_s(z) := \frac{V_{\text{fwd}}}{Z_0} \cdot e^{-j \cdot \beta \cdot z} \cdot (1 - \Gamma(z)) \quad V_s(z) := V_{\text{fwd}} \cdot e^{-j \cdot \beta \cdot z} \cdot (1 + \Gamma(z))$$

Calculate the load current, voltage, and power


$$I_L := I_s(L) \quad |I_L| = 0.1831 \quad \text{A} \quad \arg(I_L) \cdot \frac{180}{\pi} = 74.016 \quad \text{deg}$$




$$V_L := V_s(L) \quad |V_L| = 9.8603 \quad \text{V} \quad \arg(V_L) \cdot \frac{180}{\pi} = 95.817 \quad \text{deg}$$



$$P_{\text{ave}_L} := 0.5 \cdot \text{Re}(V_L \cdot \overline{I_L}) \quad P_{\text{ave}_L} = 0.83815 \quad \text{W}$$

Plot the magnitude of the current & voltage as functions of position
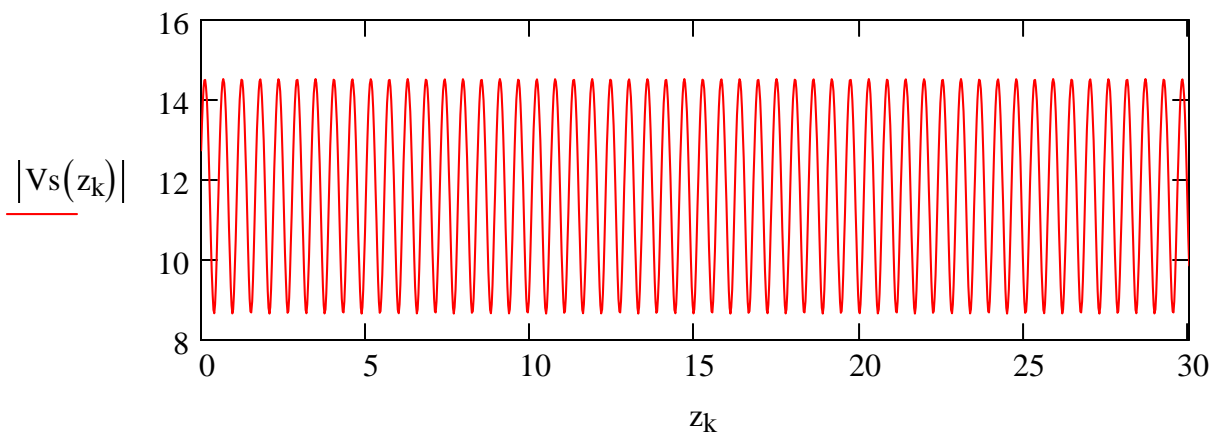
$$k := 0 .. 1200 \quad z_k := \frac{k}{1200} \cdot L$$



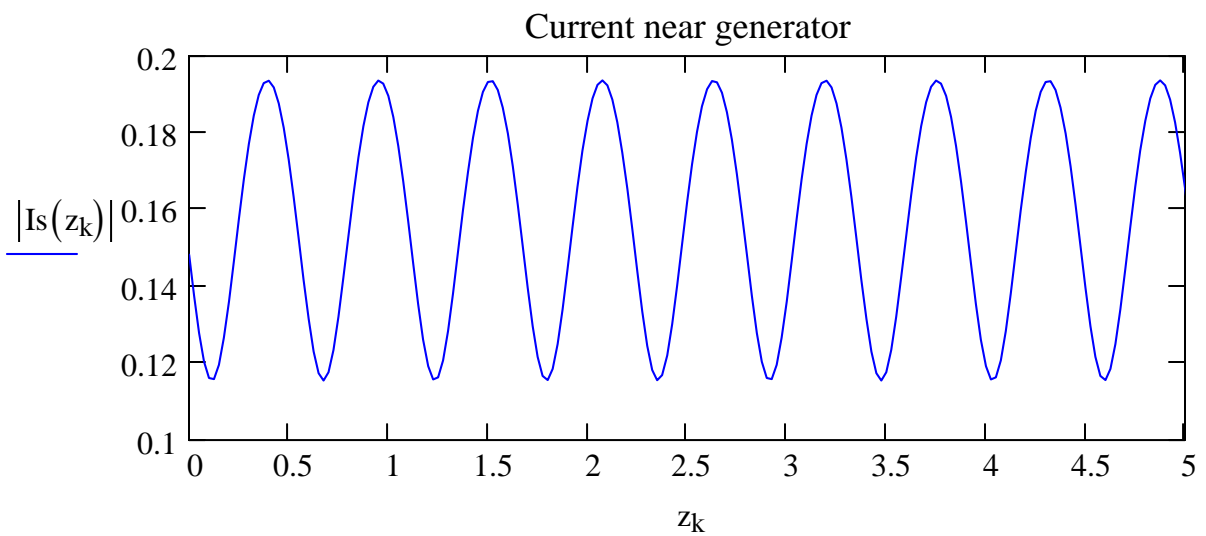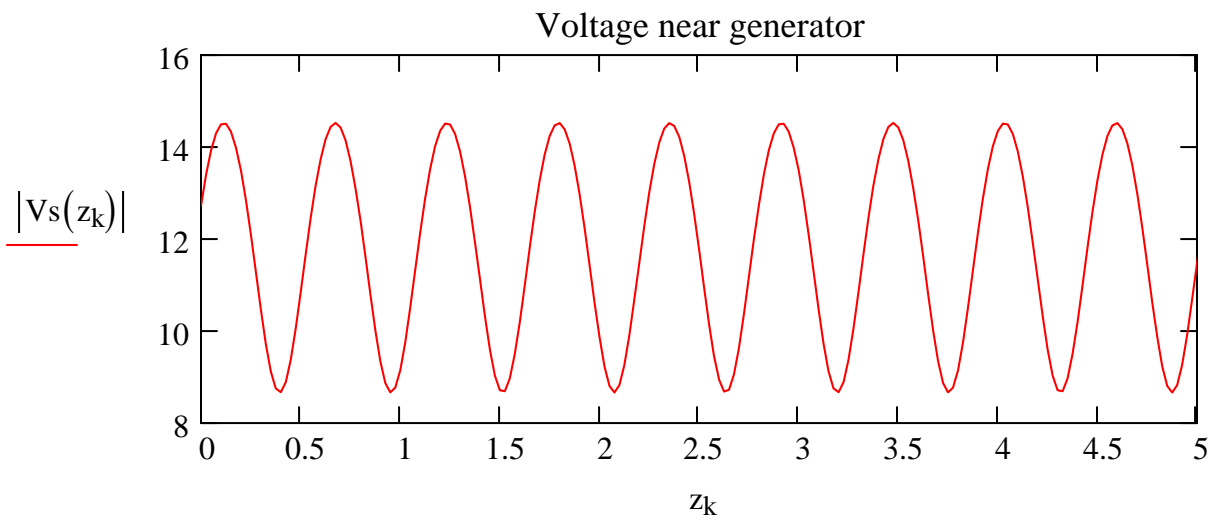
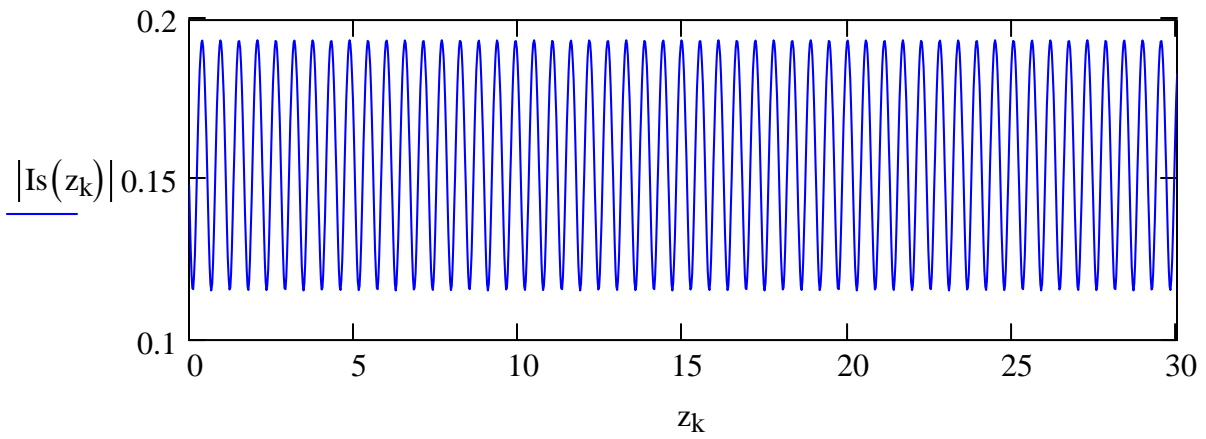
Ex. cont.

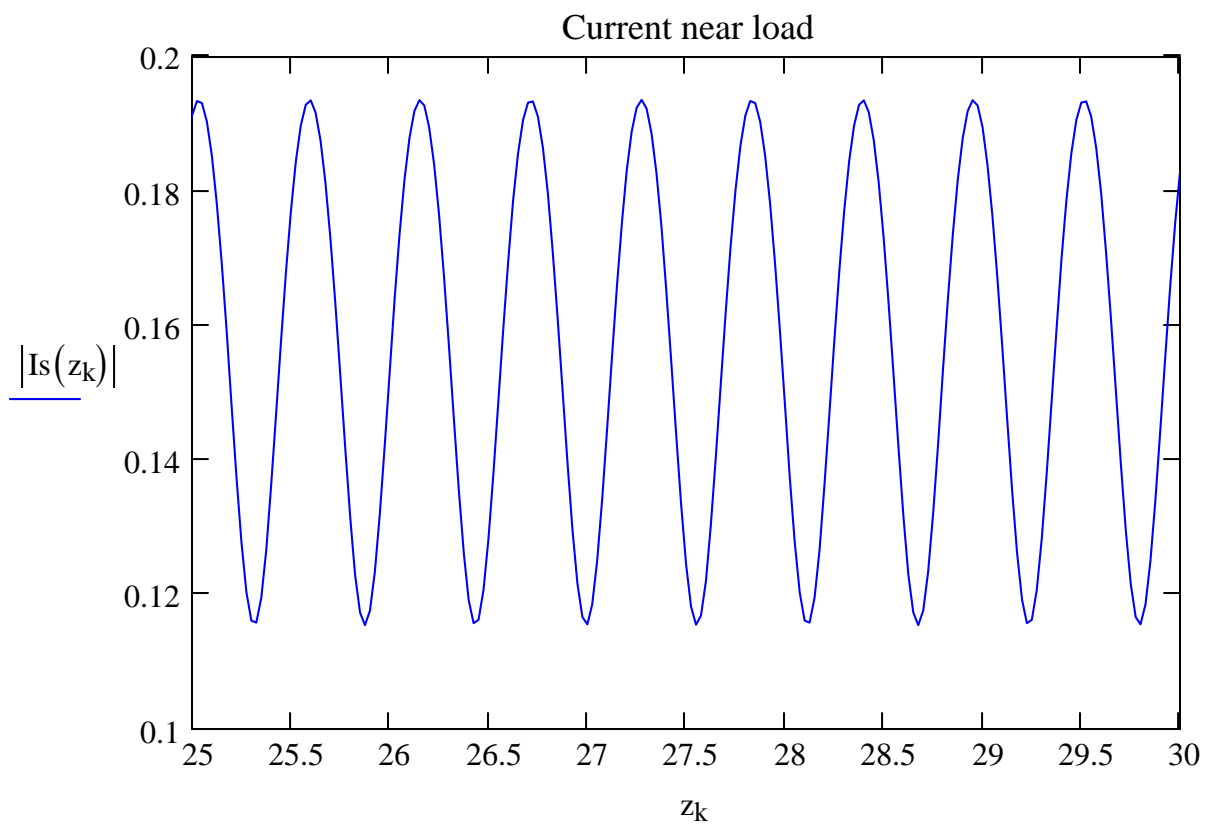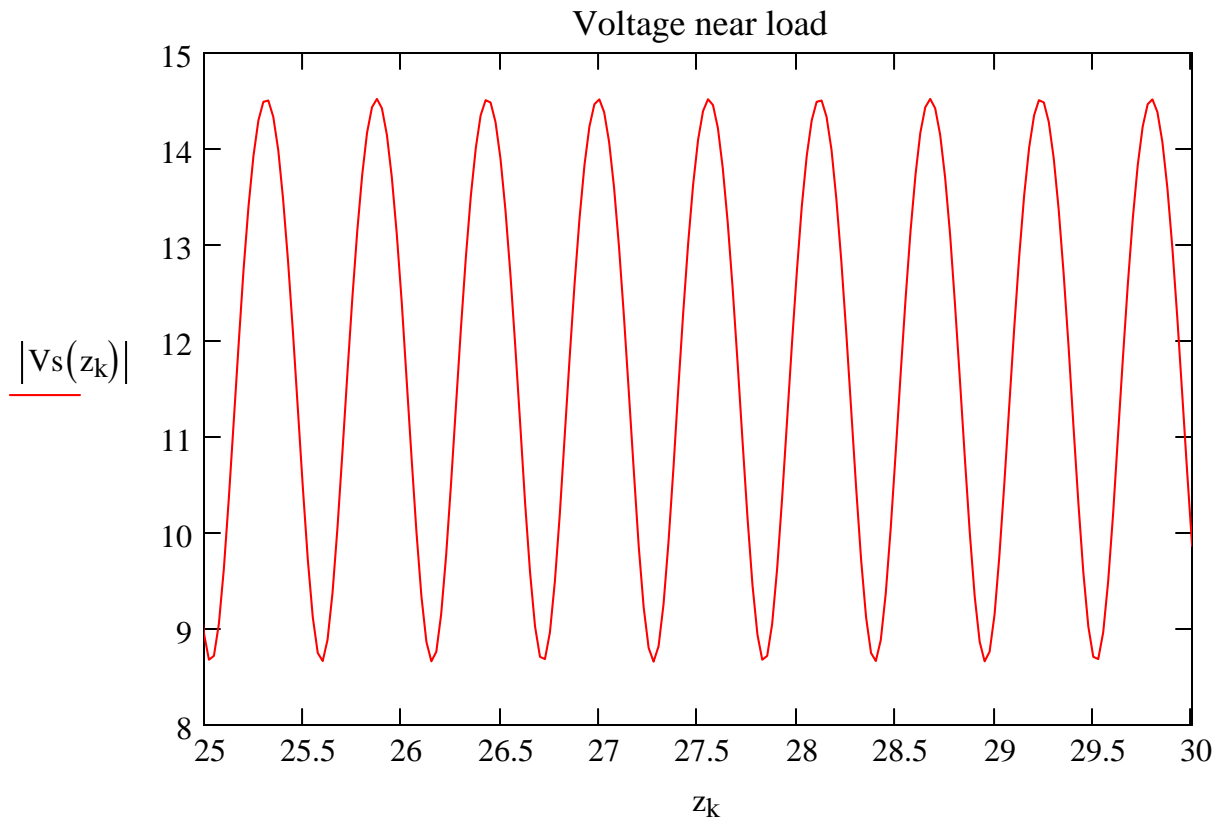Ex. cont.

Ex. cont.**Plot the input impedance as a function of position near the generator**

$$Z_{in_k} := Z_0 \cdot \left(\frac{1 + \Gamma(z_k)}{1 - \Gamma(z_k)} \right) \quad R_{in_k} := \text{Re}(Z_{in_k}) \quad X_{in_k} := \text{Im}(Z_{in_k})$$

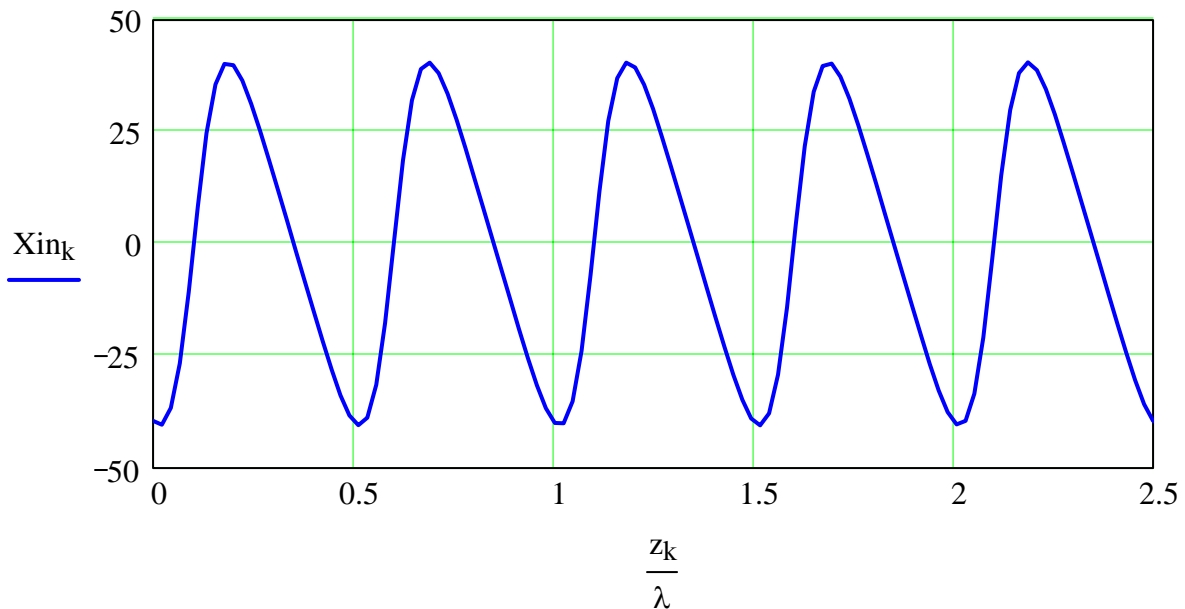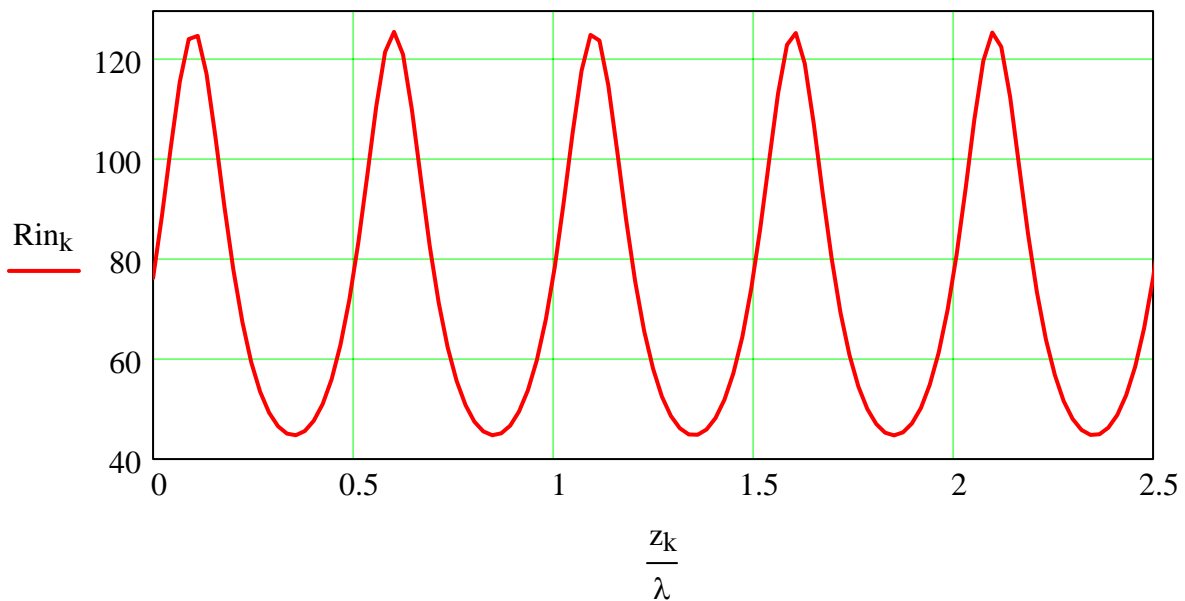Remember Z_{in} is complex, separate the real & imaginary parts for plotting.



Everything repeats at $\lambda/2$ intervals!