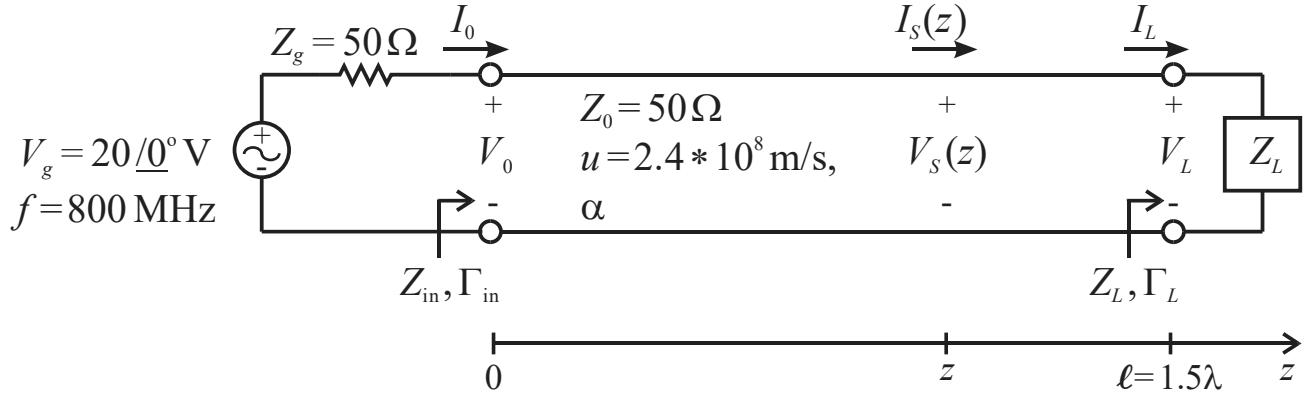


Lossy & Lossless transmission line (TL) standing wave examples

For the TL circuit shown below, we will study the current & voltage standing waves for both the lossless ($\alpha = 0$) and lossy ($\alpha = 0.4 \text{ Np/m}$) cases for loads Z_L : $Z_{sc} = 0$ (short circuit), $Z_{oc} = \infty$ (open circuit), $Z_{gen} = 30 + j50 \Omega$ (general), and $Z_m = Z_0 = 50 \Omega$ (matched). As is often done in TL datasheets, the characteristic impedance has been rounded off to a real number.



Given values

$$V_g := 20 \cdot e^{j \cdot 0} \text{ V} \quad Z_g := 50 \Omega \quad f := 800 \cdot 10^6 \text{ Hz}$$

$$Z_0 := 50 \Omega \quad u := 2.4 \cdot 10^8 \text{ m/s} \quad \alpha := 0.4 \text{ Np/m} \quad L\lambda := 1.5$$

$$Z_{sc} := 0 \Omega \quad Z_{oc} := 10^{99} \Omega \quad Z_{gen} := 30 + j \cdot 50 \Omega \quad Z_m := Z_0$$

General quantities (load independent)

$$\omega := 2 \cdot \pi \cdot f \quad \omega = 5.027 \times 10^9 \text{ rad/s} \quad \lambda := \frac{u}{f} \quad \lambda = 0.3 \text{ m}$$

$$L := L\lambda \cdot \lambda \quad L = 0.45 \text{ m}$$

$$\beta := \frac{\omega}{u} \quad \beta = 20.944 \text{ rad/m} \quad (\text{used by itself for lossless cases})$$

$$\gamma := \alpha + j \cdot \beta \quad \gamma = 0.4 + 20.944i \text{ 1/m} \quad (\text{used for lossy cases})$$

$$n := 0 .. 150 \quad z_n := \frac{n}{150} \cdot L \quad \text{define locations along the TL}$$

Short circuit load, Lossless TL ($\alpha = 0$)

$$\Gamma_{LSc} := \frac{Z_{Sc} - Z_0}{Z_{Sc} + Z_0}$$

$$\boxed{\Gamma_{LSc} = -1}$$

$$\boxed{SWR_{Sc} = \infty}$$

$$\Gamma_{InsClL} := \Gamma_{LSc} \cdot e^{-j \cdot 2 \cdot \beta \cdot L}$$

$$Z_{InsClL} := Z_0 \cdot \frac{1 + \Gamma_{InsClL}}{1 - \Gamma_{InsClL}}$$



$$V_{0sClL} := V_g \cdot \frac{Z_{InsClL}}{Z_g + Z_{InsClL}}$$

$$I_{0sClL} := \frac{V_g}{Z_g + Z_{InsClL}}$$

$$V_{0p_sClL} := 0.5 \cdot (V_{0sClL} + Z_0 \cdot I_{0sClL}) \quad V_{0m_sClL} := V_{0sClL} - V_{0p_sClL}$$

$$V_{s_sClL_n} := V_{0p_sClL} \cdot e^{-j \cdot \beta \cdot z_n} + V_{0m_sClL} \cdot e^{j \cdot \beta \cdot z_n}$$
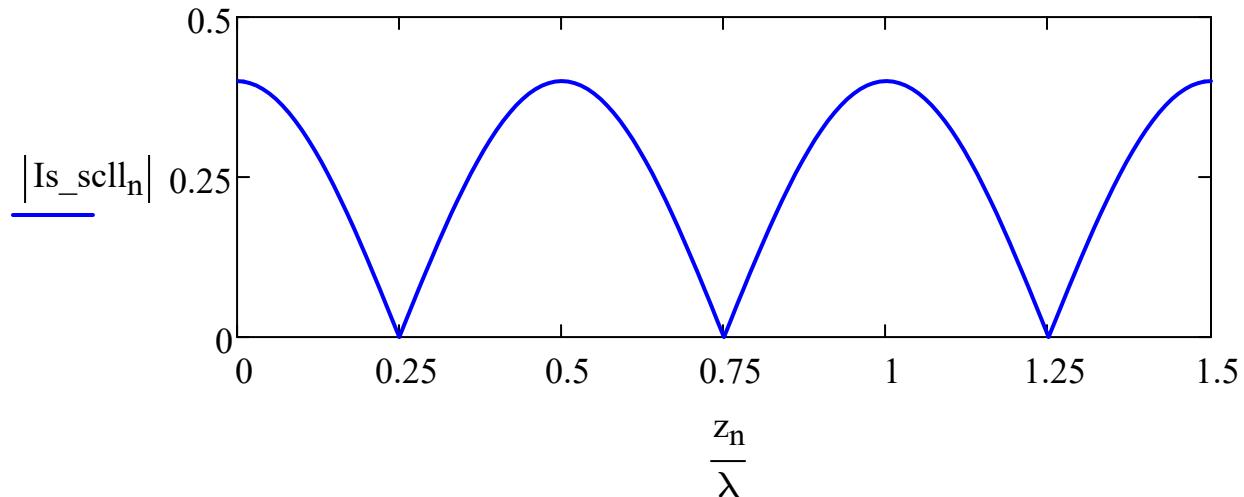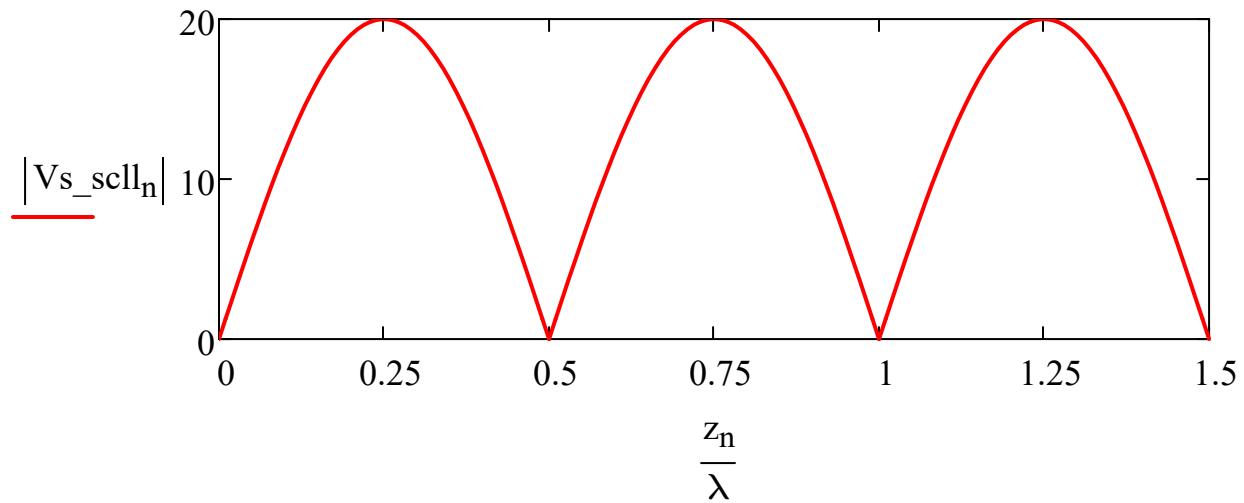
$$I_{s_sClL_n} := \frac{V_{0p_sClL}}{Z_0} \cdot e^{-j \cdot \beta \cdot z_n} - \frac{V_{0m_sClL}}{Z_0} \cdot e^{j \cdot \beta \cdot z_n}$$



Note, the current & voltage standing waves repeat at $\lambda/2$ intervals!

Short circuit load, Lossy TL

$$\Gamma_{\text{insc}} := \Gamma_{\text{Lsc}} \cdot e^{-2 \cdot \gamma \cdot L}$$

$$Z_{\text{insc}} := Z_0 \cdot \frac{1 + \Gamma_{\text{insc}}}{1 - \Gamma_{\text{insc}}}$$

$$V_{0\text{sc}} := V_g \cdot \frac{Z_{\text{insc}}}{Z_g + Z_{\text{insc}}}$$



$$I_{0\text{sc}} := \frac{V_g}{Z_g + Z_{\text{insc}}}$$

$$V_{0p\text{ sc}} := 0.5 \cdot (V_{0\text{sc}} + Z_0 \cdot I_{0\text{sc}})$$

$$V_{0m\text{ sc}} := V_{0\text{sc}} - V_{0p\text{ sc}}$$

$$V_{s\text{ sc}_n} := V_{0p\text{ sc}} \cdot e^{-\gamma \cdot z_n} + V_{0m\text{ sc}} \cdot e^{\gamma \cdot z_n}$$
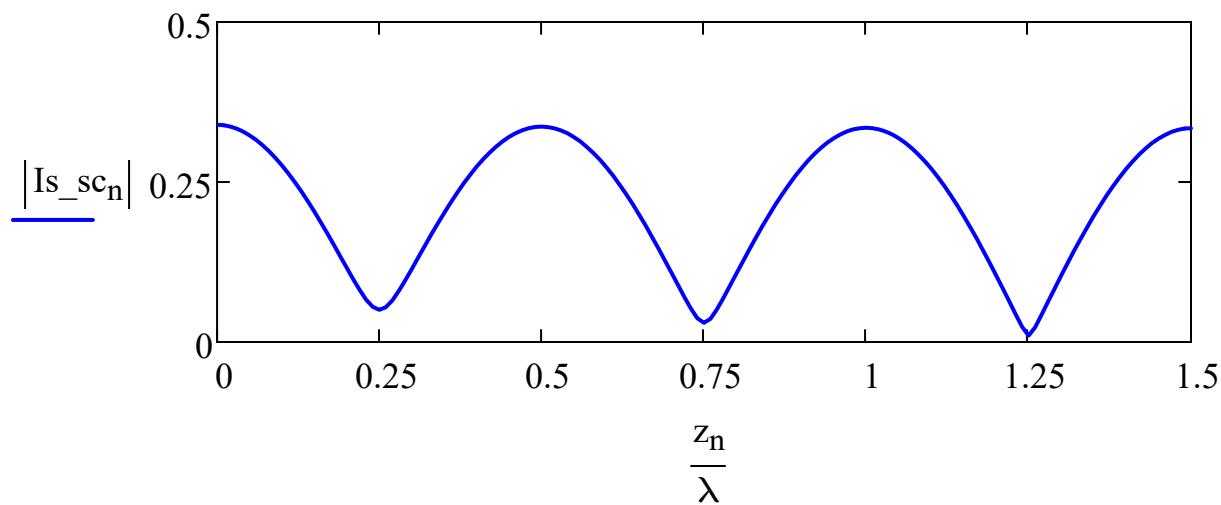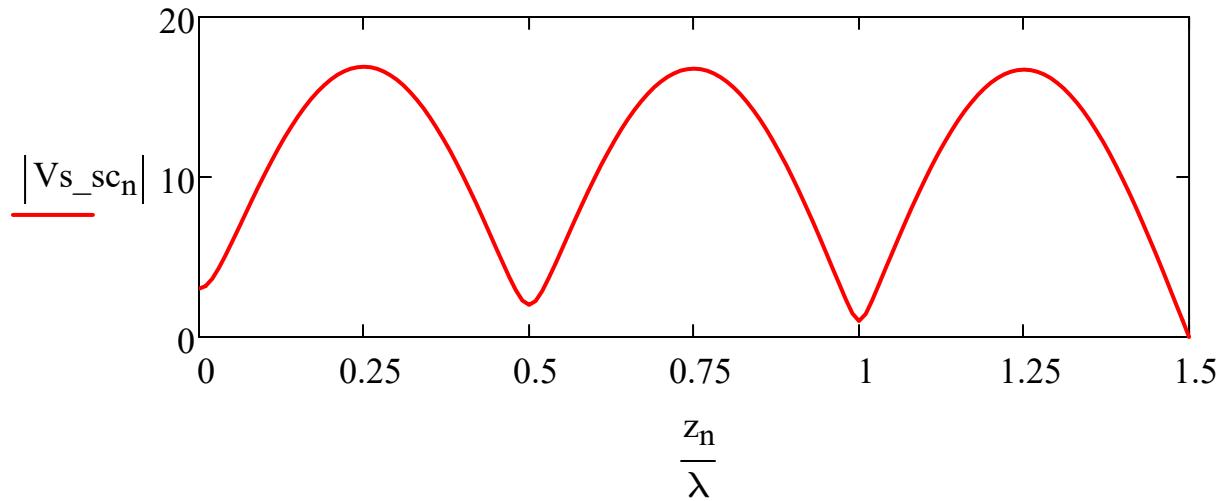
$$I_{s\text{ sc}_n} := \frac{V_{0p\text{ sc}}}{Z_0} \cdot e^{-\gamma \cdot z_n} - \frac{V_{0m\text{ sc}}}{Z_0} \cdot e^{\gamma \cdot z_n}$$



Note how the standing wave minima are NOT zero as you go away from the load on the lossy TL. Max & min occur at $\lambda/2$ intervals.

Open circuit load, Lossless TL ($\alpha = 0$)

$$\Gamma_{Loc} := \frac{Z_{oc} - Z_0}{Z_{oc} + Z_0}$$

$$\boxed{\Gamma_{Loc} = 1}$$

$$\boxed{SWR_{oc} = \infty}$$

$$\Gamma_{inocll} := \Gamma_{Loc} \cdot e^{-j \cdot 2 \cdot \beta \cdot L}$$

$$Z_{inocll} := Z_0 \cdot \frac{1 + \Gamma_{inocll}}{1 - \Gamma_{inocll}}$$

$$V_{0ocll} := V_g \cdot \frac{Z_{inocll}}{Z_g + Z_{inocll}}$$



$$I_{0ocll} := \frac{V_g}{Z_g + Z_{inocll}}$$

$$V_{0p_ocll} := 0.5 \cdot (V_{0ocll} + Z_0 \cdot I_{0ocll})$$

$$V_{0m_ocll} := V_{0ocll} - V_{0p_ocll}$$

$$V_{s_ocll_n} := V_{0p_ocll} \cdot e^{-j \cdot \beta \cdot z_n} + V_{0m_ocll} \cdot e^{j \cdot \beta \cdot z_n}$$
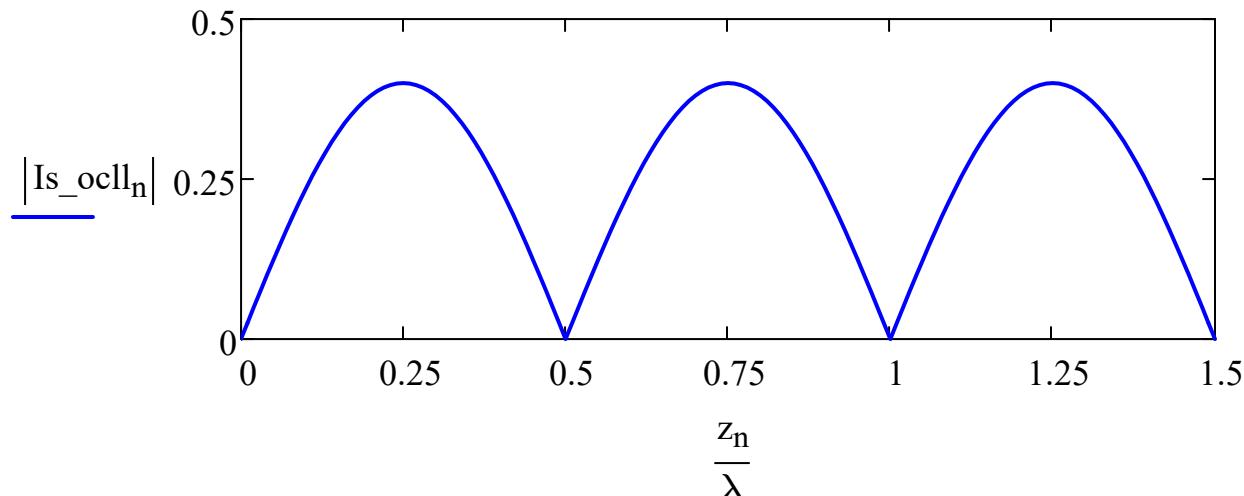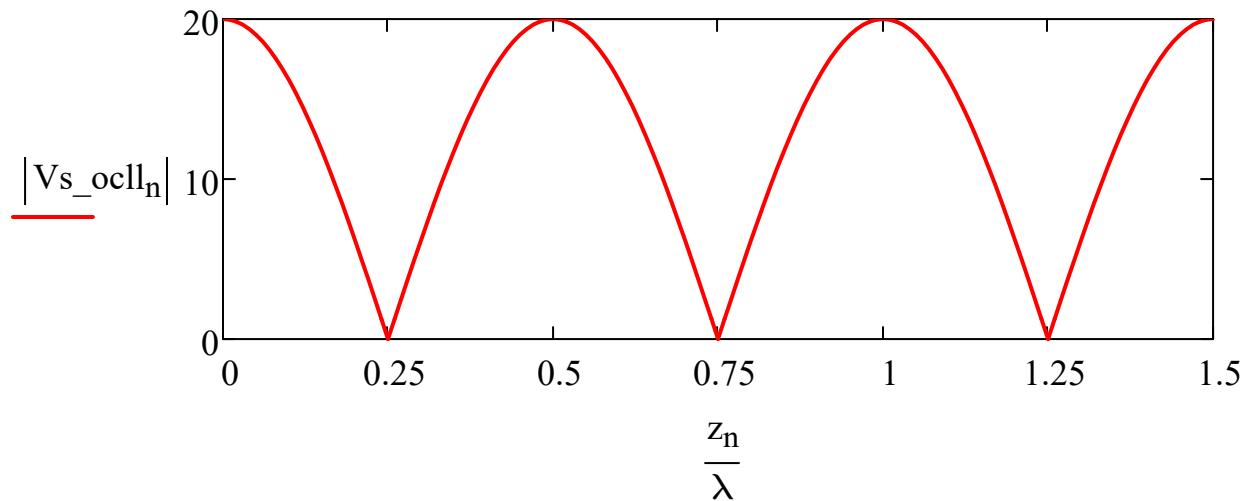
$$I_{s_ocll_n} := \frac{V_{0p_ocll}}{Z_0} \cdot e^{-j \cdot \beta \cdot z_n} - \frac{V_{0m_ocll}}{Z_0} \cdot e^{j \cdot \beta \cdot z_n}$$



Note, the current & voltage standing waves repeat at $\lambda/2$ intervals!

Open circuit load, Lossy TL

$$\Gamma_{inoc} := \Gamma_{Loc} \cdot e^{-2 \cdot \gamma \cdot L}$$

$$Z_{inoc} := Z_0 \cdot \frac{1 + \Gamma_{inoc}}{1 - \Gamma_{inoc}}$$

$$V_{0oc} := V_g \cdot \frac{Z_{inoc}}{Z_g + Z_{inoc}}$$



$$I_{0oc} := \frac{V_g}{Z_g + Z_{inoc}}$$

$$V_{0p_oc} := 0.5 \cdot (V_{0oc} + Z_0 \cdot I_{0oc})$$

$$V_{0m_oc} := V_{0oc} - V_{0p_oc}$$

$$V_{s_oc_n} := V_{0p_oc} \cdot e^{-\gamma \cdot z_n} + V_{0m_oc} \cdot e^{\gamma \cdot z_n}$$
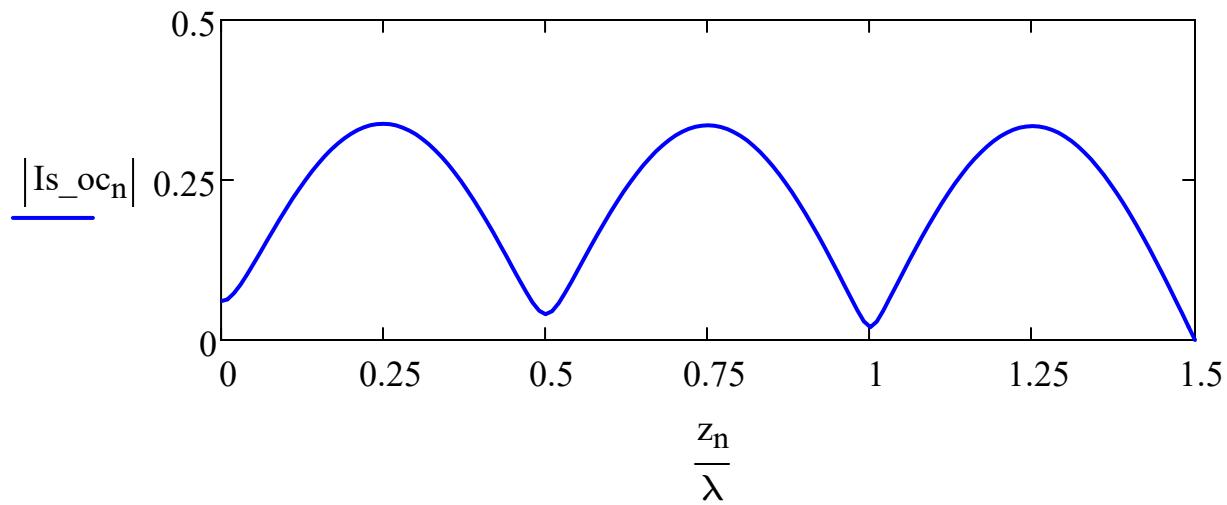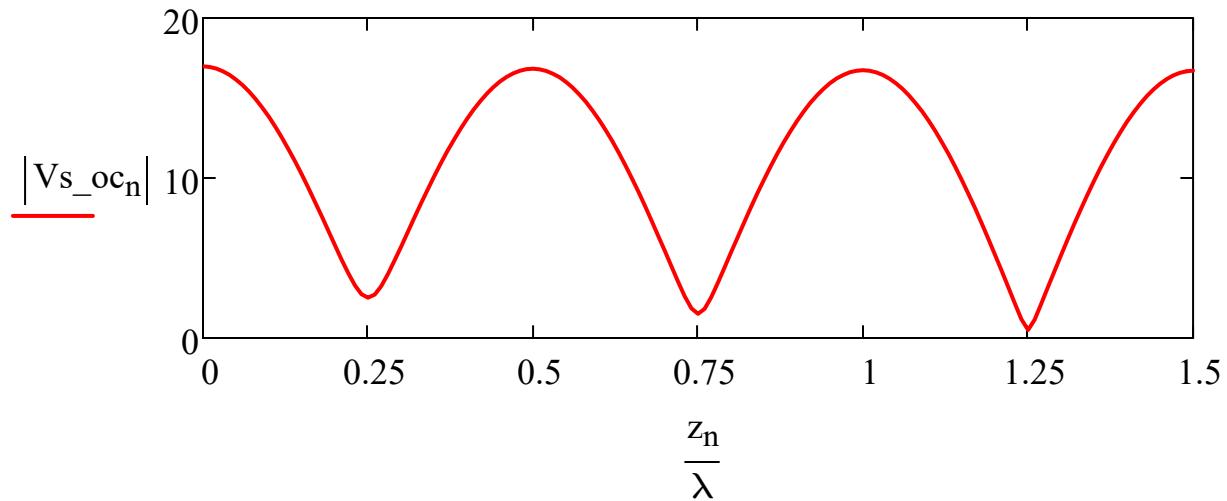
$$I_{s_oc_n} := \frac{V_{0p_oc}}{Z_0} \cdot e^{-\gamma \cdot z_n} - \frac{V_{0m_oc}}{Z_0} \cdot e^{\gamma \cdot z_n}$$



Note how the standing wave minima are NOT zero as you go away from the load on the lossy TL. Max & min occur at $\lambda/2$ intervals.

General load, Lossless TL ($\alpha = 0$)

$$\Gamma_{Lgen} := \frac{Z_{gen} - Z_0}{Z_{gen} + Z_0} \quad |\Gamma_{Lgen}| = 0.571$$

$$S_{gen} := \frac{1 + |\Gamma_{Lgen}|}{1 - |\Gamma_{Lgen}|} \quad S_{gen} = 3.66$$

$$\Gamma_{ingenll} := \Gamma_{Lgen} \cdot e^{-j \cdot 2 \cdot \beta \cdot L}$$

$$Z_{ingenll} := Z_0 \cdot \frac{1 + \Gamma_{ingenll}}{1 - \Gamma_{ingenll}}$$

$$V_{0gll} := V_g \cdot \frac{Z_{ingenll}}{Z_g + Z_{ingenll}}$$



$$I_{0gll} := \frac{V_g}{Z_g + Z_{ingenll}}$$

$$V_{0p_genll} := 0.5 \cdot (V_{0gll} + Z_0 \cdot I_{0gll})$$

$$V_{0m_genll} := V_{0gll} - V_{0p_genll}$$

$$V_{s_genll_n} := V_{0p_genll} \cdot e^{-j \cdot \beta \cdot z_n} + V_{0m_genll} \cdot e^{j \cdot \beta \cdot z_n}$$
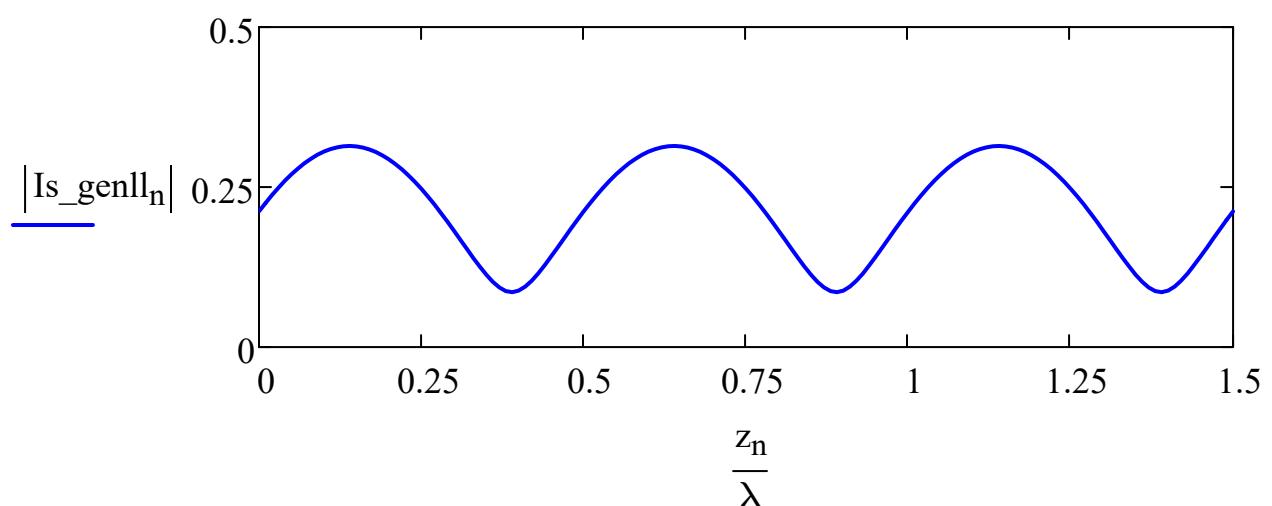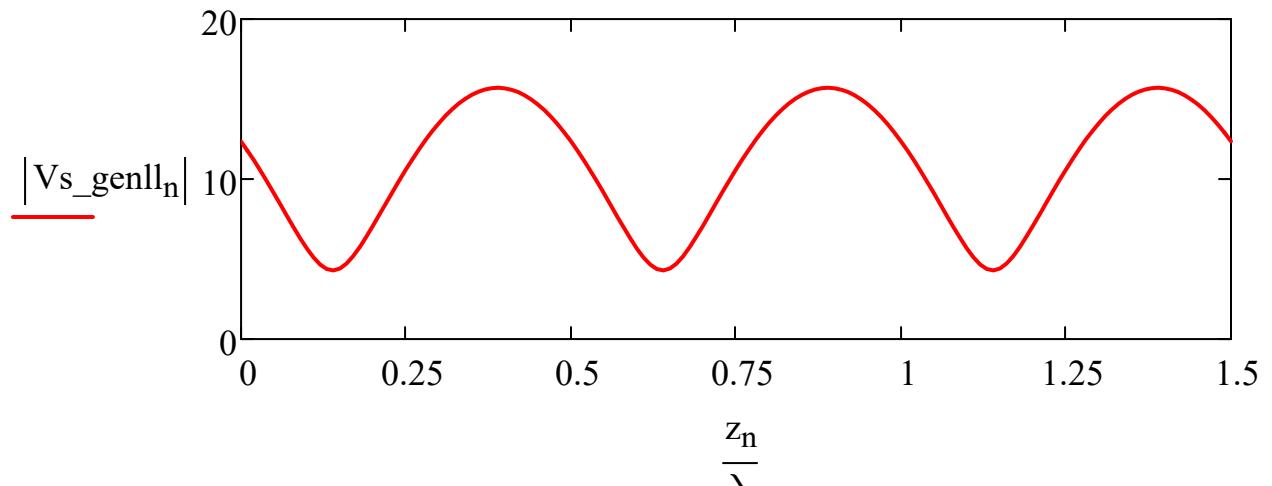
$$I_{s_genll_n} := \frac{V_{0p_genll}}{Z_0} \cdot e^{-j \cdot \beta \cdot z_n} - \frac{V_{0m_genll}}{Z_0} \cdot e^{j \cdot \beta \cdot z_n}$$



General load, Lossy TL

$$\Gamma_{\text{ingen}} := \Gamma L_{\text{gen}} \cdot e^{-2 \cdot \gamma \cdot L}$$

$$Z_{\text{ingen}} := Z_0 \cdot \frac{1 + \Gamma_{\text{ingen}}}{1 - \Gamma_{\text{ingen}}}$$



$$V_{0\text{gen}} := V_g \cdot \frac{Z_{\text{ingen}}}{Z_g + Z_{\text{ingen}}}$$

$$I_{0\text{gen}} := \frac{V_g}{Z_g + Z_{\text{ingen}}}$$

$$V_{0p\text{gen}} := 0.5 \cdot (V_{0\text{gen}} + Z_0 \cdot I_{0\text{gen}}) \quad V_{0m\text{gen}} := V_{0\text{gen}} - V_{0p\text{gen}}$$

$$V_{s\text{gen}_n} := V_{0p\text{gen}} \cdot e^{-\gamma \cdot z_n} + V_{0m\text{gen}} \cdot e^{\gamma \cdot z_n}$$
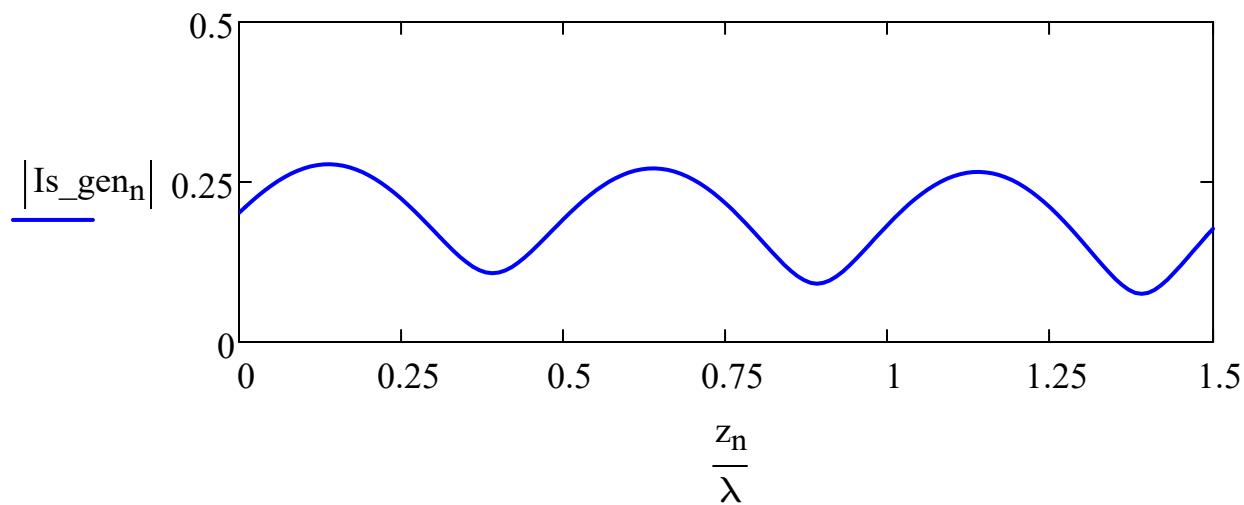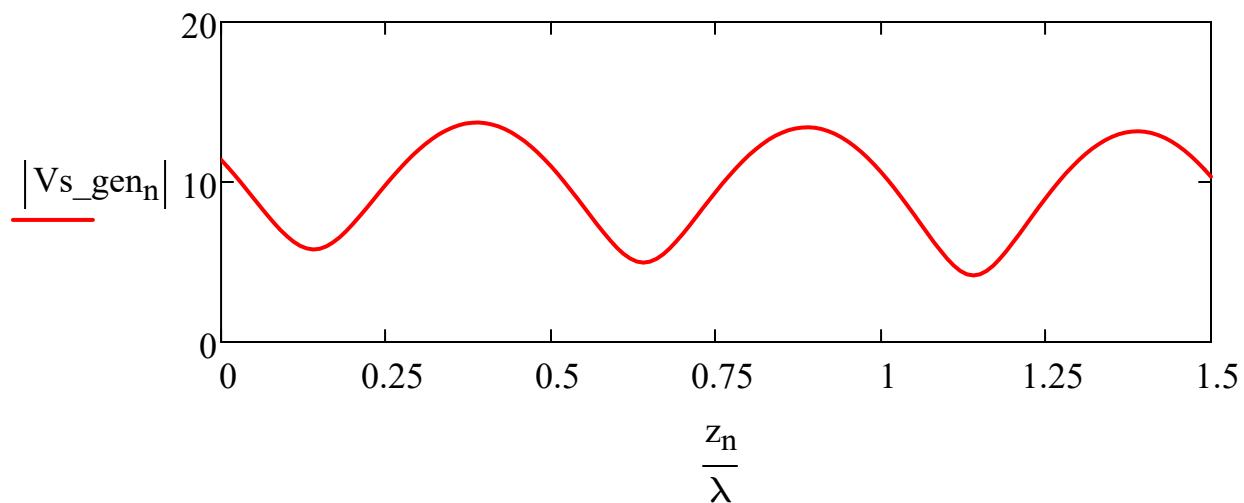
$$I_{s\text{gen}_n} := \frac{V_{0p\text{gen}}}{Z_0} \cdot e^{-\gamma \cdot z_n} - \frac{V_{0m\text{gen}}}{Z_0} \cdot e^{\gamma \cdot z_n}$$



Note how the standing wave changes as you go away from the load on the lossy TL. Max & min occur at $\lambda/2$ intervals.

Matched load, Lossless TL ($\alpha = 0$)

$$\Gamma_{Lm} := \frac{Z_m - Z_0}{Z_m + Z_0} \quad |\Gamma_{Lm}| = 0 \quad \text{No reflected/backward traveling waves means - NO standing waves!}$$

$$S_m := \frac{1 + |\Gamma_{Lm}|}{1 - |\Gamma_{Lm}|} \quad S_m = 1$$



$$\Gamma_{inmll} := \Gamma_{Lm} \cdot e^{-j \cdot 2 \cdot \beta \cdot L} \quad Z_{inmll} := Z_0 \cdot \frac{1 + \Gamma_{inmll}}{1 - \Gamma_{inmll}}$$

$$V_{0mll} := V_g \cdot \frac{Z_{inmll}}{Z_g + Z_{inmll}} \quad I_{0mll} := \frac{V_g}{Z_g + Z_{inmll}}$$

$$V_{0p_mll} := 0.5 \cdot (V_{0mll} + Z_0 \cdot I_{0mll}) \quad V_{0m_mll} := V_{0mll} - V_{0p_mll}$$

$$V_{s_mll_n} := V_{0p_mll} \cdot e^{-j \cdot \beta \cdot z_n} + V_{0m_mll} \cdot e^{j \cdot \beta \cdot z_n}$$
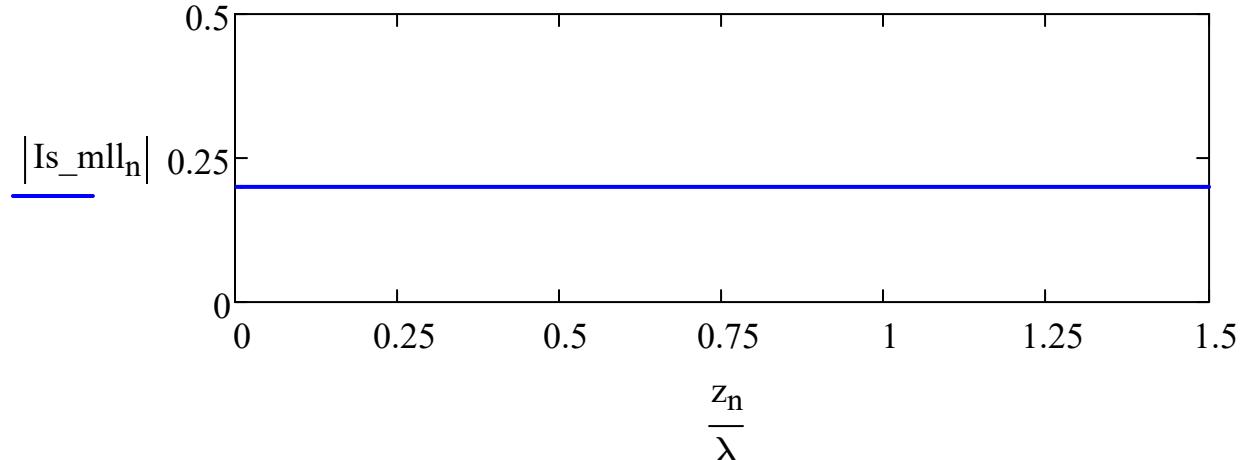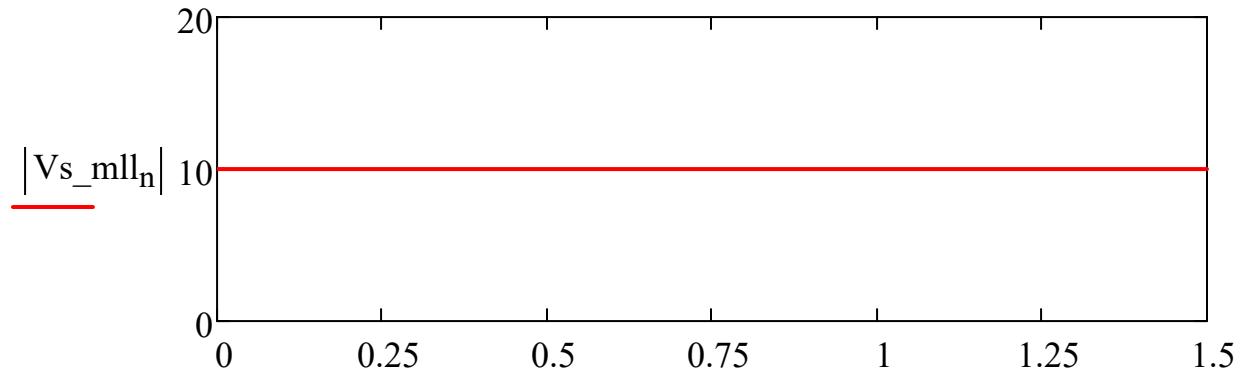
$$I_{s_mll_n} := \frac{V_{0p_mll}}{Z_0} \cdot e^{-j \cdot \beta \cdot z_n} - \frac{V_{0m_mll}}{Z_0} \cdot e^{j \cdot \beta \cdot z_n}$$



Matched load, Lossy TL

$$\Gamma_{inm} := \Gamma_{Lm} \cdot e^{-2 \cdot \gamma \cdot L}$$

$$Z_{inm} := Z_0 \cdot \frac{1 + \Gamma_{inm}}{1 - \Gamma_{inm}}$$

$$V_{0m} := V_g \cdot \frac{Z_{inm}}{Z_g + Z_{inm}}$$



$$I_{0m} := \frac{V_g}{Z_g + Z_{inm}}$$

$$V_{0p_m} := 0.5 \cdot (V_{0m} + Z_0 \cdot I_{0m})$$

$$V_{0m_m} := V_{0m} - V_{0p_m}$$

$$V_{s_m_n} := V_{0p_m} \cdot e^{-\gamma \cdot z_n} + V_{0m_m} \cdot e^{\gamma \cdot z_n}$$
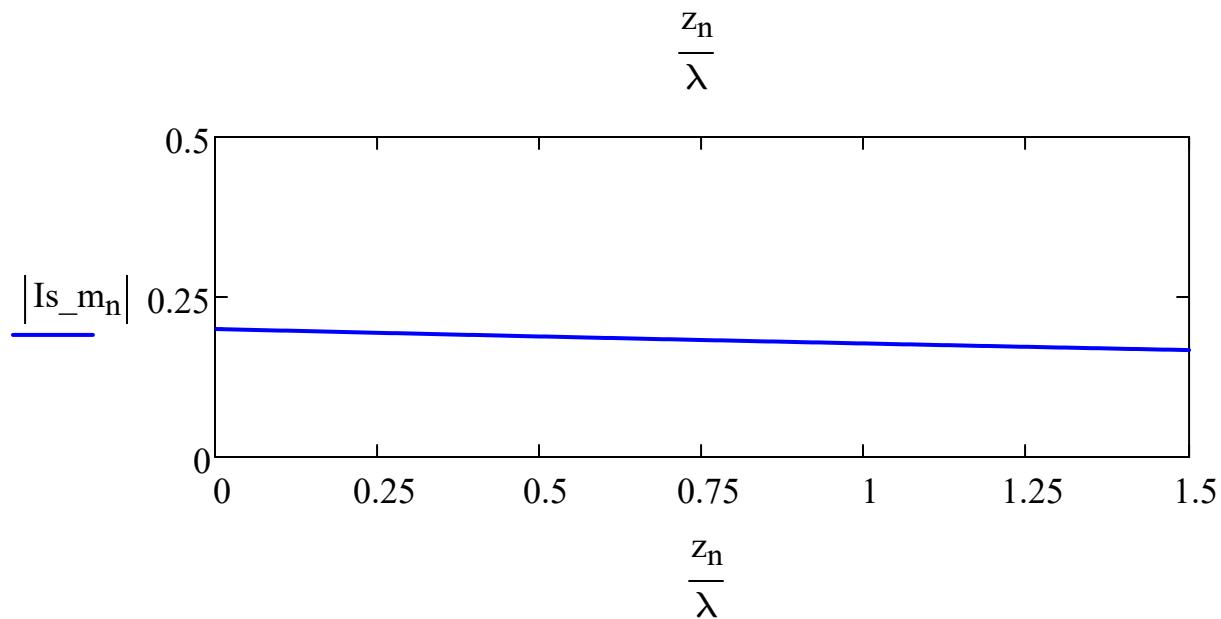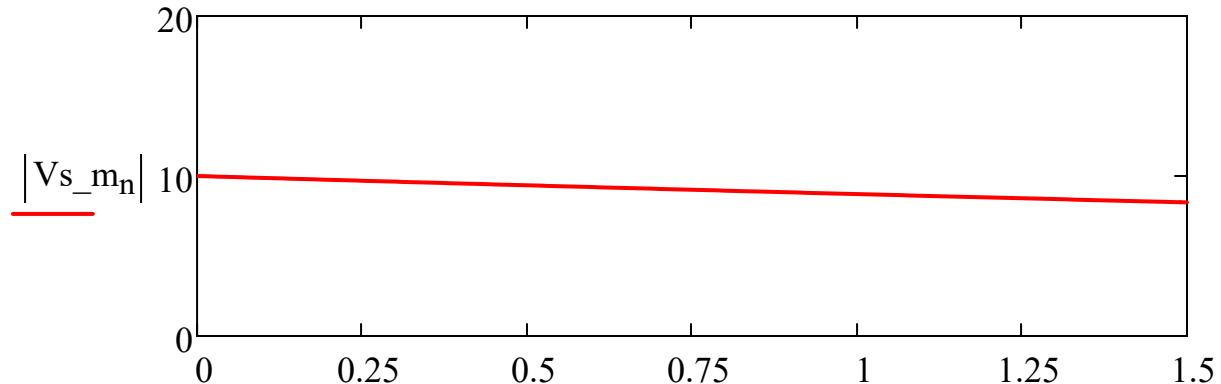
$$I_{s_m_n} := \frac{V_{0p_m}}{Z_0} \cdot e^{-\gamma \cdot z_n} - \frac{V_{0m_m}}{Z_0} \cdot e^{\gamma \cdot z_n}$$



NO standing waves! However, note the forward propagating waves decay as you go from the source toward the load on lossy TL.