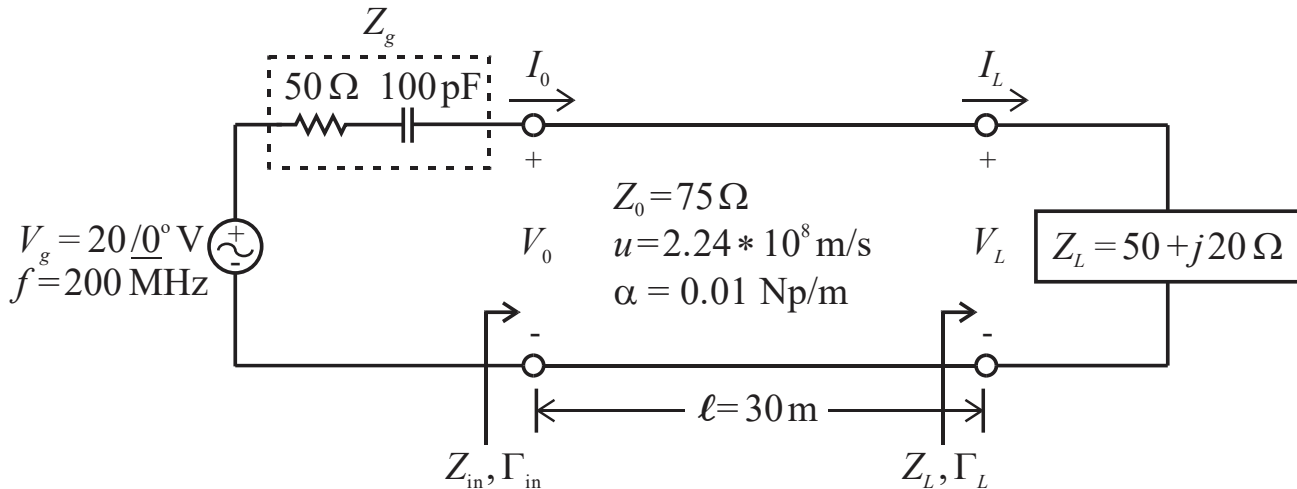


EE 381 Lossy Transmission Line example with power

For the circuit shown below, calculate the standing wave ratio as well as input & load currents, voltages, powers, reflection coefficients, and impedances. Also, plot the magnitude of the current and voltage as a function of position near generator.



Enter given information

$$Z_L := 50 + j \cdot 20 \quad \Omega$$

$$V_g := 20 \cdot e^{j \cdot 0 \cdot \frac{\pi}{180}} \text{ V} \quad f := 200 \cdot 10^6 \text{ Hz} \quad R_g := 50 \quad \Omega \quad C_g := 100 \cdot 10^{-12} \text{ F}$$

$$\underline{L} := 30 \text{ m} \quad u := 2.24 \cdot 10^8 \text{ m/s} \quad Z_0 := 75 \quad \Omega \quad \alpha := 0.01 \text{ Np/m}$$

Calculate variables related to generator and transmission line

$$\omega := 2 \cdot \pi \cdot f \quad \omega = 1.257 \times 10^9 \text{ rad/s} \quad \beta := \frac{\omega}{u} \quad \beta = 5.61 \text{ rad/m} \quad \gamma := \alpha + j \cdot \beta$$

$$Z_g := R_g - \frac{j}{2 \cdot \pi \cdot f \cdot C_g} \quad Z_g = 50 - 7.9577i \quad \Omega \quad \lambda := \frac{u}{f} \quad \lambda = 1.12 \text{ m}$$

Calculate reflection coefficients and SWR


$$\Gamma_L := \frac{Z_L - Z_0}{Z_L + Z_0} \quad |\Gamma_L| = 0.2529 \quad \arg(\Gamma_L) \cdot \frac{180}{\pi} = 132.25 \text{ deg}$$

$$\Gamma_{in} := \Gamma_L \cdot e^{-2 \cdot \gamma \cdot L} \quad |\Gamma_{in}| = 0.1388 \quad \arg(\Gamma_{in}) \cdot \frac{180}{\pi} = -73.464 \text{ deg}$$

$$\text{SWR} := \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} \quad \text{SWR} = 1.677$$

Calculate input impedance

$$Z_{in} := Z_0 \cdot \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} \quad \boxed{Z_{in} = 78.2287 - 21.2269i} \quad \Omega$$

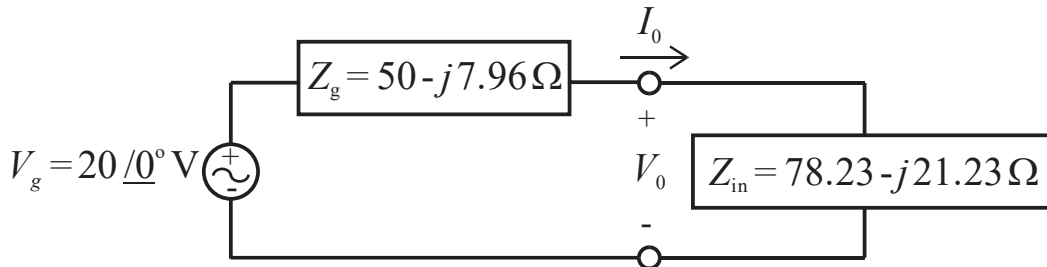Calculate input current, voltage, and power using equivalent circuit

$$I_0 := \frac{V_g}{Z_g + Z_{in}} \quad \boxed{|I_0| = 0.1521} \text{ A} \quad \boxed{\arg(I_0) \cdot \frac{180}{\pi} = 12.822} \text{ deg}$$

$$V_0 := V_g \cdot \frac{Z_{in}}{Z_g + Z_{in}} \quad \boxed{|V_0| = 12.3274} \text{ V} \quad \boxed{\arg(V_0) \cdot \frac{180}{\pi} = -2.359} \text{ deg}$$

$$P_{ave_in} := 0.5 \cdot \text{Re}(V_0 \cdot \bar{I}_0) \quad \boxed{P_{ave_in} = 0.9047} \text{ W}$$

Calculate phasor forward traveling voltage wave amplitude V_0^+

$$V_{fwd} := \frac{V_0}{1 + \Gamma_{in}} \quad |V_{fwd}| = 11.7629 \text{ V} \quad \arg(V_{fwd}) \cdot \frac{180}{\pi} = 4.935 \text{ deg}$$

Define reflection coefficient, phasor current & voltage in terms of position

$$\Gamma(z) := \Gamma_L \cdot e^{-2 \cdot \gamma \cdot (L-z)}$$

$$I_s(z) := \frac{V_{fwd}}{Z_0} \cdot e^{-\gamma \cdot z} \cdot (1 - \Gamma(z)) \quad V_s(z) := V_{fwd} \cdot e^{-\gamma \cdot z} \cdot (1 + \Gamma(z))$$

Calculate the load current, voltage, and power




$$I_L := I_s(L) \quad \boxed{|I_L| = 0.13768} \text{ A} \quad \boxed{\arg(I_L) \cdot \frac{180}{\pi} = 72.988} \text{ deg}$$

$$V_L := V_s(L) \quad \boxed{|V_L| = 7.4141} \text{ V} \quad \boxed{\arg(V_L) \cdot \frac{180}{\pi} = 94.789} \text{ deg}$$

$$P_{ave_L} := 0.5 \cdot \text{Re}(V_L \cdot \bar{I}_L) \quad \boxed{P_{ave_L} = 0.4739} \text{ W} \quad \text{Smaller than input power!}$$

Plot magnitude of current & voltage and power as functions of position

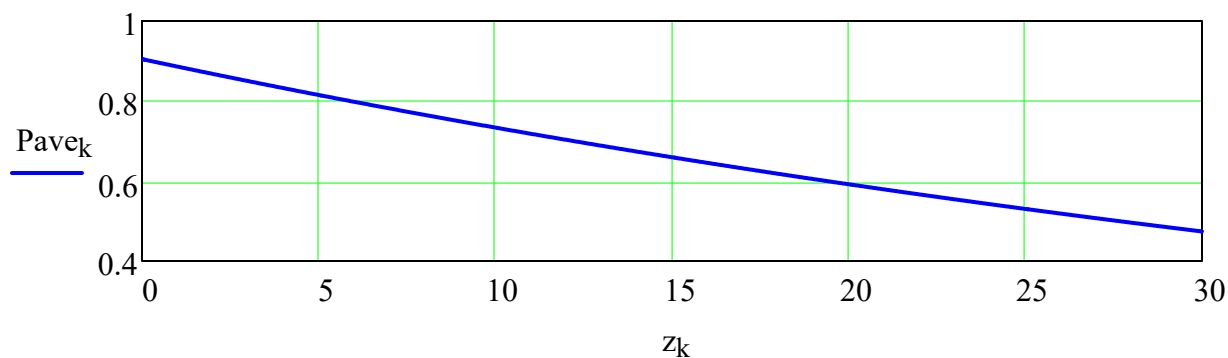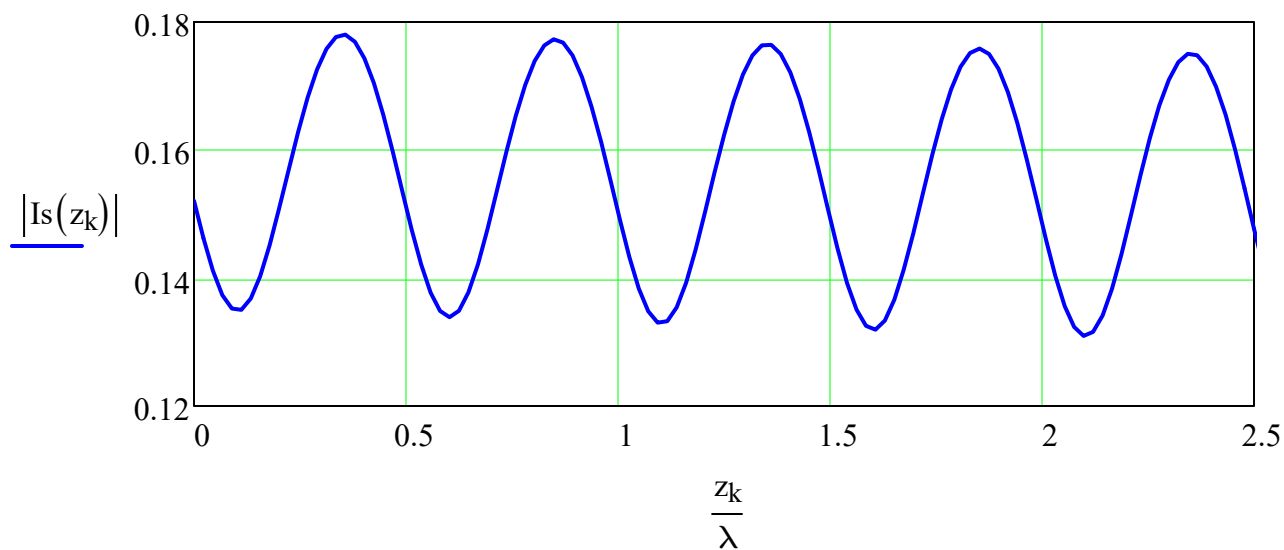
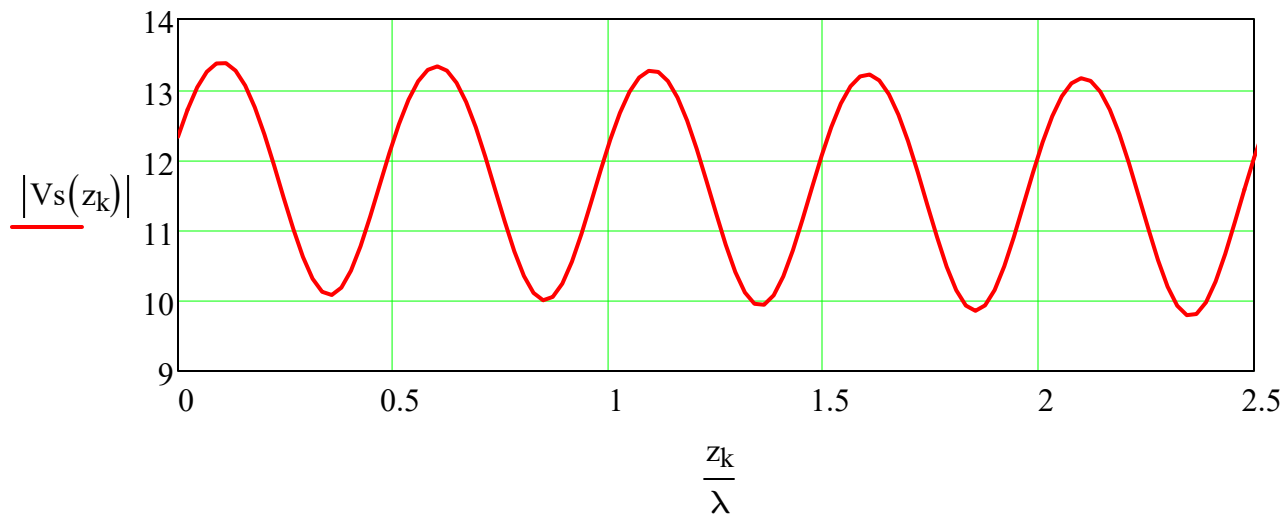
$$k := 0..1200 \quad z_k := \frac{k}{1200} \cdot L \quad \text{Pave}_k := 0.5 \cdot \text{Re}\left(V_s(z_k) \cdot \overline{I_s(z_k)}\right)$$



Plot the input impedance as a function of position near the generator

$$\underline{Z}_{in_k} := Z_0 \cdot \left(\frac{1 + \Gamma(z_k)}{1 - \Gamma(z_k)} \right) \quad R_{in_k} := \text{Re}(Z_{in_k}) \quad X_{in_k} := \text{Im}(Z_{in_k})$$

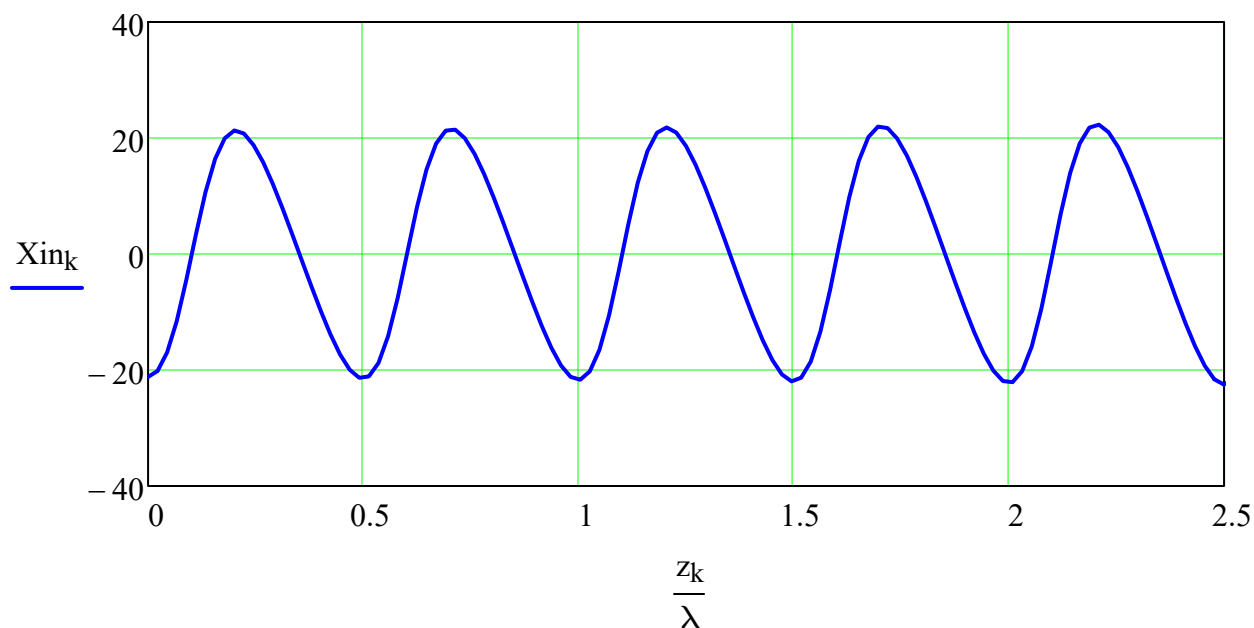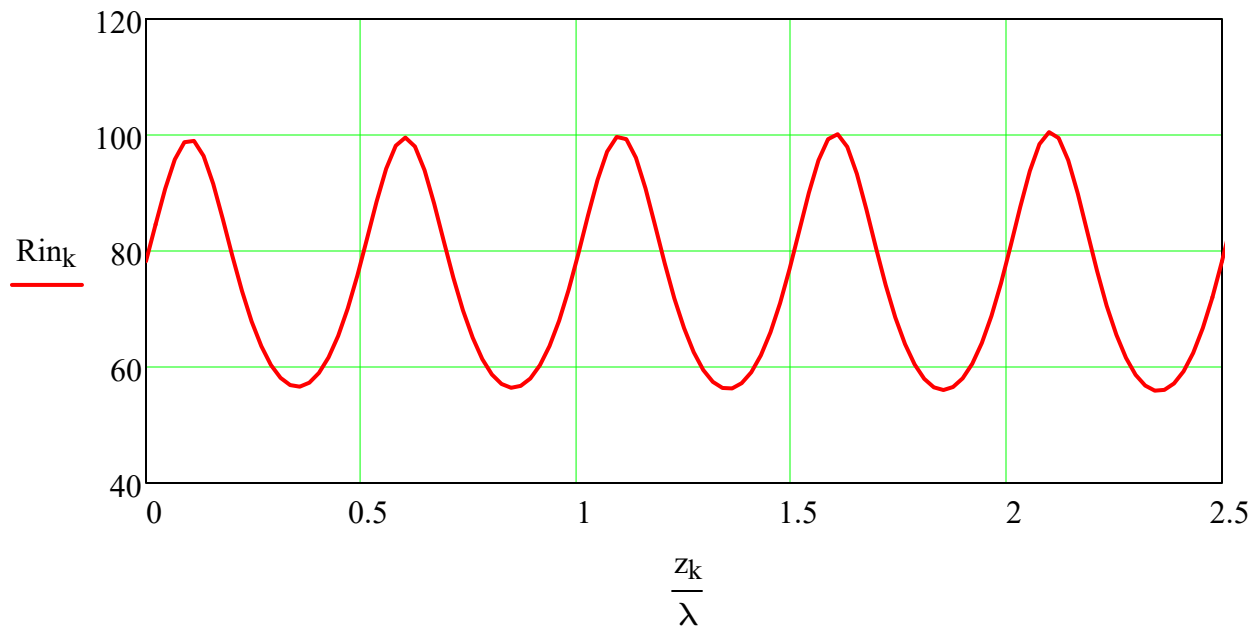Remember Z_{in} is complex, separate the real & imaginary parts for plotting.



Everything nearly repeats at $\lambda/2$ intervals on this low loss TL!