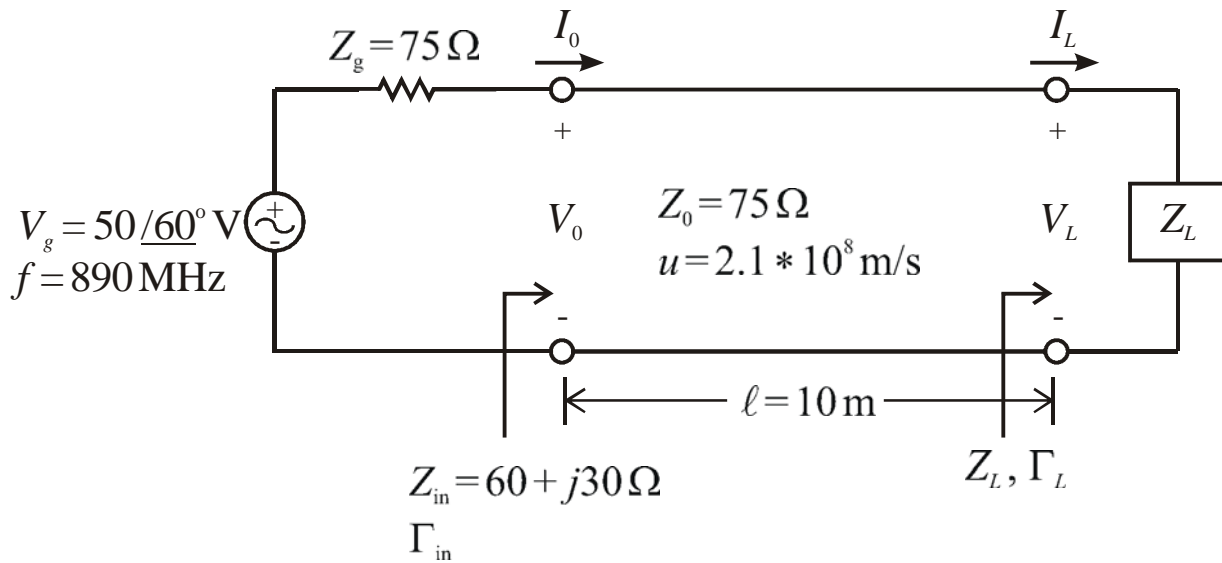


EE381 Lossless Transmission Line example 2



For the lossless transmission line circuit shown, calculate quantities of interest, especially at the input and load ends of the transmission line.

Given:

$$V_g := 50 \cdot e^{j \cdot 60 \cdot \frac{\pi}{180}} \text{ V} \quad f := 890 \cdot 10^6 \text{ Hz} \quad Z_g := 75 \quad \Omega$$

$$Z_{in} := 60 + j \cdot 30 \quad \Omega \quad Z_0 := 75 \quad \Omega \quad L := 10.0 \text{ m} \quad u := 2.1 \cdot 10^8 \text{ m/s}$$

$$\Gamma_0 := \frac{Z_{in} - Z_0}{Z_{in} + Z_0} \quad \boxed{|\Gamma_0| = 0.2425} \quad \boxed{\arg(\Gamma_0) \cdot \frac{180}{\pi} = 104.036} \text{ deg}$$

$$\beta := \frac{2 \cdot \pi \cdot f}{u} \quad \beta = 26.629 \text{ rad/m} \quad \lambda := \frac{u}{f} \quad \lambda = 0.23596 \text{ m}$$


$$\beta L := \beta \cdot L \quad \beta L = 266.287 \text{ rad} \quad \beta L \cdot \frac{180}{\pi} = 15257 \text{ deg} \quad \frac{\beta L}{2 \cdot \pi} = 42.381 \lambda$$

$$\Gamma_L := \Gamma_0 \cdot e^{j \cdot 2 \cdot \beta \cdot L} \quad \boxed{|\Gamma_L| = 0.2425} \quad \boxed{\arg(\Gamma_L) \cdot \frac{180}{\pi} = 18.322} \text{ deg}$$

$$Z_L := Z_0 \cdot \frac{(1 + \Gamma_L)}{1 - \Gamma_L} \quad \boxed{Z_L = 117.973 + 19.113i} \quad \Omega$$

EE381 Lossless Transmission Line example 2 cont.

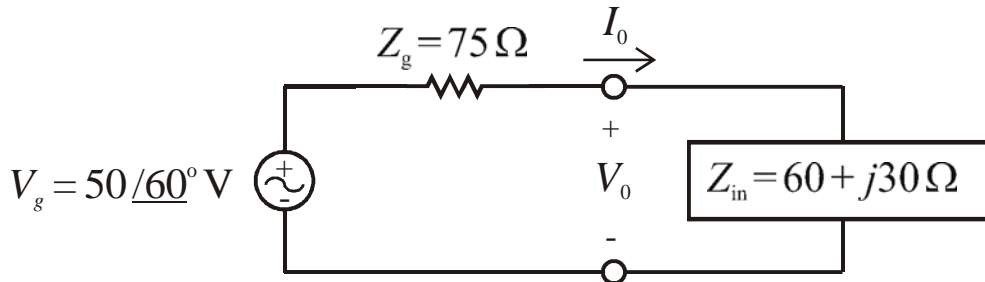Draw equivalent circuit at input of the lossless transmission line.



$$V_0 := V_g \cdot \frac{Z_{in}}{Z_g + Z_{in}} \quad |V_0| = 24.25356 \text{ V} \quad \arg(V_0) \cdot \frac{180}{\pi} = 74.036 \text{ deg}$$

$$I_0 := \frac{V_g}{Z_g + Z_{in}} \quad |I_0| = 0.36155 \text{ A} \quad \arg(I_0) \cdot \frac{180}{\pi} = 47.471 \text{ deg}$$

$$V_{plus} := \frac{V_0}{1 + \Gamma_0} \quad |V_{plus}| = 25 \text{ V} \quad \arg(V_{plus}) \cdot \frac{180}{\pi} = 60 \text{ deg}$$

$$V_L := V_{plus} \cdot e^{-j\beta \cdot L} \cdot (1 + \Gamma_L) \quad |V_L| = 30.81501 \quad \arg(V_L) \cdot \frac{180}{\pi} = -73.597 \text{ deg}$$

$$I_L := \frac{V_{plus}}{Z_0} \cdot e^{-j\beta \cdot L} \cdot (1 - \Gamma_L) \quad |I_L| = 0.25784 \quad \arg(I_L) \cdot \frac{180}{\pi} = -82.799 \text{ deg}$$

EE381 Lossless Transmission Line example 2 cont.

Let's plot $|V(z)|$ and $|I(z)|$ for values of z near the load $z = L = 10$ m.

$$n := 0..2000 \quad z_n := \frac{n}{2000} \cdot L \quad \Gamma_{z_n} := \Gamma_L \cdot e^{-j \cdot 2 \cdot \beta \cdot (L - z_n)}$$

$$V_{s_n} := V_{\text{plus}} \cdot e^{-j \cdot \beta \cdot z_n} \cdot (1 + \Gamma_{z_n}) \quad I_{s_n} := \frac{V_{\text{plus}}}{Z_0} \cdot e^{-j \cdot \beta \cdot z_n} \cdot (1 - \Gamma_{z_n})$$

