

EE 381 Quiz #1 (Fall 2017)

Name Key A

Instructions: Closed book & notes. Place answers in indicated spaces and show all work for credit.

Useful equations: $u = f\lambda = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$, $LC = \mu\epsilon$, $\beta = \omega\sqrt{LC} = \frac{\omega}{u}$, $\lambda = \frac{u}{f} = \frac{2\pi}{\beta}$, $Z_0 = \frac{V_0^+}{I_0^+} = \sqrt{\frac{L}{C}}$

A lossless 28 cm-long transmission line has a characteristic impedance of 50Ω and velocity of propagation of 2.1×10^8 m/s. Determine the inductance and capacitance per unit length. If operated at 550 MHz, calculate the phase constant, wavelength, and length (in terms of wavelength) of the transmission line.

$$\frac{Z_0}{u} = \frac{\sqrt{L/C}}{1/\sqrt{LC}} = L = \frac{50}{2.1 \times 10^8} = \underline{2.38095 \times 10^{-7} \text{ H/m}}$$

$$\frac{1}{uZ_0} = \frac{1}{\frac{1}{\sqrt{LC}} \sqrt{L/C}} = C = \frac{1}{50(2.1 \times 10^8)} = \underline{9.52381 \times 10^{-11} \text{ F/m}}$$

$$\beta = \omega\sqrt{LC} = \frac{\omega}{u} = \frac{2\pi(550 \times 10^6)}{2.1 \times 10^8} = \underline{16.456 \text{ rad/m}}$$

$$\lambda = \frac{u}{f} = \frac{2.1 \times 10^8}{550 \times 10^6} = \underline{0.381 \text{ m}} = \underline{38.18 \text{ cm}}$$

$$\frac{\ell}{\lambda} = \frac{28 \text{ cm}}{38.18 \text{ cm}} = \underline{0.73} \Rightarrow \underline{\ell = 0.73\lambda}$$

capacitance per unit length = 95.238 pF/m phase constant = 16.456 rad/m
 inductance per unit length = 238.095 nH/m wavelength = 38.18 cm
 transmission line length (in terms of wavelength) = 0.73λ

EE 381 Quiz #1 (Fall 2017)

Name Key B

Instructions: Closed book & notes. Place answers in indicated spaces and show all work for credit.

Useful equations: $u = f\lambda = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$, $LC = \mu\epsilon$, $\beta = \omega\sqrt{LC} = \frac{\omega}{u}$, $\lambda = \frac{u}{f} = \frac{2\pi}{\beta}$, $Z_0 = \frac{V_0^+}{I_0^+} = \sqrt{\frac{L}{C}}$

A lossless 42 cm-long transmission line has a characteristic impedance of 50Ω and velocity of propagation of 2.2×10^8 m/s. Determine the inductance and capacitance per unit length. If operated at 450 MHz, calculate the phase constant, wavelength, and length (in terms of wavelength) of the transmission line.

$$\frac{Z_0}{u} = \frac{\sqrt{L/C}}{1/\sqrt{LC}} = L = \frac{50}{2.2 \times 10^8} = \underline{2.27 \times 10^{-7} \text{ H/m}}$$

$$\frac{1}{uZ_0} = \frac{1}{\frac{1}{\sqrt{LC}} \sqrt{L/C}} = C = \frac{1}{50(2.2 \times 10^8)} = \underline{9.09 \times 10^{-11} \text{ F/m}}$$

$$\beta = \frac{\omega}{u} = \frac{2\pi(450 \times 10^6)}{2.2 \times 10^8} = \underline{12.85197 \text{ rad/m}}$$

$$\lambda = \frac{u}{f} = \frac{2.2 \times 10^8}{450 \times 10^6} = 0.48 \text{ m} = \underline{48.88 \text{ cm}}$$

$$\frac{\ell}{\lambda} = \frac{42 \text{ cm}}{48.88 \text{ cm}} = 0.85909 \Rightarrow \underline{\ell = 0.85909 \lambda}$$

capacitance per unit length = 90.90 pF/m phase constant = 12.852 rad/m

inductance per unit length = 227.27 nH/m wavelength = 48.88 cm

transmission line length (in terms of wavelength) = 0.8591 \lambda