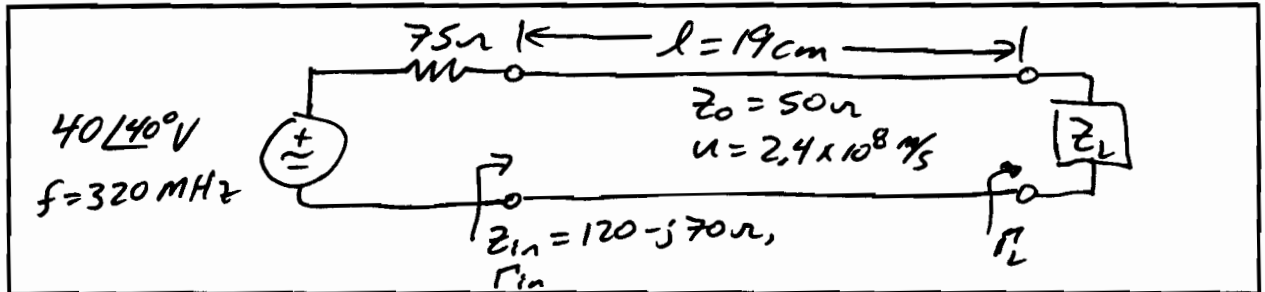


EE 381 Quiz #2 (Fall 2017)

Name Key A

Instructions: Closed book & notes (see back). Place answers in indicated spaces and show all work for credit.

A lossless 19 cm-long transmission line (50Ω characteristic impedance and 2.4×10^8 m/s velocity of propagation) is terminated with an unknown load. It is driven by a generator with voltage $40\angle 40^\circ$ V and impedance 75Ω operating at 320 MHz. If the input impedance is measured to be $120 - j70 \Omega$, sketch a fully labeled drawing of this transmission line circuit. Then, find the phase constant, input & load reflection coefficients, load impedance, and standing wave ratio. **Express reflection coefficients in polar/phasor format w/ angles in degrees, and impedances in rectangular format.**



$$\beta = \frac{\omega}{u} = \frac{2\pi(320 \times 10^6)}{2.4 \times 10^8} = \underline{8.37758 \text{ rad/m}}$$

$$\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = \frac{(120 - j70) - 50}{(120 - j70) + 50} = \underline{0.53846 \angle -22.61986^\circ}$$

$$\Gamma_L = \Gamma_{in} e^{+j2\beta l} = (0.5385 \angle -22.62^\circ) e^{+j2(8.37758)(0.19)}$$

$$= \underline{0.53846 \angle 159.7801^\circ}$$

$$Z_L = Z_0 \left[\frac{1 + \Gamma_L}{1 - \Gamma_L} \right] = 50 \left[\frac{1 + 0.5385 \angle 159.78^\circ}{1 - 0.5385 \angle 159.78^\circ} \right]$$

$$= \underline{15.4327 + j8.0898 \Omega}$$

$$S = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 0.53846}{1 - 0.53846} = \underline{3.333}$$

$$\beta = \underline{8.3776 \text{ rad/m}} \quad \Gamma_{in} = \underline{0.5385 \angle -22.62^\circ} \quad \Gamma_L = \underline{0.5385 \angle 159.78^\circ}$$


$$Z_L = \underline{15.433 + j8.0898 \Omega} \quad S = \underline{3.333}$$

EE 381 Quiz #2 (Fall 2017)

Name Key C

Instructions: Closed book & notes (see back). Place answers in indicated spaces and show all work for credit.

A lossless 16 cm-long transmission line (75Ω characteristic impedance and 2.2×10^8 m/s velocity of propagation) is terminated with an unknown load. It is driven by a generator with voltage $30 \angle 30^\circ$ V and impedance 50Ω operating at 340 MHz. If the input impedance is measured to be $100 - j40 \Omega$, sketch a fully labeled drawing of this transmission line circuit. Then, find the phase constant, input & load reflection coefficients, load impedance, and standing wave ratio. **Express reflection coefficients in polar/phasor format w/ angles in degrees, and impedances in rectangular format.**

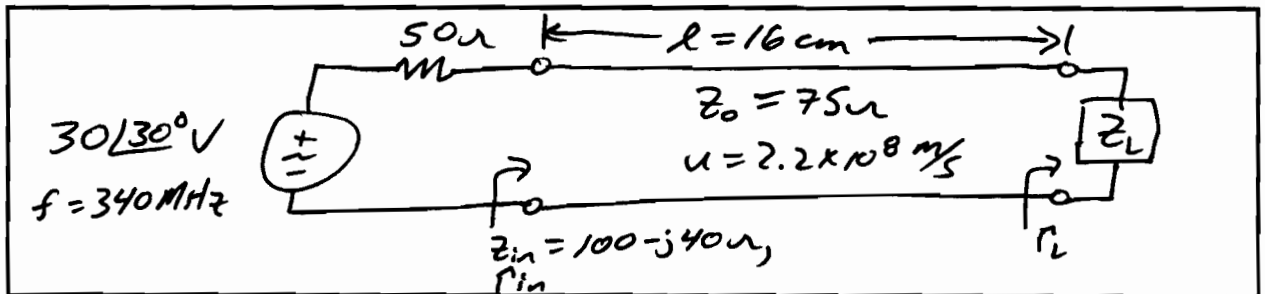

$$\beta = \frac{\omega}{u} = \frac{2\pi(340 \times 10^6)}{2.2 \times 10^8} = \underline{9.7104 \text{ rad/m}}$$

$$\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = \frac{(100 - j40) - 75}{(100 - j40) + 75} = \underline{0.26277 \angle -45.1196^\circ}$$

$$\Gamma_L = \Gamma_{in} e^{+j2\beta l} = (0.263 \angle -45.1^\circ) e^{j2(9.71)(0.16)} \\ = \underline{0.26277 \angle 132.9167^\circ}$$

$$Z_L = Z_0 \left[\frac{1 + \Gamma_L}{1 - \Gamma_L} \right] = 75 \left[\frac{1 + 0.263 \angle 132.9^\circ}{1 - 0.263 \angle 132.9^\circ} \right] \\ = \underline{48.9324 + j20.2293 \Omega}$$

$$S = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} = \frac{1 + 0.26277}{1 - 0.26277} = \underline{1.7128}$$

$$\beta = \underline{9.7104 \text{ rad/m}} \quad \Gamma_{in} = \underline{0.2628 \angle -45.12^\circ} \quad \Gamma_L = \underline{0.2628 \angle 132.92^\circ}$$

$$Z_L = \underline{48.932 + j20.229 \Omega} \quad S = \underline{1.7128}$$