

Homework 3
EE 381 Electric & Magnetic Fields (Fall 2024)
Wednesday, September 18, 2024

- 1) A lossless transmission line ($Z_0 = 50 \Omega$, $u = 2.08 \times 10^8$ m/s) of length 28.8λ is terminated with an unknown load. Using a vector network analyzer (VNA), an input reflection coefficient of $\Gamma_{in} = 0.50 \angle 60^\circ$ is measured. The transmission line (TL) is then connected to a generator with a voltage $36 \angle 0^\circ$ V and impedance 50Ω operating at 2 GHz. Draw the TL circuit. Then, determine the (a) propagation constant & wavelength, (b) input impedance, (c) phasor current & voltage and time-average power at the input, (d) phasor forward voltage wave amplitude, (e) phasor current & voltage and time-average power at the load.
- 2) Repeat the previous problem if the transmission line is now assumed to be lossy with a measured attenuation of 18 dB/100 ft.
- 3) For a matching network, a radar engineer needs a capacitive reactance of $-j40 \Omega$ at a frequency of 4 GHz. To achieve this goal, they are required to use stubs made from 50Ω coaxial transmission line with a phase velocity of 2.5×10^8 m/s. To allow connectors to be attached, the stubs must have a minimum length of 2 cm. Find the length of the shortest possible stubs with (a) open-circuit and (b) short-circuit terminations and sketch the resulting equivalent circuits.
- 4) 11.40 Use Smith chart. Also, determine input reflection coefficient.
- 5) 11.43 Use Smith chart. Also, determine the maximum and minimum impedances along the transmission line. Put locations in terms of wavelength λ .
- 6) 11.49 Use Smith chart. First, calculate wavelength λ .

Due Wednesday, September 25, 2024.

Notes:

- Express all currents, voltages, & reflection coefficients in the polar/phasor format with angles in degrees (e.g., $10 \angle 30^\circ$ V). Express impedances in rectangular format (e.g., $10 + j30 \Omega$).
- Where relevant, use **one** Smith chart per problem inserted immediately after the corresponding problem. **Clearly label** all work and relevant quantities on each Smith chart (e.g., Z_0 , f or λ , all points, arcs, distances, ...).