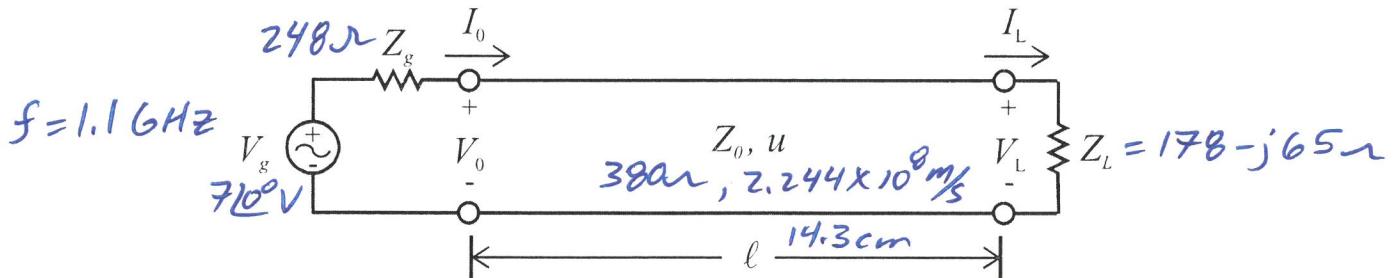


EE 381 Electric and Magnetic Fields Quiz #2 (Fall 2024)

Name *Key A*

Instructions: Open book & notes. Write answers in indicated spaces and show all work for credit.

For the circuit shown, the generator, $V_g = 7\angle 0^\circ$ V & $Z_g = 248 \Omega$, operates at a frequency of 1.1 GHz. It is connected to a lossless twin-lead transmission line where $Z_0 = 380 \Omega$, $u = 2.244 \times 10^8$ m/s, and $\ell = 14.3$ cm. The load impedance is $Z_L = 178 - j65 \Omega$. Calculate the phase constant, input and load reflection coefficients, input impedance, and SWR for this circuit.



$$\beta = \frac{\omega}{u} = \frac{2\pi(1.1 \times 10^9)}{2.244 \times 10^8} = 30.80 \text{ rad/m}$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{(178 - j65) - 380}{(178 + j65) + 380} = 0.3777 \angle -155.52^\circ$$

$$\Gamma_{in} = \Gamma_L e^{-j2\beta\ell} = (0.3777 \angle -155.52^\circ) e^{-j2(30.80)(0.143)} \\ = 0.3777 \angle 59.776^\circ$$

$$SWR = \frac{1+|\Gamma|}{1-|\Gamma|} = \frac{1+0.3777}{1-0.3777} = 2.214$$

$$Z_{in} = Z_0 \frac{1+\Gamma_{in}}{1-\Gamma_{in}} = 380 \frac{1+0.3777 \angle 59.776^\circ}{1-0.3777 \angle 59.776^\circ} \\ = 427.315 + j325.361 \Omega$$

phase constant = *30.80 rad/m*

load refl. coeff. = *0.3777 ∠ -155.52°*

input refl. coeff. = *0.3777 ∠ 59.776°*

SWR = *2.214*

input impedance = *427.3 + j325.361 Ω*


Express reflection coefficients in polar form, e.g., $A\angle\theta$ (deg), & impedance in rectangular form, e.g., $R + jX$.

EE 381 Electric and Magnetic Fields Quiz #2 (Fall 2024)

Name Key B

Instructions: Open book & notes. Write answers in indicated spaces and show all work for credit.

For the circuit shown, the generator, $V_g = 5\angle 0^\circ$ V & $Z_g = 388 \Omega$, operates at a frequency of 1.7 GHz. It is connected to a lossless twin-lead transmission line where $Z_0 = 380 \Omega$, $u = 2.635 \times 10^8$ m/s, and $\ell = 21.3$ cm. The load impedance is $Z_L = 138 + j95 \Omega$. Calculate the phase constant, input and load reflection coefficients, input impedance, and SWR for this circuit.

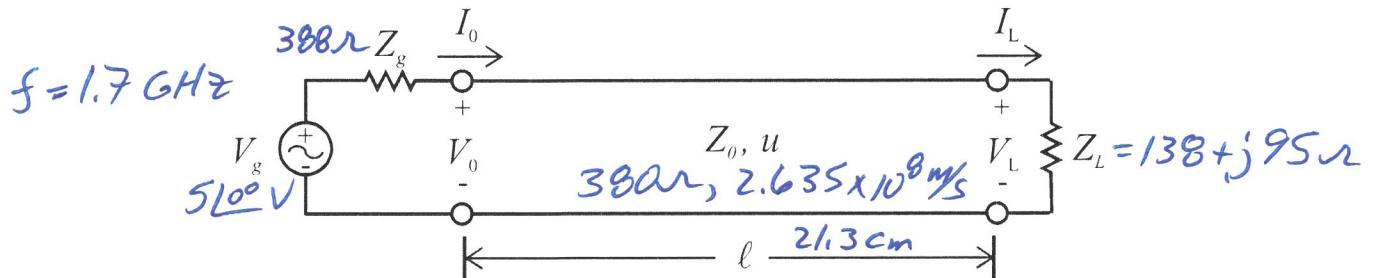

$$\beta = \frac{\omega}{u} = \frac{2\pi(1.7 \times 10^9)}{2.635 \times 10^8} = 40.5367 \text{ rad/m}$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{(138 + j95) - 380}{(138 + j95) + 380} = 0.4937 \angle 148.174^\circ$$

$$\Gamma_{in} = \Gamma_L e^{-j2\beta\ell} = (0.4937 \angle 148.174^\circ) e^{-j2(40.5367)(0.213)} \\ = 0.4937 \angle -121.245^\circ$$

$$SWR = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 0.4937}{1 - 0.4937} = 2.95$$

$$Z_{in} = Z_0 \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} = 380 \frac{1 + 0.4937 \angle -121.245^\circ}{1 - 0.4937 \angle -121.245^\circ} \\ = 163.682 - j182.686 \Omega$$

phase constant = 40.5367 rad/m

load refl. coeff. = $0.4937 \angle 148.174^\circ$

input refl. coeff. = $0.4937 \angle -121.245^\circ$

SWR = 2.95

input impedance = $163.68 - j182.69 \Omega$

Express reflection coefficients in polar form, e.g., $A\angle\theta$ (deg), & impedance in rectangular form, e.g., $R + jX$.