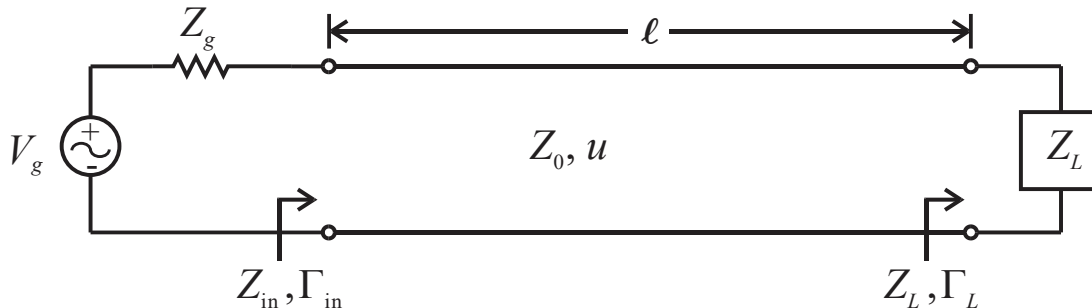


EE 381 Electric and Magnetic Fields Quiz #3 (Fall 2025)

Name KEY A

Instructions: Closed book & notes. Show all work for credit. Clearly label all points/work on Smith chart. Put reflection coefficients in polar format w/ angles in degrees. Express impedances in rectangular format.

Consider a lossless transmission line circuit where $Z_0 = 80 \Omega$, $f = 400 \text{ MHz}$, $u = 2.2 \times 10^8 \text{ m/s}$, $\ell = 69.47 \text{ cm}$, and the **input** impedance is measured to be $48 - j88 \Omega$. Using a **Smith Chart, compass, & straight edge**, find the input & load reflection coefficients, load impedance, and SWR.



- Normalize $z_{in} = Z_{in} / Z_0 = (48 - j88) / 80 \Rightarrow z_{in} = \mathbf{0.6 - j1.1 \Omega/\Omega}$.
- Plot z_{in} on Smith chart by finding intersection of $r=0.6$ circle with $x=-1.1$ arc.
- Set compass to distance from center of Smith chart to z_{in} point. Draw circle, centered on Smith Chart, through z_{in} point.
- Use compass to make marks on 'RFL COEFF, E or I' and 'SWR' scales. Read off $|\Gamma| = \mathbf{0.6}$ and $\mathbf{SWR = 4}$.
- Use straightedge to draw radial line through z_{in} from center of Smith chart. Use "ANGLE OF REFLECTION COEFFICIENT IN DEGREES" scale to read $\angle \Gamma_{in} = \mathbf{-75.5^\circ}$. Put magnitude & angle together to get input reflection coefficient $\mathbf{\Gamma_{in} = 0.6 \angle -75.5^\circ}$.
- Calculate wavelength to be $\lambda = u / f = 2.2 \times 10^8 / 400 \times 10^6 = 0.55 \text{ m} = 55 \text{ cm}$. The TL length in wavelengths is $\ell/\lambda = 69.47 / 55 = 1.263$. Subtract $2(0.5) = 1$ (i.e., remove integer multiples of $n\lambda/2$) to get $\ell/\lambda = \mathbf{0.263}$.
- Move $\ell/\lambda = \mathbf{0.263}$ in the "WAVELENGTHS TOWARD LOAD" direction on arc of constant $|\Gamma|$ from input point (0.3552) to load point ($0.3552 - 0.263 = 0.0922$) and draw radial line from center of Smith chart. The intersection of line & circle is location of z_L .
- At load point, read $\angle \Gamma_L = \mathbf{113.9^\circ}$ on "ANGLE OF REFLECTION COEFFICIENT IN DEGREES" scale and $z_L = \mathbf{0.35 + j0.6 \Omega/\Omega}$. The load reflection coefficient is then $\mathbf{\Gamma_L = 0.6 \angle 113.9^\circ}$ and load impedance is $Z_L = z_L Z_0 = (0.35 + j0.6) 80 \Rightarrow \mathbf{Z_L = 28 + j48 \Omega}$.

input refl. coeff. = $\mathbf{\Gamma_{in} = 0.6 \angle -75.5^\circ}$

load refl. coeff. = $\mathbf{\Gamma_L = 0.6 \angle 113.9^\circ}$

load impedance = $\mathbf{Z_L = 28 + j48 \Omega}$

SWR = $\mathbf{4}$


Exact answers- input refl. coeff. = $\Gamma_{in} = 0.603 \angle -75.475^\circ$

load refl. coeff. = $\Gamma_L = 0.603 \angle 113.95^\circ$

load impedance = $Z_L = 27.49 + j 47.57 \Omega$

SWR = 4.036

Simple Smith Chart

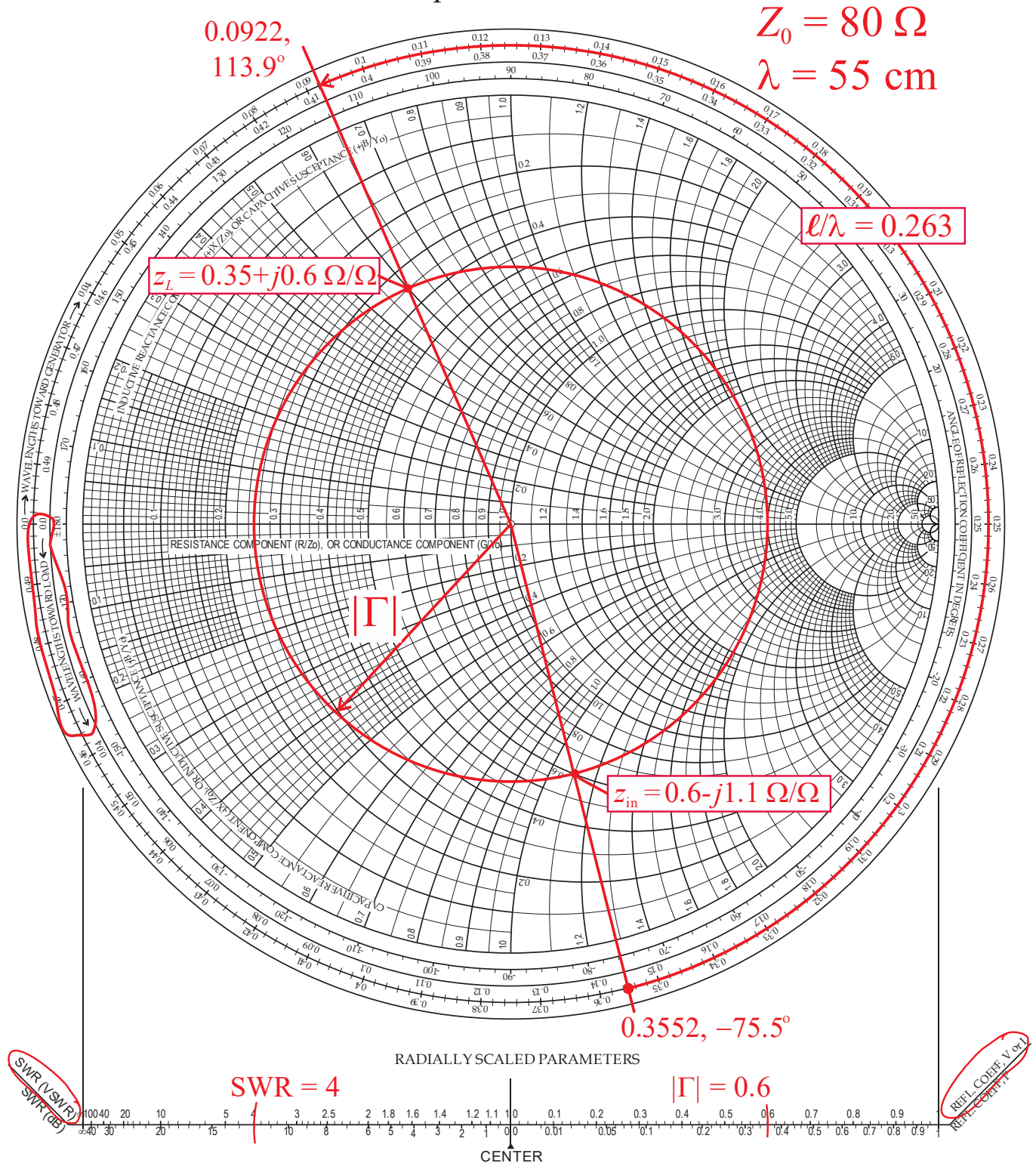


EE 381 Electric and Magnetic Fields Quiz #3 (Fall 2025)

Name KEY B

Instructions: Closed book & notes. Show all work for credit. Clearly label all points/work on Smith chart. Put reflection coefficients in polar format w/ angles in degrees. Express impedances in rectangular format.

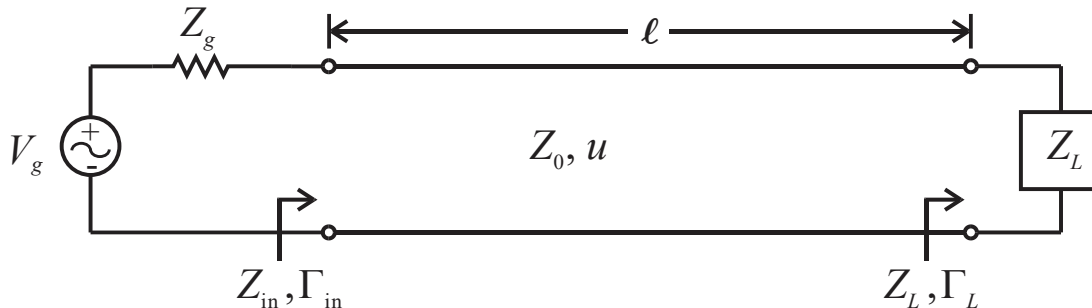Consider a lossless transmission line circuit where $Z_0 = 60 \Omega$, $f = 500 \text{ MHz}$, $u = 2.4 \times 10^8 \text{ m/s}$, $\ell = 53.26 \text{ cm}$, and the **input** impedance is measured to be $54 + j102 \Omega$. Using a **Smith Chart, compass, & straight edge**, find the input & load reflection coefficients, load impedance, and SWR.



- Normalize $z_{in} = Z_{in} / Z_0 = (54 + j102) / 60 \Rightarrow z_{in} = \mathbf{0.9 + j1.7 \Omega/\Omega}$.
- Plot z_{in} on Smith chart by finding intersection of $r=0.9$ circle with $x=1.7$ arc.
- Set compass to distance from center of Smith chart to z_{in} point. Draw circle, centered on Smith Chart, through z_{in} point.
- Use compass to make marks on ‘RFL COEFF, E or I’ and ‘SWR’ scales. Read off $|\Gamma| = \mathbf{0.67}$ and $\mathbf{SWR = 5}$.
- Use straightedge to draw radial line through z_{in} from center of Smith chart. Use “ANGLE OF REFLECTION COEFFICIENT IN DEGREES” scale to read $\angle \Gamma_{in} = \mathbf{51.6^\circ}$. Put magnitude & angle together to get input reflection coefficient $\mathbf{\Gamma_{in} = 0.67 \angle 51.6^\circ}$.
- Calculate wavelength to be $\lambda = u / f = 2.4 \times 10^8 / 500 \times 10^6 = 0.48 \text{ m} = 48 \text{ cm}$. The TL length in wavelengths is $\ell/\lambda = 53.26 / 48 = 1.11$. Subtract $2(0.5) = 1$ (i.e., remove integer multiples of $n\lambda/2$) to get $\ell/\lambda = \mathbf{0.11}$.
- Move $\ell/\lambda = \mathbf{0.263}$ in the “WAVELENGTHS TOWARD LOAD” direction on arc of constant $|\Gamma|$ from input point (0.1782) to load point ($0.1782 - 0.11 = 0.0682$) and draw radial line from center of Smith chart. The intersection of line & circle is location of z_L .
- At load point, read $\angle \Gamma_L = \mathbf{130.6^\circ}$ on “ANGLE OF REFLECTION COEFFICIENT IN DEGREES” scale & $\mathbf{z_L = 0.24 + j0.44 \Omega/\Omega}$. The load reflection coefficient is then $\mathbf{\Gamma_L = 0.67 \angle 130.6^\circ}$ & load impedance is $Z_L = z_L Z_0 = (0.24 + j0.44)60 \Rightarrow \mathbf{Z_L = 14.4 + j26.4 \Omega}$.

input refl. coeff. = $\mathbf{\Gamma_{in} = 0.67 \angle 51.6^\circ}$

load refl. coeff. = $\mathbf{\Gamma_L = 0.67 \angle 130.6^\circ}$

load impedance = $\mathbf{Z_L = 14.4 + j26.4 \Omega}$

SWR = $\mathbf{5}$

Exact answers- input refl. coeff. = $\Gamma_{in} = 0.668 \angle 51.55^\circ$

load refl. coeff. = $\Gamma_L = 0.668 \angle 130.45^\circ$

load impedance = $Z_L = 14.37 + j 26.37 \Omega$

SWR = 5.023

Simple Smith Chart

$Z_0 = 60 \Omega$

$\lambda = 48 \text{ cm}$

