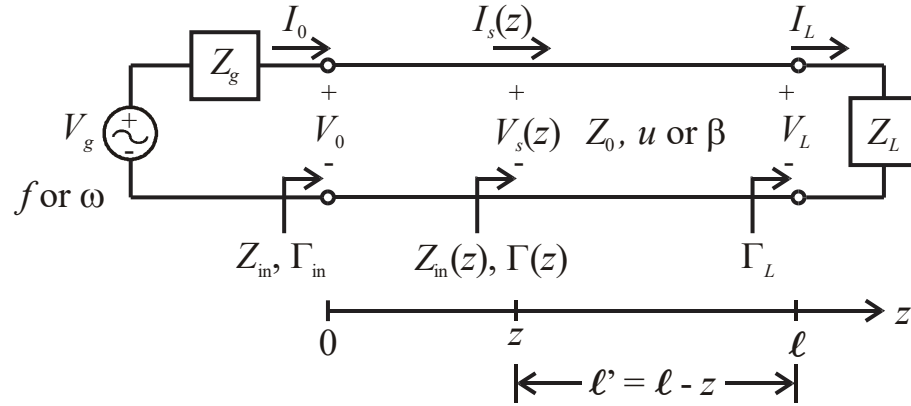


Lossless Transmission Lines (TLs)



Phase velocity (m/s): $u = f\lambda = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$

where f is frequency (Hz), ω is radian frequency (rad/s), and L & C are the per-unit-length inductance & capacitance.

Phase constant (rad/m): $\beta = \frac{\omega}{u} = \frac{2\pi}{\lambda} = \omega\sqrt{LC}$

Wavelength (m): $\lambda = \frac{u}{f} = \frac{2\pi}{\beta}$

Characteristic impedance (Ω): $Z_0 = \frac{V_0^+}{I_0^+} = \frac{-V_0^-}{I_0^-} = \sqrt{\frac{L}{C}} = R_0$ (real positive value)

Phasor voltage: $V_s(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z} = V_0^+ e^{-j\beta z} [1 + \Gamma(z)]$ for $0 \leq z \leq \ell$.

Phasor current: $I_s(z) = I_0^+ e^{-j\beta z} + I_0^- e^{+j\beta z} = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{+j\beta z} = \frac{V_0^+}{Z_0} e^{-j\beta z} [1 - \Gamma(z)]$ for $0 \leq z \leq \ell$.

where $V_0^+ = |V_0^+| \angle \theta_V^+$, $V_0^- = |V_0^-| \angle \theta_V^-$, $I_0^+ = |I_0^+| \angle \theta_I^+$, and $I_0^- = |I_0^-| \angle \theta_I^-$ are complex coefficients representing the amplitudes of the forward and backward traveling voltages and currents.

Forward and backward traveling voltages (V) and currents (A):

Note that, at the input ($z = 0$), $V_s(0) = V_0 = V_0^+ + V_0^-$ and $I_s(0) = I_0 = I_0^+ + I_0^- = \frac{V_0^+}{Z_0} - \frac{V_0^-}{Z_0}$

$$V_0^+ = 0.5(V_0 + I_0 Z_0) = \frac{V_0}{1 + \Gamma(0)} = 0.5(V_L + I_L Z_0) e^{+j\beta \ell} \quad \text{and} \quad I_0^+ = \frac{V_0^+}{Z_0}$$

$$V_0^- = 0.5(V_0 - I_0 Z_0) = V_0 - V_0^+ = 0.5(V_L - I_L Z_0) e^{-j\beta \ell} = V_0^+ \Gamma(0) \quad \text{and} \quad I_0^- = \frac{-V_0^-}{Z_0}$$

Time-domain voltage: $V(z, t) = |V_0^+| \cos(\omega t - \beta z + \theta_V^+) + |V_0^-| \cos(\omega t + \beta z + \theta_V^-)$ for $0 \leq z \leq \ell$.

$$I(z, t) = |I_0^+| \cos(\omega t - \beta z + \theta_I^+) + |I_0^-| \cos(\omega t + \beta z + \theta_I^-)$$

Time-domain current: $= \frac{|V_0^+|}{Z_0} \cos(\omega t - \beta z + \theta_V^+) - \frac{|V_0^-|}{Z_0} \cos(\omega t + \beta z + \theta_V^-)$ for $0 \leq z \leq \ell$.

Reflection coefficient (unitless): $\Gamma(z) = \frac{V_{\text{ref}}(z)}{V_{\text{inc}}(z)} = \frac{-I_{\text{ref}}(z)}{I_{\text{inc}}(z)} = \frac{Z_{\text{in}}(z) - Z_0}{Z_{\text{in}}(z) + Z_0} = \Gamma_L e^{-j2\beta(\ell-z)} = \Gamma_{\text{in}} e^{j2\beta z}$ for $0 \leq z \leq \ell$.

of particular interest are: **load reflection coefficient** $\Gamma_L = \frac{V_0^-}{V_0^+} e^{+j2\beta\ell} = \Gamma(0) e^{+j2\beta\ell} = \Gamma_{\text{in}} e^{+j2\beta\ell} = \frac{Z_L - Z_0}{Z_L + Z_0}$

and

input reflection coefficient $\Gamma_{\text{in}} = \Gamma(\ell) = \frac{Z_{\text{in}}(\ell) - Z_0}{Z_{\text{in}}(\ell) + Z_0} = \frac{Z_{\text{in}} - Z_0}{Z_{\text{in}} + Z_0} = \Gamma_L e^{-j2\beta\ell}$.

Notes: $|\Gamma(z)|$ is constant and $0 \leq |\Gamma(z)| \leq 1$ for passive loads and transmission lines.

Input impedance (Ω): $Z_{\text{in}}(z) = \frac{V_s(z)}{I_s(z)} = Z_0 \left[\frac{Z_L + jZ_0 \tan[\beta(\ell-z)]}{Z_0 + jZ_L \tan[\beta(\ell-z)]} \right] = Z_0 \left[\frac{1 + \Gamma(z)}{1 - \Gamma(z)} \right]$ for $0 \leq z \leq \ell$.

at input $z = 0$: $Z_{\text{in}}(0) = Z_{\text{in}} = \frac{V_0}{I_0} = Z_0 \left[\frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} \right] = Z_0 \left[\frac{Z_L + jZ_0 \tan(\beta\ell)}{Z_0 + jZ_L \tan(\beta\ell)} \right] = Z_0 \left[\frac{1 + \Gamma(0)}{1 - \Gamma(0)} \right] = Z_0 \left[\frac{1 + \Gamma_{\text{in}}}{1 - \Gamma_{\text{in}}} \right]$

at load $z = \ell$: $Z_{\text{in}}(\ell) = Z_L = \frac{V_L}{I_L} = Z_0 \left[\frac{1 + \Gamma_L}{1 - \Gamma_L} \right]$

Standing wave ratio (unitless): $SWR = S = \frac{V_{\text{max}}}{V_{\text{min}}} = \frac{I_{\text{max}}}{I_{\text{min}}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$ and $1 \leq S < \infty$ for passive loads.


Power (W): $P_{\text{ave}}(z) = 0.5 \text{Re}\{V(z)I^*(z)\} = 0.5 \frac{|V_0^+|^2}{Z_0} [1 - |\Gamma(z)|^2]$ for $0 \leq z \leq \ell$.

Input Power (W): $P_{\text{ave}}(0) = P_{\text{in}} = 0.5 \text{Re}\{V_0 I_0^*\} = 0.5 \frac{|V_0^+|^2}{Z_0} [1 - |\Gamma_{\text{in}}|^2]$

Load Power (W): $P_{\text{ave}}(\ell) = P_L = 0.5 \text{Re}\{V_L I_L^*\} = 0.5 \frac{|V_0^+|^2}{Z_0} [1 - |\Gamma_L|^2]$

Note: Time-average real power is constant on a lossless transmission line, i.e., $P_{\text{ave}}(z) = P_{\text{in}} = P_L$.

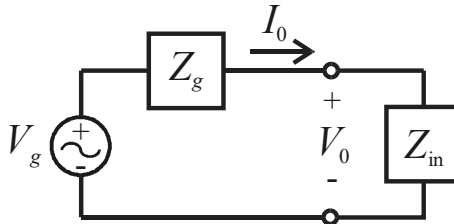The input phasor voltage $V_s(0) = V_0$ and current $I_s(0) = I_0$ can be found using the equivalent circuit-



where, by circuit theory, $V_0 = V_g \left(\frac{Z_{\text{in}}}{Z_g + Z_{\text{in}}} \right)$ and $I_0 = \frac{V_g}{Z_g + Z_{\text{in}}}$.