

- 11.30 Find the input impedance of a short-circuited coaxial transmission line of Figure 11.48 if $Z_0 = 65 + j38 \Omega$, $\gamma = 0.7 + j2.5/\text{m}$, $\ell = 0.8 \text{ m}$.


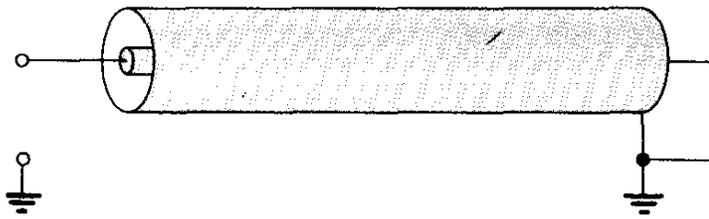


FIGURE 11.48

For Problem 11.30

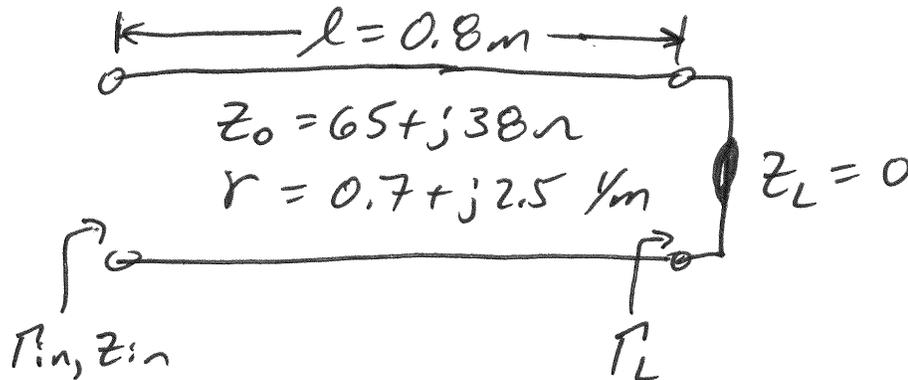- Also, calculate the load Γ_L & input Γ_{in} reflection coefficients.



$$(11.36) \quad \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{0 - Z_0}{0 + Z_0} \Rightarrow \underline{\underline{\Gamma_L = -1}}$$

$$(11.37) \quad \Gamma(z) = \Gamma_L e^{-2\gamma \ell'} \quad \ell' = \ell - z$$

$$\hookrightarrow \Gamma_{in} = \Gamma(0) = \Gamma_L e^{-2\gamma \ell}$$

$$= -1 e^{-2(0.7 + j2.5)0.8}$$

$$\underline{\underline{\Gamma_{in} = 0.32628 \angle -49.183^\circ}}$$

$$(11.33) \quad Z_{in} = Z_0 \left[\frac{Z_L + Z_0 \tanh(\gamma \ell)}{Z_0 + Z_L \tanh(\gamma \ell)} \right] \text{ or } Z_0 \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}}$$

$$= (65 + j38) \frac{1 + 0.3263 \angle -49.18^\circ}{1 - 0.3263 \angle -49.18^\circ}$$

$$\underline{\underline{Z_{in} = 113.024 + j2.726 \Omega}}$$