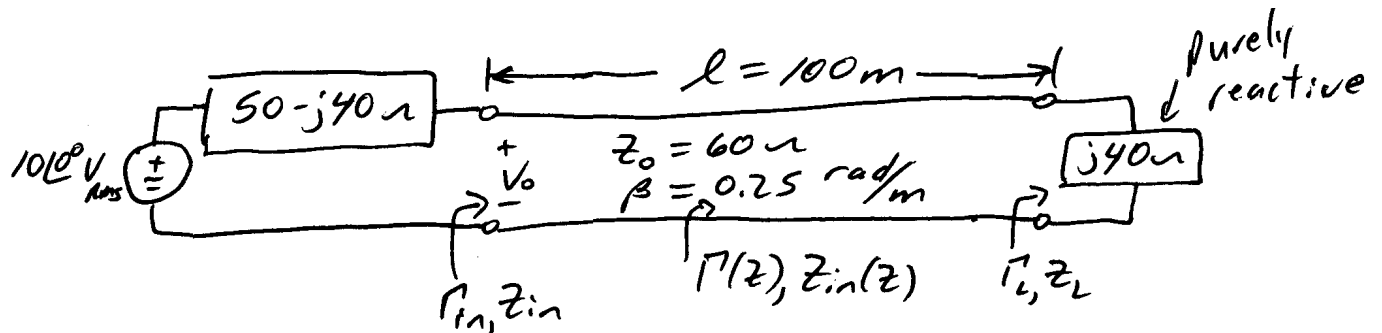


11.33 A 60Ω lossless line is connected to a source with $V_g = 10 \angle 0^\circ \text{ V}_{\text{rms}}$ and $Z_g = 50 - j40 \Omega$ and terminated with a load of $j40 \Omega$. If the line is 100 m long and $\beta = 0.25 \text{ rad/m}$, calculate Z_{in} and V at

- (a) The sending end
- (b) The receiving end
- (c) 4 m from the load
- (d) 3 m from the source

• Note that generator voltage is in RMS. Before parts b)-d), find V_0^+ , V_0^- , & $V_s(z)$ in RMS. **Hint:** What the text calls V is $V_s(z)$.



$$(11.36) \Gamma_L = \frac{z_L - z_0}{z_L + z_0} = \frac{j40 - 60}{j40 + 60} = 1 \angle 112.6199^\circ$$

$$\Gamma(z) = \Gamma_L e^{-j2\beta(l-z)} = (1 \angle 112.62^\circ) e^{-j0.5(100-z)}$$


a) sending end $\Rightarrow z=0$

$$\Gamma_{\text{in}} = \Gamma(0) = (1 \angle 112.62^\circ) e^{-j0.5(100)} = 1 \angle 127.8309^\circ$$

$$z_{\text{in}}(0) = z_{\text{in}} = z_0 \frac{1 + \Gamma_{\text{in}}}{1 - \Gamma_{\text{in}}} = 60 \frac{1 + 1 \angle 127.83^\circ}{1 - 1 \angle 127.83^\circ}$$

$$\underline{z_{\text{in}}(0) = z_{\text{in}} = j29.374 \Omega}$$

Equivalent Circuit

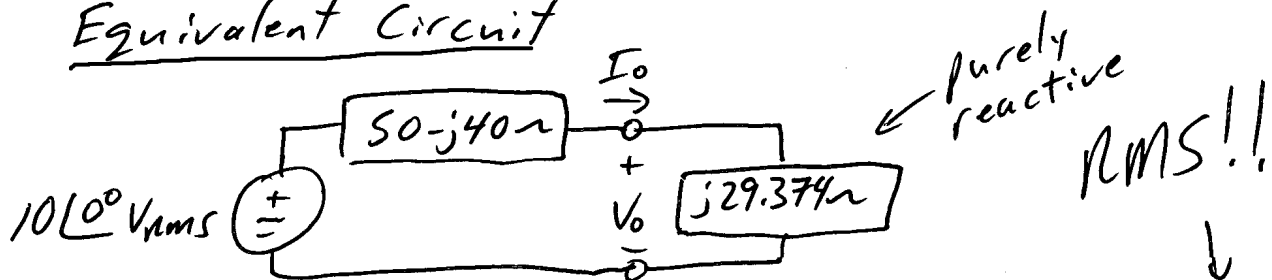

$$V_0 = V_s(0) = 10 \angle 0^\circ \frac{j29.374}{50 - j40 + j29.374} = \underline{5.746 \angle 101.998^\circ \text{ V}_{\text{rms}}}$$

$$I_0 = \frac{10 \angle 0^\circ}{50 - j40 + j29.374} = 0.19563 \angle 111.998^\circ \text{ A}_{\text{rms}}$$

Before parts b)-d), find V_0^+ , V_0^- , and $V_s(z)$.

$$(11.27a) \quad V_0^+ = \frac{1}{2} [V_0 + I_0 z_0] \quad \text{or} \quad \frac{V_0}{1 + \Gamma_{in}} = \frac{5.746 \angle 102^\circ}{1 + 1 \angle 127.83^\circ}$$

$$\underline{V_0^+ = 6.5345 \angle 38.083^\circ \text{ V}_{rms}}$$

$$(11.27b) \quad V_0^- = \frac{1}{2} [V_0 - I_0 z_0] \quad \text{or} \quad V_0 - V_0^+ = (5.746 \angle 102^\circ) - 6.53 \angle 38^\circ$$

$$\underline{V_0^- = 6.5345 \angle 165.914^\circ \text{ V}_{rms}}$$

$$(11.24) \quad V_s(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z}$$

$$V_s(z) = (6.5345 \angle 38.08^\circ) e^{-j0.25z} + (6.5345 \angle 165.91^\circ) e^{j0.25z} \text{ V}_{rms}$$

$$0 \leq z \leq 100 \text{ m}$$

b) receiving end ($z = l = 100 \text{ m}$)

$$\underline{Z_{in}(100 \text{ m}) = Z_L = j40 \Omega \quad (\text{given})}$$

$$V_s(100 \text{ m}) = V_L = (6.53 \angle 38^\circ) e^{-j0.25(100)} + (6.53 \angle 166^\circ) e^{j0.25(100)}$$

$$\underline{V_s(100 \text{ m}) = V_L = 7.2494 \angle 101.998^\circ \text{ V}_{rms}}$$

c) 4 m from load $\Rightarrow z = 100 - 4 = 96 \text{ m}$

$$\Gamma(96 \text{ m}) = (1 \angle 112.62^\circ) e^{-j0.5(100-96)} = 1 \angle -1.972^\circ$$

$$Z_{in}(96 \text{ m}) = 60 \left(\frac{1 + 1 \angle -1.972^\circ}{1 - 1 \angle -1.972^\circ} \right)$$

$$\underline{Z_{in}(96 \text{ m}) = -j3486.755 \Omega}$$

c) cont.

$$V_s(96m) = (6.53 \angle 38^\circ) e^{-j0.25(96)} + (6.53 \angle 166^\circ) e^{j0.25(96)}$$

$$\underline{\underline{V_s(96m) = 13.067 \angle 101.998^\circ \text{ V}_{rms}}}$$

d) 3m from source $\Rightarrow z = 3m$

$$\Gamma(3m) = (1 \angle 112.62^\circ) e^{-j0.5(100-3)}$$

$$\Gamma(3m) = 1 \angle -146.225^\circ$$

$$Z_{in}(3m) = 60 \left(\frac{1 + 1 \angle -146.225^\circ}{1 - 1 \angle -146.225^\circ} \right)$$

$$\underline{\underline{Z_{in}(3m) = -j18.215 \Omega}}$$

$$V_s(3m) = (6.53 \angle 38^\circ) e^{-j0.25(3)} + (6.53 \angle 166^\circ) e^{j0.25(3)}$$

$$\underline{\underline{V_s(3m) = 3.796 \angle -78.002^\circ \text{ V}_{rms}}}$$