

11.41 A lossless $100\ \Omega$ transmission line is terminated in an unknown impedance Z_L . The standing wave ratio is 2.4, and the nearest voltage minimum is 0.2λ from the load. Find Z_L and Γ .

- Use Smith chart. Also, find $Z_{\min}$.

- 1) Using the “SWR (VSWR)” scale, set compass to 2.4. Then, use compass to draw a circle, centered on Smith chart.
- 2) Read $r_{\min} = 0.417$ where the circle intersects the real axis to left of center. Unnormalize to get $Z_{\min} = z_{\min} Z_0 = (0.417)100 \Rightarrow \boxed{Z_{\min} = 41.7\ \Omega}$.
- 3) Next, use compass to mark the “REFL. COEFF. V or I” scale below Smith chart on right side to find $|\Gamma| = |\Gamma| = 0.41$.
- 4) Use a straight edge to draw radial line from center of Smith chart through $r_{\min}$ and outer rings of Smith chart at **0** on “WAVELENGTHS TOWARD LOAD” scale. Use a straight edge to draw radial line from center of Smith chart through 0.2 on “WAVELENGTHS TOWARD LOAD” scale.
- 5) At intersection of this radial line and the $|\Gamma| = 0.41$ circle, read normalized load impedance to be $z_L = 1.65 - j0.96\ \Omega/\Omega$. Calculate load impedance to be $Z_L = z_L Z_0 = (1.65 - j0.96)100 \Rightarrow \boxed{Z_L = 165 - j96\ \Omega}$.
- 6) Use the “ANGLE OF REFLECTION COEFFICIENT IN DEGREES” scale to read $\angle \Gamma_L = -36^\circ$. Put magnitude and angle of the load reflection coefficient together to get $\Rightarrow \boxed{\Gamma = \Gamma_L = 0.41 \angle -36^\circ}$.

Simple Smith Chart

$Z_0 = 100 \Omega$
 λ unspecified

