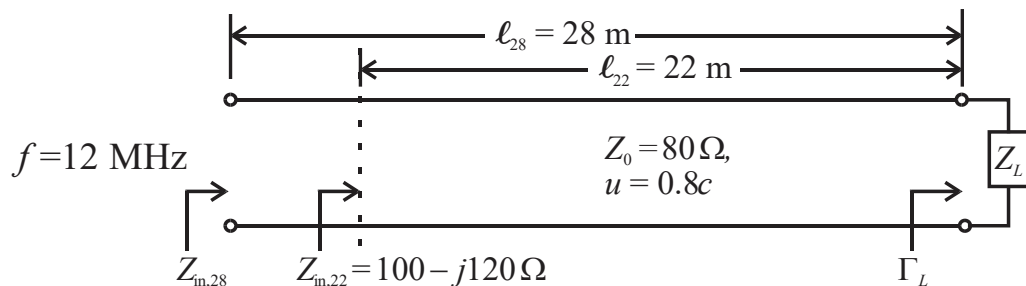


11.49 An $80\ \Omega$ transmission line operating at 12 MHz is terminated by a load Z_L . At 22 m from the load, the input impedance is $100 - j120\ \Omega$. If $u = 0.8c$,

- Calculate Γ_L , $Z_{in, \max}$, and $Z_{in, \min}$.
- Find Z_L , s , and the input impedance at 28 m from the load.
- How many $Z_{in, \max}$ and $Z_{in, \min}$ are there between the load and the $100 - j120\ \Omega$ input impedance?

- Use Smith chart. First, calculate wavelength λ .



➤ Wavelength $\lambda = u/f = 0.8(2.9979 \times 10^8)/12 \times 10^6 \Rightarrow \lambda = 19.986\ \text{m}$.

a)

- Normalize $Z_{in,22}$ & plot on Smith chart. $z_{in,22} = Z_{in}/Z_0 = (100 - j120)/80 = 1.25 - j1.5\ \Omega/\Omega$.
- Set compass to distance between center of Smith chart and $z_{in,22}$. Use compass to draw circle, centered on Smith chart, through $z_{in,22}$.
- Next, use compass to mark the “REFL. COEFF. V or I” scale below Smith chart on right side to find $|\Gamma_{in}| = |\Gamma_L| = 0.562$.
- Calculate $l_{22}/\lambda = 22/19.986 = 1.101$. Move $1.101 - 2(0.5) = 0.101$ on circle of constant $|\Gamma|$ from $z_{in,22}$ point in “WAVELENGTHS TOWARD LOAD” direction from 0.1845 to $0.1845 + 0.101 = 0.2855$. Draw radial line from center of Smith chart.
- Use the “ANGLE OF REFLECTION COEFFICIENT IN DEGREES” scale to read $\angle \Gamma_L = 25.7^\circ$.
- Put magnitude & angle of the load reflection coefficient together $\Gamma_L = 0.562 \angle 25.7^\circ$.
- At intersection of $|\Gamma| = 0.562$ circle w/ real axis to right of origin read, $r_{\max} = 3.57$. Calculate maximum input impedance $Z_{in, \max} = r_{\max} Z_0 = (3.57)80 \Rightarrow Z_{in, \max} = 285.6\ \Omega$.
- At intersection of $|\Gamma| = 0.562$ circle w/ real axis to left of origin read, $r_{\min} = 0.28$. Calculate minimum impedance $Z_{in, \min} = r_{\min} Z_0 = (0.28)80 \Rightarrow Z_{in, \min} = 22.4\ \Omega$.

b)

- At Γ_L point, read off normalized load impedance $z_L = 2.25 + j1.61\ \Omega/\Omega$.
- Calculate load impedance $Z_L = z_L Z_0 = (2.25 + j1.61)80 \Rightarrow Z_L = 180 + j128.8\ \Omega$.
- Use compass to mark SWR (VSWR) scale below Smith chart on left side.
- Read standing wave ratio to be $s = \text{SWR} = r_{\max} = 3.57$.

- Calculate $l_{28}/\lambda = 28/19.986 = 1.401$. Move $1.401 - 2(0.5) = 0.401$ on the circle of constant $|\Gamma|$ in “WAVELENGTHS TOWARD GENERATOR” direction from z_L point, i.e., to $0.401 - 0.2855 = 0.1155$. Draw radial line from center of Smith chart.
- Read $z_{in,28} = 0.47 + j0.77 \Omega/\Omega$. Calculate the input impedance 28 m from load to be $Z_{in,28} = z_{in,28} Z_0 = (0.47 + j0.77)80 \Rightarrow Z_{in,28} = 37.6 + j61.6 \Omega$.

c) Since $l_{22}/\lambda = 1.101$ or by looking at Smith chart, we will pass through the $Z_{in,max}$ (r_{max}) point **3 times** and through the $Z_{in,min}$ (r_{min}) point **2 times**.

