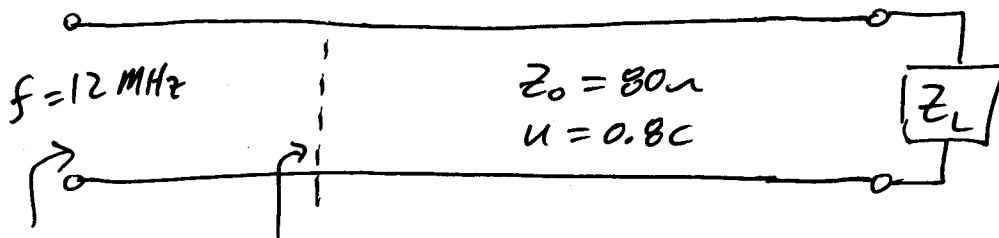


11.49 An 80Ω transmission line operating at 12 MHz is terminated by a load Z_L . At 22 m from the load, the input impedance is $100 - j120 \Omega$. If $u = 0.8c$,

- Calculate Γ_L , $Z_{in, max}$, and $Z_{in, min}$.
- Find Z_L , s , and the input impedance at 28 m from the load.
- How many $Z_{in, max}$ and $Z_{in, min}$ are there between the load and the $100 - j120 \Omega$ input impedance?

- Solve this problem analytically, don't use Smith chart.



$$Z_{in}(l' = 28m) \quad Z_{in}(l' = 22m) = 100 - j120 \Omega$$

$$\beta = \frac{\omega}{u} = \frac{2\pi(12 \times 10^6)}{0.8(2.9979 \times 10^8)} = 0.31438 \frac{\text{rad}}{\text{m}} \quad (11.21a)$$

$$(11.37) \quad \Gamma_{in, 22} = \frac{Z_{in, 22} - Z_0}{Z_{in, 22} + Z_0} = \frac{(100 - j120) - 80}{(100 - j120) + 80} = 0.56235 \angle -46.848^\circ$$

$$VSWR = S = \frac{1 + |\Gamma|}{1 - |\Gamma|} = 3.570 \quad (11.38a)$$

$$a) \quad \Gamma_L = \Gamma_{in, 22} e^{j2\beta l'} = 0.56235 \angle -46.848^\circ e^{j2(0.3144)22}$$

$$\hookrightarrow \underline{\underline{\Gamma_L = 0.56235 \angle 25.701^\circ}}$$

$$(11.39a) \quad Z_{in, max} = S Z_0 = 3.57(80) \Rightarrow \underline{\underline{Z_{in, max} = 285.59 \Omega}}$$

$$(11.39b) \quad Z_{in, min} = \frac{Z_0}{S} = \frac{80}{3.57} \Rightarrow \underline{\underline{Z_{in, min} = 22.41 \Omega}}$$

b) (11.36) & notes

$$Z_L = Z_0 \frac{1 + \Gamma_L}{1 - \Gamma_L} = 80 \frac{1 + 0.56 \angle 25.7^\circ}{1 - 0.56 \angle 25.7^\circ} \Rightarrow \underline{\underline{Z_L = 180.65 + j128.86 \Omega}}$$

b) cont. Per earlier calculation, $S = 3.570$

$$\begin{aligned}
 (11.34) \quad Z_{in}(l' = 28m) &= Z_0 \left[\frac{Z_L + jZ_0 \tan(\beta l')}{Z_0 + jZ_L \tan(\beta l')} \right] \\
 &= 80 \left[\frac{(180.65 + j128.86) + j80 \tan(0.3144(28))}{80 + j(180.65 + j128.86) \tan(0.3144(28))} \right] \\
 \underline{\underline{Z_{in}(l' = 28m) = 37.637 + j61.447 \, \Omega}}
 \end{aligned}$$

c) First find λ & $\lambda/2$

$$\lambda = \frac{u}{f} = \frac{0.8(2.9979 \times 10^8)}{12 \times 10^6} = 19.986 \, m$$

$$\frac{l}{\lambda} = \frac{22m}{19.986} = 1.101 \quad \text{or} \quad \frac{l}{\lambda/2} = 2.201$$

$\Rightarrow$ we will see at least two min & max

$$Z_{in, \max} \text{ occur when } \Gamma(z) = \Gamma_{\max} = |\Gamma| e^{j\theta_{\max}} = \Gamma_L e^{-j2\beta l'}$$

$$\text{where } \theta_{\max} = 0, -2\pi, -4\pi, \dots = \theta_L - 2\beta l' = \theta_L - 2\beta(22 - z_{\max})$$

$$\theta_{\max} = 25.701^\circ \left(\frac{\pi}{180}\right) - 2(0.3144)(22 - z_{\max})$$

$$\#1 \quad \theta_{\max,1} = 0 \Rightarrow z_{\max,1} = \frac{0 - 25.7(\pi/180) + 2(0.3144)22}{2(0.3144)} = 21.287 \, m$$

$$\#2 \quad \theta_{\max,2} = -2\pi \Rightarrow z_{\max,2} = \frac{-2\pi - 25.7(\pi/180) + 2(0.3144)22}{2(0.3144)} = 11.294 \, m$$

$$\#3 \quad \theta_{\max,3} = -4\pi \Rightarrow z_{\max,3} = \frac{-4\pi - 25.7(\pi/180) + 2(0.3144)22}{2(0.3144)} = 1.3 \, m$$

$\Rightarrow$ There are three (3) $Z_{in, \max}$

c) $Z_{in, min}$ occur when $\Gamma(z) = \Gamma_{min} = |\Gamma| e^{j\theta_{min}} = \Gamma_L e^{-j2\beta l'}$

where $\theta_{min} = -\pi, -3\pi, \dots = \theta_L - 2\beta l' = \theta_L - 2\beta(22 - z_{min})$

$$\theta_{min} = 25.701^\circ \left(\frac{\pi}{180}\right) - 2(0.3144)(22 - z_{min})$$

#1 $\theta_{min1} = -\pi \Rightarrow z_{min1} = \frac{-\pi - 25.7(\frac{\pi}{180}) + 2(0.3144)22}{2(0.3144)} = 16.29m$

#2 $\theta_{min2} = -3\pi \Rightarrow z_{min2} = \frac{-3\pi - 25.7(\frac{\pi}{180}) + 2(0.3144)22}{2(0.3144)} = 6.3m$

#3 $\theta_{min3} = -5\pi \Rightarrow z_{min3} = \frac{-5\pi - 25.7(\frac{\pi}{180}) + 2(0.3144)22}{2(0.3144)} = -3.7m$
No!

$\Rightarrow$ There are two (2) $Z_{in, min}$