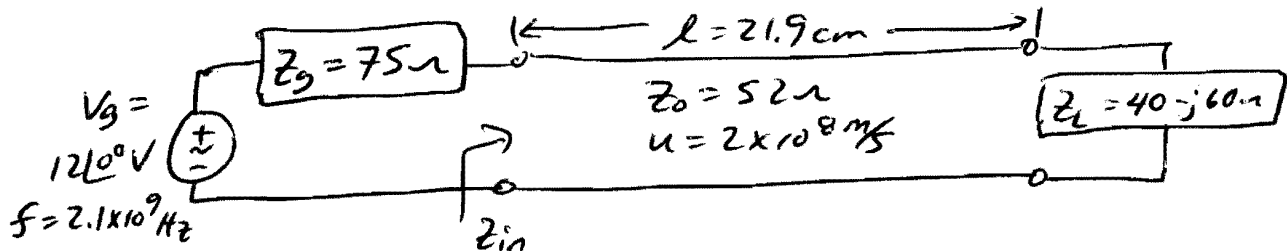


A lossless coaxial transmission line ( $Z_0 = 52 \Omega$ ,  $u = 2 \times 10^8$  m/s) of length  $l = 21.9$  cm is terminated with a load  $Z_L = 40 - j60 \Omega$ . The transmission line is connected to a  $75 \Omega$  signal generator operating at  $2.1$  GHz with a phasor voltage  $V_g = 12 \angle 0^\circ$  V. First, sketch the transmission line circuit. Then, determine (a) the phase constant  $\beta$ , wavelength  $\lambda$ , & length  $l$  (in terms of  $\lambda$ ) of the transmission line, (b) input impedance  $Z_{in}$ , and (c) total input phasor current  $I_0$  & voltage  $V_0$ .



$$a) \quad \beta = \frac{\omega}{u} = \frac{2\pi(2.1 \times 10^9)}{2 \times 10^8} = \underline{\underline{65.973 \text{ rad/m}}}$$

$$\lambda = \frac{2\pi}{\beta} = \frac{u}{f} = \frac{2 \times 10^8}{2.1 \times 10^9} = \underline{\underline{0.09524 \text{ m} = 9.524 \text{ cm}}}$$


$$l = \frac{21.9 \text{ cm}}{9.524 \text{ cm}/\lambda} = \underline{\underline{2.2995 \lambda}}$$

$$b) \quad (11.34) \quad Z_{in} = Z_0 \left[ \frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)} \right] \quad \text{where } \beta l = \frac{2\pi}{\lambda} 2.2995 \lambda = 4.599\pi$$

$$Z_{in} = 52 \left[ \frac{(40 - j60) + j52 \tan(4.599\pi)}{52 + j(40 - j60) \tan(4.599\pi)} \right]$$

$$\underline{\underline{Z_{in} = 34.356 + j53.892 \Omega}}$$

c)

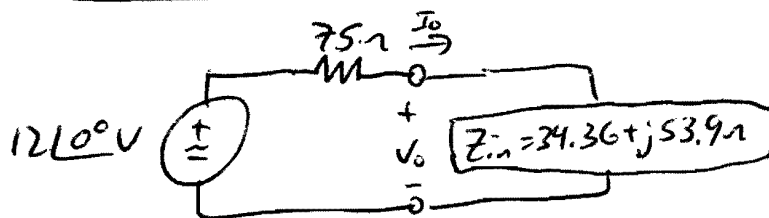

$$I_0 = \frac{12 \angle 0^\circ}{75 + (34.36 + j53.9)} = \underline{\underline{0.09843 \angle -26.235^\circ \text{ A}}}$$

$$\underline{\underline{V_0 = I_0 Z_{in} = 6.291 \angle 31.248^\circ \text{ V}}}$$