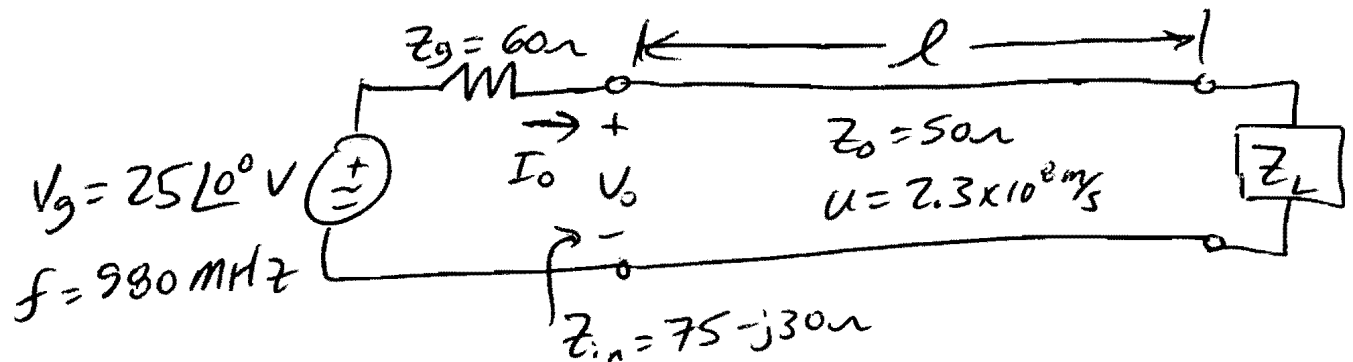



A lossless transmission line ( $Z_0 = 50 \Omega$ ,  $u = 2.3 \times 10^8$  m/s) of some length  $l$  is terminated with an unknown load  $Z_L$ . Using a vector network analyzer (VNA), an input impedance  $Z_{in} = 75 - j30 \Omega$  is measured. The transmission line is connected to a generator operating at 980 MHz with a voltage  $v_g(t) = 25 \cos(\omega t)$  V and impedance  $Z_g = 60 \Omega$ . Draw the transmission line circuit. Then, determine (a) the phase constant  $\beta$  & wavelength  $\lambda$  for the transmission line, (b) the phasor current  $I_0$  & voltage  $V_0$  at the input, (c) the input reflection coefficient  $\Gamma_{in}$ , (d) the phasor forward  $V_0^+$  & backward  $V_0^-$  voltages, (e) the equations for the phasor current  $I_s(z)$  & voltage  $V_s(z)$  along the transmission line, and (f) the time-domain equations for the current  $I(z,t)$  & voltage  $V(z,t)$  along the transmission line.



$$a) \beta = \frac{\omega}{u} = \frac{2\pi(980 \times 10^6)}{2.3 \times 10^8} = \underline{\underline{26.772 \text{ rad/m}}}$$

$$\lambda = \frac{u}{f} = \frac{2.3 \times 10^8}{980 \times 10^6} = \underline{\underline{0.23469 \text{ m}}}$$

b) Equivalent Circuit @ input

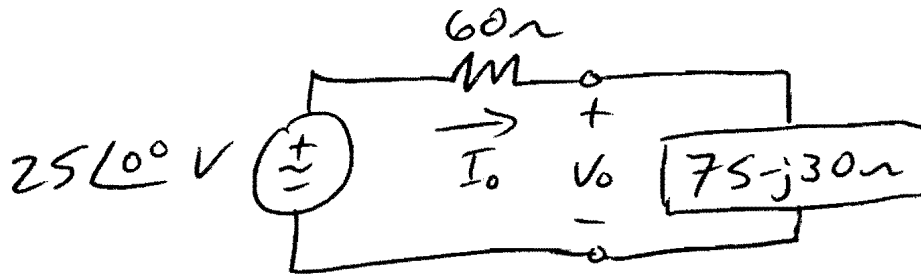

$$I_0 = \frac{25 \angle 0^\circ}{60 + (75 - j30)} = \underline{\underline{0.180775 \angle 12.5288^\circ \text{ A}}}$$

$$V_0 = (25 \angle 0^\circ) \frac{75 - j30}{60 + (75 - j30)} = \underline{\underline{14.6026 \angle -9.273^\circ \text{ V}}}$$

$$c) \Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = \frac{(75 - j30) - 50}{(75 - j30) + 50}$$

$$\Gamma_{in} = 0.3038 \angle -36.699^\circ$$

$$d) \text{ From } V_s(0) = V_0 = V_0^+ e^{-j\beta(0)} (1 + \Gamma_{in}(0))$$

$$\hookrightarrow V_0^+ = \frac{V_0}{1 + \Gamma_{in}} = \frac{14.603 \angle -9.273^\circ}{1 + 0.3038 \angle -36.7^\circ}$$

$$V_0^+ = 11.619 \angle -0.967^\circ \text{ V}$$

$$\Gamma_{in} = \frac{V_0^-}{V_0^+} e^0 \Rightarrow V_0^- = \Gamma_{in} V_0^+ = (0.3038 \angle -36.7^\circ)(11.619 \angle -0.967^\circ)$$

$$V_0^- = 3.5298 \angle -37.6656^\circ \text{ V}$$

$$e) V_s(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$$

$$V_s(z) = (11.619 \angle -0.967^\circ) e^{-j26.772z} + (3.53 \angle -37.7^\circ) e^{j26.772z} \text{ (V)}$$

$$0 \leq z \leq \ell$$

$$I_s(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{j\beta z}$$

$$= \left( \frac{11.619 \angle -0.967^\circ}{50} \right) e^{-j26.772z} - \left( \frac{3.53 \angle -37.7^\circ}{50} \right) e^{j26.772z}$$

$$I_s(z) = (0.2324 \angle -0.967^\circ) e^{-j26.772z} - (0.0706 \angle -37.7^\circ) e^{j26.772z} \text{ (A)}$$

$$0 \leq z \leq \ell$$

$$f) V(z,t) = \text{Re} \{ V_s(z) e^{j\omega t} \}$$

$$V(z,t) = 11.619 \cos(\omega t - 26.772z - 0.967^\circ) + 3.53 \cos(\omega t + 26.772z - 37.7^\circ) \text{ V}$$

---


$$\text{where } \omega = 2\pi(980 \times 10^6) = 6.1575 \times 10^9 \text{ rad/s} \quad 0 \leq z \leq \ell$$

$$I(z,t) = \text{Re} \{ I_s e^{j\omega t} \}$$

$$I(z,t) = 0.2324 \cos(\omega t - 26.772z - 0.967^\circ) - 0.0706 \cos(\omega t + 26.772z - 37.7^\circ) \text{ A}$$

---


$$\text{where } \omega = 6.1575 \times 10^9 \text{ rad/s} \quad 0 \leq z \leq \ell$$