

A twin-lead transmission line, made with perfectly conducting wires of diameter 2 mm and a center-to-center spacing of 12 mm, is in a vacuum chamber. It is connected to a signal generator operating at 105.1 MHz. Find (a) the resistance per-unit-length  $R$ , inductance per-unit-length  $L$ , conductance per-unit-length  $G$  & capacitance-per-unit-length  $C$ , (b) phase constant  $\beta$ , (c) wavelength  $\lambda$ , (d) phase velocity, and (e) characteristic impedance  $Z_0$  of the transmission line.

a) perfectly conducting  $\Rightarrow \sigma_c \rightarrow \infty$ .

From Table 11.1

$$R = \frac{1}{\pi a \sigma_c} \xrightarrow{\sigma_c \rightarrow \infty} = \underline{\underline{0}}$$

$$L = \frac{\mu}{\pi} \cosh^{-1}\left(\frac{d}{2a}\right) = \frac{4\pi \times 10^{-7}}{\pi} \cosh^{-1}\left(\frac{12 \times 10^{-3}}{2 \times 10^{-3}}\right) \quad \leftarrow \text{vacuum}$$

$$\underline{\underline{L = 0.991 \mu\text{H}/\text{m} = 991.1555 \text{ nH}/\text{m}}}$$

$$G = \frac{\pi \sigma \rightarrow 0 \text{ (vacuum)}}{\cosh^{-1}(d/2a)} = \underline{\underline{0}}$$

$$C = \frac{\pi \epsilon}{\cosh^{-1}(d/2a)} = \frac{\pi (8.85412 \times 10^{-12})}{\cosh^{-1}\left(\frac{12 \times 10^{-3}}{2 \times 10^{-3}}\right)}$$

$$\underline{\underline{C = 11.2257 \text{ pF}/\text{m}}}$$

b) (11.21a)  $\beta = \omega \sqrt{LC}$

$$= 2\pi (105.1 \times 10^6) \sqrt{991.2 \times 10^{-9} (11.23 \times 10^{-12})}$$

$$\underline{\underline{\beta = 2.2027 \text{ rad}/\text{m}}}$$

$$c) \quad \lambda = \frac{2\pi}{\beta} = \frac{2\pi}{2.2027} = \underline{\underline{2.8525 \text{ m}}}$$

$$d) \quad u = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{991.2 \times 10^{-9} (11.23 \times 10^{-12})}}$$

(1.21b)

$$\underline{\underline{u = 2.9979 \times 10^8 \text{ m/s}}}$$

$$e) \quad (1.21c) \quad z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{991.2 \times 10^{-9}}{11.23 \times 10^{-12}}}$$

$$\underline{\underline{z_0 = 297.142 \Omega}}$$