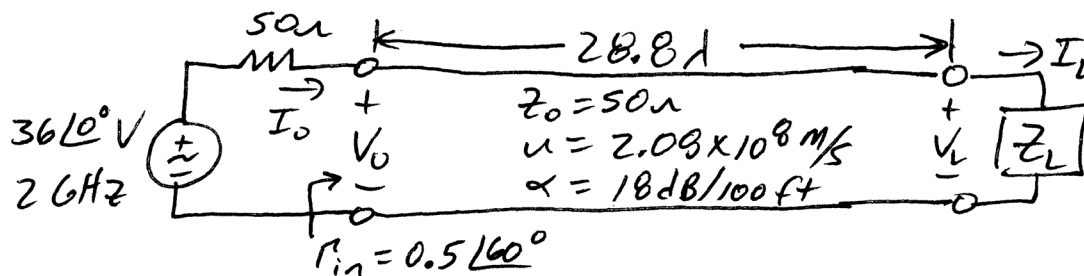


Repeat the previous problem if the transmission line is now assumed to be lossy with a measured attenuation of 18 dB/100 ft.

A lossless transmission line ($Z_0 = 50 \Omega$, $u = 2.08 \times 10^8$ m/s) of length 28.8λ is terminated with an unknown load. Using a vector network analyzer (VNA), an input reflection coefficient of $\Gamma_{in} = 0.50 \angle 60^\circ$ is measured. The transmission line (TL) is then connected to a generator with a voltage $36 \angle 0^\circ$ V and impedance 50Ω operating at 2 GHz. Draw the TL circuit. Then, determine the (a) propagation constant & wavelength, (b) input impedance, (c) phasor current & voltage and time-average power at the input, (d) phasor forward voltage wave amplitude, (e) phasor current & voltage and time-average power at the load.



$$a) \alpha = \frac{18 \text{ dB}}{100 \text{ ft}} \left(\frac{0.3048 \text{ ft}}{\text{m}} \right) \left(\frac{1 \text{ NP}}{20 \log e \text{ dB}} \right) \Rightarrow \alpha = 0.006316 \text{ NP/m}$$

$$(11.21) \beta = \frac{\omega}{u} = \frac{2\pi(2 \times 10^9)}{2.08 \times 10^8} \Rightarrow \beta = 60.4152 \text{ rad/m}$$

$$(11.11) \underline{\underline{\gamma = \alpha + j\beta = 0.006316 + j60.4152 \text{ m}^{-1}}}$$

$$(11.14) \lambda = \frac{2\pi}{\beta} = \frac{2\pi}{60.4152} \Rightarrow \underline{\underline{\lambda = 0.104 \text{ m}}} \text{ (same)}$$

$$b) \text{ Notes } Z_{in} = Z_0 \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} = 50 \frac{1 + 0.5 \angle 60^\circ}{1 - 0.5 \angle 60^\circ}$$

$$\underline{\underline{Z_{in} = 50 + j57.735 \Omega}} \text{ (same)}$$

c) Using Circuits

$$I_0 = \frac{36 \angle 0^\circ}{50 + (50 + j57.735)} \Rightarrow \underline{\underline{I_0 = 0.3118 \angle -30^\circ \text{ A}}}$$

$$V_0 = 36 \angle 0^\circ \frac{50 + j57.735}{50 + 50 + j57.735} \Rightarrow \underline{\underline{V_0 = 23.8118 \angle 19.107^\circ \text{ V}}}$$

$$c) \text{ cont. } P_{in} = \frac{1}{2} \operatorname{Re}\{V_0 I_0^*\} = \frac{1}{2} \operatorname{Re}\{23.8 \angle 19.1^\circ (0.312 \angle +30^\circ)\}$$

$$\underline{\underline{P_{in} = 2.43 \text{ W}}} \quad (\text{same})$$

$$d) (11.27) \quad V_0^+ = \frac{1}{2} [V_0 + I_0 z_0] = \frac{1}{2} [23.8 \angle 19.1^\circ + (0.312 \angle -30^\circ) 50]$$

$$\underline{\underline{V_0^+ = 18 \angle 0^\circ \text{ V}}} \quad (\text{same})$$

$$e) \text{ Notes } \Gamma_L = \Gamma_{in} e^{2\gamma l} = 0.5 \angle 60^\circ e^{2(0.00632 + j60.415)28.9(0.104)}$$

$$\Gamma_L = 0.5193 \angle -84^\circ \quad (\text{bigger})$$

$$I_L = \frac{V_0^+}{z_0} e^{-\gamma l} (1 - \Gamma_L)$$

$$= \frac{18 \angle 0^\circ}{50} e^{-(0.00632 + j60.415)28.9(0.104)} (1 - 0.5193 \angle -84^\circ)$$

$$\underline{\underline{I_L = 0.3806 \angle 100.638^\circ \text{ A}}}$$

$$V_L = V_0^+ e^{-\gamma l} (1 + \Gamma_L)$$

$$= 18 \angle 0^\circ e^{-(0.00632 + j60.415)28.9(0.104)} (1 + 0.5193 \angle -84^\circ)$$

$$\underline{\underline{V_L = 20.7355 \angle 45.902^\circ \text{ V}}}$$

$$P_L = \frac{1}{2} \operatorname{Re}\{V_L I_L^*\} = \frac{1}{2} \operatorname{Re}\{20.74 \angle 45.9^\circ (0.381 \angle -100.6^\circ)\}$$

$$\underline{\underline{P_L = 2.2785 \text{ W}}} \quad (\text{smaller})$$