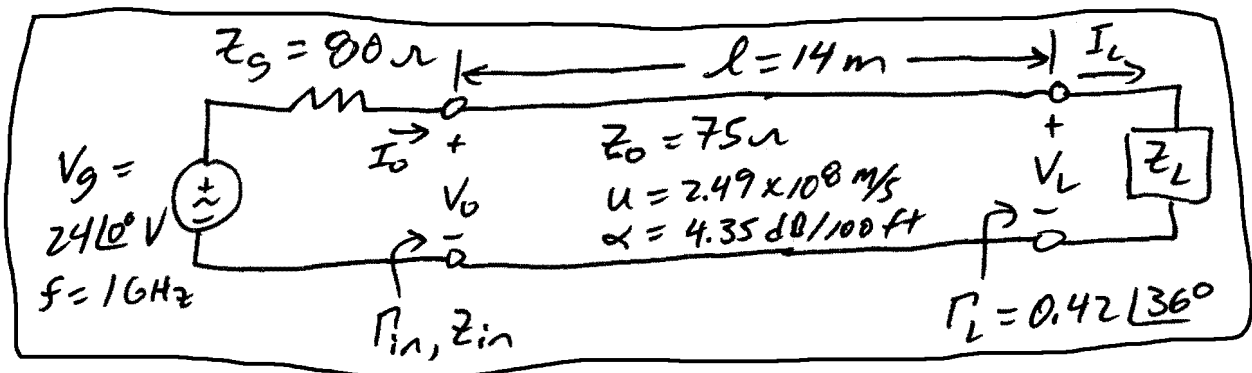


An RG-11 coaxial transmission line ( $Z_0 = 75 \Omega$ ,  $u = 2.49 \times 10^8$  m/s,  $\alpha = 4.35$  dB/100 ft) of length 14 m is terminated with a load. Using a vector network analyzer (VNA), a load reflection coefficient of  $\Gamma_L = 0.42 \angle 36^\circ$  is measured. The transmission line is connected to a generator with  $V_g = 24 \angle 0^\circ$  V and  $Z_g = 80 \Omega$  operating at 1 GHz. First, sketch the transmission line circuit. Then, determine (a) the attenuation (Np/m), phase (rad/m), & propagation constants, (b) SWR & load impedance, (c) input reflection coefficient & impedance, (d) phasor input current & voltage, (e) phasor forward voltage wave amplitude, (f) phasor load current & voltage, and (g) time-average power input and delivered to load.



$$a) \alpha = \frac{4.35 \text{ dB}}{100 \text{ ft}} \left( \frac{3.28084 \text{ ft}}{1 \text{ m}} \right) \left( \frac{1 \text{ Np}}{20 \log e \text{ dB}} \right) \Rightarrow \alpha = 0.016431 \frac{\text{Np}}{\text{m}}$$

$$(11.14) \beta = \frac{\omega}{u} = \frac{2\pi (1 \times 10^9)}{2.49 \times 10^8} \Rightarrow \beta = 25.2337 \frac{\text{rad}}{\text{m}}$$

$$(11.11) \gamma = \alpha + j\beta \Rightarrow \gamma = 0.016431 + j25.2337 \text{ m}^{-1}$$

$$b) (11.38a) \text{SWR} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} = \frac{1 + 0.42}{1 - 0.42} \Rightarrow \text{SWR} = 2.448$$

$$Z_L = Z_0 \frac{1 + \Gamma_L}{1 - \Gamma_L} = 75 \frac{1 + 0.42 \angle 36^\circ}{1 - 0.42 \angle 36^\circ} \Rightarrow Z_L = 124.33 + j74.53 \Omega$$


$$c) (11.37) \Gamma_{in} = \Gamma_L e^{-2\gamma l} = (0.42 \angle 36^\circ) e^{-2(0.0164 + j25.234)14}$$

$$\Gamma_{in} = 0.2651 \angle -125.928^\circ$$

$$c) \text{ cont. } Z_{in} = Z_0 \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} = 75 \frac{1 + 0.2651 \angle -125.93^\circ}{1 - 0.2651 \angle -125.93^\circ}$$

$$\underline{Z_{in} = 50.476 - j23.311 \Omega}$$

d) Use equivalent circuit

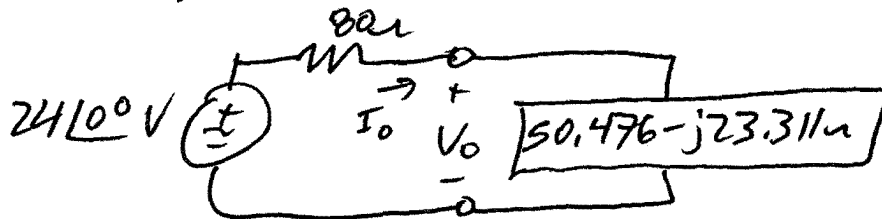

$$I_0 = \frac{24 \angle 0^\circ}{80 + (50.476 - j23.311)} \Rightarrow \underline{I_0 = 0.1811 \angle 10.13^\circ \text{ A}}$$

$$V_0 = 24 \angle 0^\circ \frac{50.476 - j23.311}{80 + (50.476 - j23.311)} \Rightarrow \underline{V_0 = 10.0675 \angle -14.659^\circ \text{ V}}$$

$$e) (11.27a) \quad V_0^+ = \frac{1}{2} [V_0 + I_0 Z_0] = \frac{1}{2} [10.07 \angle -14.66^\circ + 0.1811 \angle 10.13^\circ (75)]$$

$$\underline{V_0^+ = 11.5546 \angle -0.3948^\circ \text{ V}}$$

$$f) \text{ Notes } V_L = V_0^+ e^{-\gamma L} (1 + \Gamma_L) \\ = 11.555 \angle -0.395^\circ e^{-(0.0164 + j25.234)14} (1 + 0.42 \angle 36^\circ)$$

$$\underline{V_L = 12.5066 \angle -70.918^\circ \text{ V}}$$

$$I_L = V_L / Z_L = \frac{12.5066 \angle -70.918^\circ}{124.33 + j74.53} \Rightarrow \underline{I_L = 0.08628 \angle -101.861^\circ \text{ A}}$$

$$g) P_{in} = 0.5 \operatorname{Re}\{V_0 I_0^*\} = 0.5 \operatorname{Re}\{10.07 \angle -14.66^\circ (0.1811 \angle -10.13^\circ)\} \Rightarrow \underline{P_{in} = 0.8275 \text{ W}}$$

$$P_L = 0.5 \operatorname{Re}\{V_L I_L^*\} = 0.5 \operatorname{Re}\{12.51 \angle -70.92^\circ (0.086 \angle 101.9^\circ)\} \Rightarrow \underline{P_L = 0.4627 \text{ W}}$$