



For the lossless transmission line circuit above, the frequency, length, and phase velocity will be left unspecified while $Z_0 = 75 \Omega$ and $Z_L = 56.25 - j75 \Omega$.

1) Normalize and plot load impedance

- Normalize $z_L = Z_L / Z_0 = (56.25 - j75) / 75 \Rightarrow \underline{z_L = 0.75 - j1 \Omega/\Omega}$.
- Plot z_L on Smith chart by finding the intersection of the $r = 0.75$ circle with the $x = -1$ arc.

2) Find load reflection coefficient and VSWR (method 1)

- Set compass to distance between center of Smith chart and z_L . Use “REFL. COEFF. V or I” scale at bottom right to determine $|\Gamma_L| = 0.5$.
- Use compass to draw $|\Gamma| = 0.5$ arc, centered on Smith chart scales, through SWR (VSWR) scale on bottom left. Read **VSWR = 3.1**.
- Use straight-edge to draw radial line from center of Smith chart through z_L and outer rings of Smith chart. Use “ANGLE OF REFLECTION COEFFICIENT IN DEGREES” scale to read $\angle \Gamma_L = -74^\circ$.
- Put magnitude and angle together to get **$\Gamma_L = 0.5 \angle -74^\circ$** . For comparison, the analytic result is $\Gamma_L = 0.5114 \angle -74.29^\circ$.

3) Find VSWR (method 2)

- Draw a circle, centered on Smith chart, through z_L .
- Read value of normalized resistance r where the $|\Gamma| = 0.5$ circle crosses the horizontal/real axis to the right of the origin to get **$r_{max} = \text{VSWR} = 3.1$** .

4) Find load admittance

- Use straight-edge to draw line from edge-to-edge of Smith chart through center of Smith chart and z_L point.

- Where the line intersects the $|\Gamma| = 0.5$ circle on the side opposite to z_L , locate and read/interpolate value of appropriate “g” circle as $g_L = 0.48$.
- Where the line intersects the $|\Gamma| = 0.5$ circle on the side opposite to z_L , locate and read/interpolate value of appropriate “b” arc as $b_L = 0.64$.
- Put together to get normalized load admittance $y_L = 0.48 + j0.64 \text{ S/S}$.
- Find load admittance by dividing y_L by characteristic impedance Z_0 to get $Y_L = y_L / Z_0 = (0.48 + j0.64) / 75 \Rightarrow \underline{Y_L = 0.0064 + j0.0083 \text{ S} = 6.4 + j8.3 \text{ mS}}$.

5) Find/locate voltage and impedance maxima

- The impedance maxima occurs where the $|\Gamma| = 0.5$ circle crosses the real axis to the right of origin. Read/interpolate “r” circles to get $r_{\max} = 3.1$.
- The maximum impedance along the transmission line is found by multiplying r_{\max} w/ Z_0 to get $Z_{\max} = Z_0 z_{\max} = 75(3.1) \Rightarrow \underline{Z_{\max} = 232.5 \Omega}$.
- The voltage maxima along the transmission line occur at r_{\max} . Starting where the radial line through z_L crosses the “WAVELENGTHS TOWARD GENERATOR” scale at 0.352, move toward the generator to the real axis to the right of origin (r_{\max} location) where the scale reads 0.25. The total distance is $(0.5 - 0.352)\lambda + 0.25\lambda = 0.398\lambda$.
- As everything repeats at $\lambda/2$ intervals on lossless TLs, the voltage maxima locations in distance from the load are $\underline{l_{\max} = 0.398\lambda + n\lambda/2}$.

5) Find/locate voltage and impedance minima

- The impedance minima occurs where the $|\Gamma| = 0.5$ circle crosses the real axis to the left of origin. Read/interpolate “r” circles to get $r_{\min} = 0.325$.
- The minimum impedance along the transmission line is found by multiplying r_{\min} w/ Z_0 to get $Z_{\min} = Z_0 z_{\min} = 75(0.325) \Rightarrow \underline{Z_{\min} = 24.375 \Omega}$.
- The voltage minima along the transmission line occur at r_{\min} . Starting where the radial line through z_L crosses the “WAVELENGTHS TOWARD GENERATOR” scale at 0.352, move toward the generator to the real axis to the left of origin (r_{\min} location) where the scale reads 0.5. The total distance is $(0.5 - 0.352)\lambda = 0.148\lambda$.
- As everything repeats at $\lambda/2$ intervals, the voltage minima locations in distance from the load are $\underline{l_{\min} = 0.148\lambda + n\lambda/2}$.

NAME	TITLE	DWG. NO.
SMITH CHART FORM 82B5PR (2-49)	KAY ELECTRIC COMPANY, PINE BROOK, N.J. ©1949 PRINTED IN U.S.A.	DATE

Superseries G.R. Form 5301-7560 N

IMPEDANCE OR ADMITTANCE COORDINATES

$Z_0 = 75 \Omega$

