

We are using an air-dielectric $50\ \Omega$ slotted line to determine an unknown load.

Slotted line with a short circuit termination

Measure adjacent voltage minima at distances $d = 90\text{ cm}$ & $d = 50\text{ cm}$ from load.

1) Find wavelength and frequency of signal

- Adjacent voltage minima are separated by half a wavelength. Therefore, $\lambda/2 = 90 - 50 = 40\text{ cm} \Rightarrow \underline{\lambda = 80\text{ cm}}$.
- The frequency is $f = u/\lambda = 3 \times 10^8 / 0.8 = 375 \times 10^6\text{ Hz} \Rightarrow \underline{f = 375\text{ MHz}}$.

Slotted line with a unknown load termination

With an unknown load attached, we measure $V_{\max} = -5\text{ dBmV}$ (multiple locations) and the voltage minima closest to the load as $V_{\min} = -15\text{ dBmV}$ at $d = 60\text{ cm}$.

1) Find VSWR and magnitude of reflection coefficient along slotted line

- Using $V_{\max} = -5\text{ dBmV} = 20 \log_{10}(V_{\max}/1\text{ mV})$, we calculate the maximum voltage magnitude $V_{\max} = 10^{-5/20} (1\text{ mV}) \Rightarrow \underline{V_{\max} = 0.562\text{ mV}}$.
- Using $V_{\min} = -15\text{ dBmV} = 20 \log_{10}(V_{\min}/1\text{ mV})$, we calculate the minimum voltage magnitude $V_{\min} = 10^{-15/20} (1\text{ mV}) \Rightarrow \underline{V_{\min} = 0.178\text{ mV}}$.
- By definition, the $\text{VSWR} = V_{\max} / V_{\min} = 10^{-5/20} / 10^{-15/20} \Rightarrow \underline{\text{VSWR} = 3.162}$.
- Set compass using “SWR (VSWR)” scale at bottom left of Smith chart.
- Use compass to mark “REFL. COEFF., V OR I” scale on bottom right of Smith chart. Read $|\Gamma| = \underline{0.52}$.

2) Find unknown load impedance

- We know that voltage minima occur at the r_{\min} point on circle of constant $|\Gamma|$. Using compass, draw a circle of $|\Gamma| = 0.52$. Where the circle crosses the horizontal axis to left of origin, mark V_{\min} point and read $r_{\min} = 0.31\ \Omega/\Omega$.
- The voltage minima closest to the unknown load is at $d = 60\text{ cm}$. Moving toward the generator, the first location of a voltage minimum for the short circuit termination was $d = 90\text{ cm}$. The distance toward the load from the V_{\min}/r_{\min} point is then $l = |60 - 90| = 30\text{ cm}$ or $l/\lambda = 30/80 \Rightarrow \underline{l/\lambda = 0.375}$.
- As the horizontal axis for V_{\min}/r_{\min} point is at 0 on the “WAVELENGTHS TOWARD LOAD” scale, draw a radial line from the center of the Smith chart through 0.375 on the “WAVELENGTHS TOWARD LOAD” scale.
- Where the radial line intersects the $|\Gamma| = 0.52$ circle, read/interpolate values of normalized load resistance and reactance as $\underline{r_L = 0.58}$ and $\underline{x_L = 0.82}$.

- Put together to get normalized load impedance $z_L = \mathbf{0.58 + j0.82 \Omega/\Omega}$.
- Find load impedance by multiplying z_L by characteristic impedance Z_0 to get $Z_L = z_L Z_0 = (0.58 + j0.82) 50 \Rightarrow \mathbf{Z_L = 29 + j41 \Omega}$.

