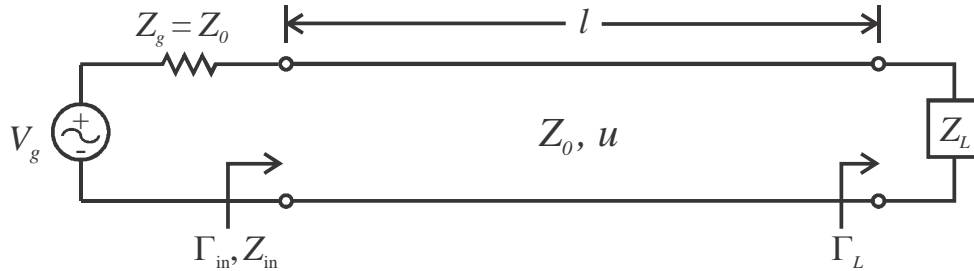


### Matching load using a discrete series components


- Assume we have a source matched to the characteristic impedance  $Z_0$  of the transmission line.




- Therefore, we are seeking to match the load  $Z_L$  to  $Z_0$  as well, i.e., we want  $Z_{in} = Z_0$ .
- To avoid power losses, we will only use purely reactive components for matching.

#### Steps

- 1) Calculate  $z_L = Z_L/Z_0$  and plot on Smith chart.
- 2) Draw circle, centered on Smith chart, through  $z_L$  point. This circle of constant  $|\Gamma|$  includes the locus of all possible  $z_{in}$  (and  $y_{in}$ ) along the transmission line with this load.
- 3) There are two points (i.e., match point points) on the circle of constant  $|\Gamma|$  that intersect the circle where the normalized resistance  $r$  is equal to one, i.e.,  $z_{m,i} = 1 \pm jx_m$ . In terms of input impedance this is where  $Z_{m,i} = Z_0 \pm jX_m$ .
- 4) Find the distance  $d_i$  from  $z_L$  to the match points using the “WAVELENGTHS TOWARD GENERATOR” scale.

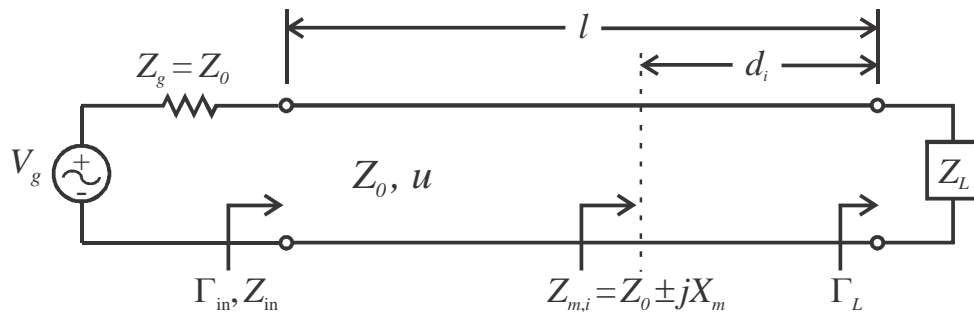


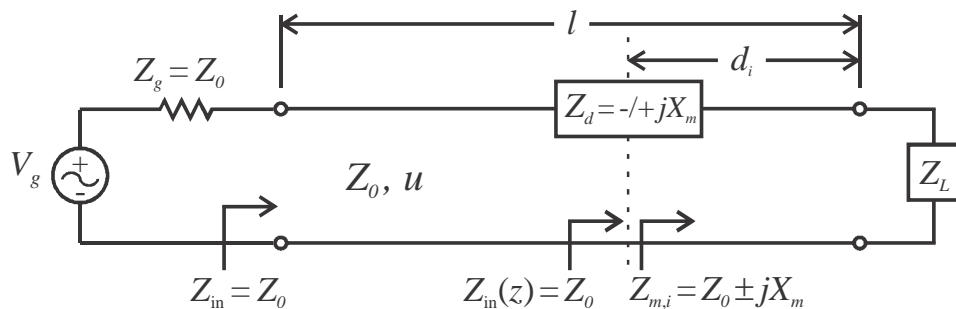- 5) Select one of the match points and add a discrete component (i.e., capacitor or inductor) in series with a reactance  $Z_m = \mp jX_m$ . Remember  $Z_{cap} = -j/\omega C$  and  $Z_{ind} = j\omega L$ .
- 6) Now, everywhere toward the generator from this location will see a normalized input impedance  $z_{in} = (1 \pm jx_m) \mp jx_m = 1$ , i.e.,  $Z_{in} = Z_0$ .


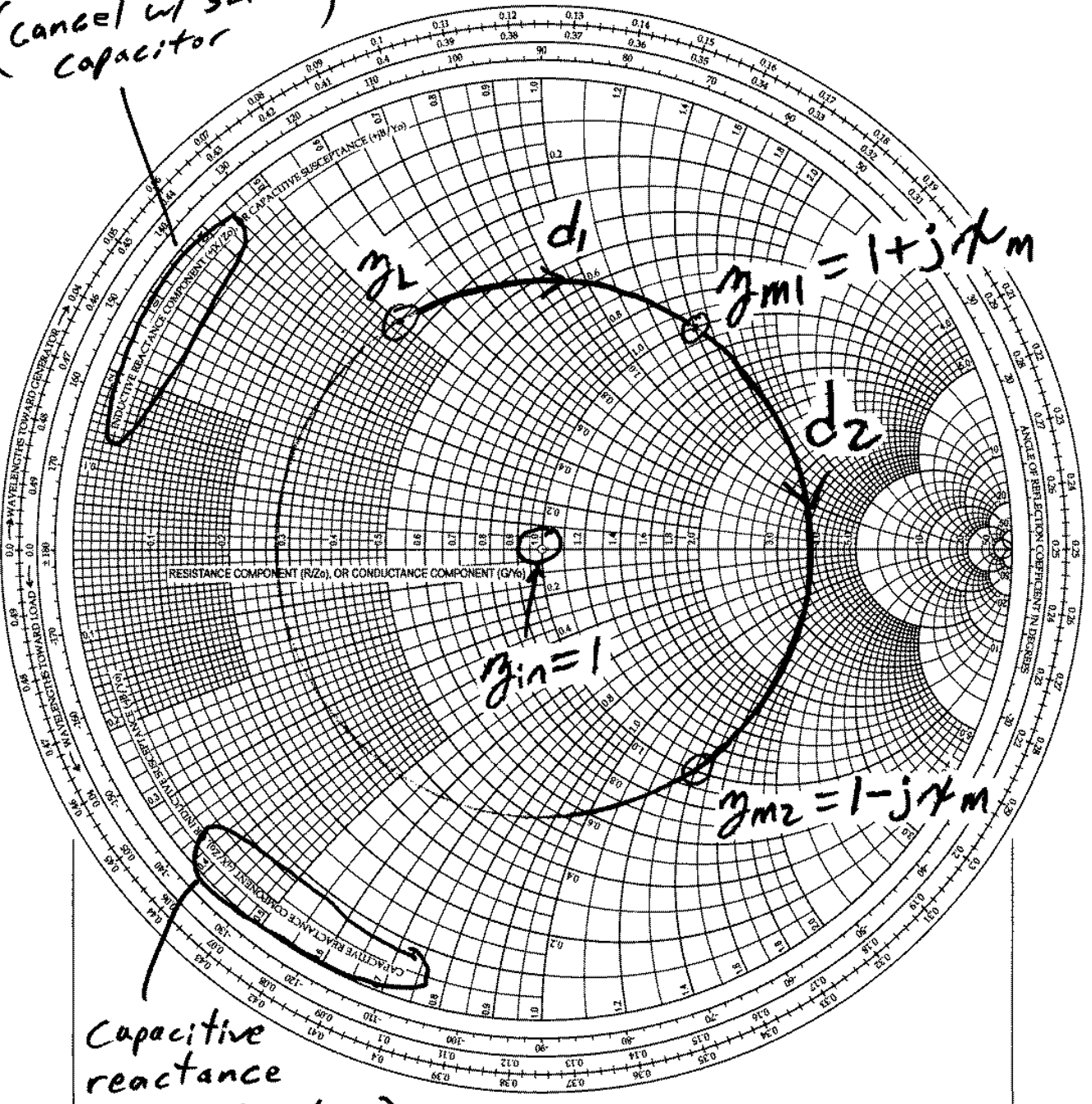
### Simple Smith Chart


Inductive Reactance  
(Cancel w/ series capacitor)



Capacitive reactance  
(Cancel w/ series inductor)

RADIALLY SCALED PARAMETERS

SWR (VSWR)  
S.W.R. (dB)

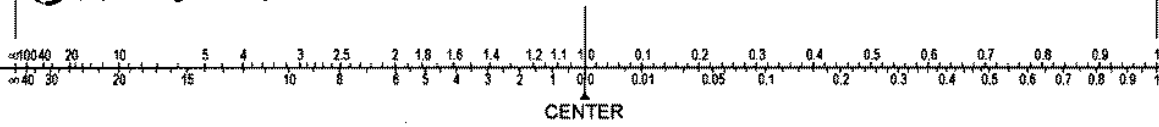

REFL. COEFF. V or I  
REFL. COEFF. P