


**EE 382 Lossy Transmission Line Example Problem**

$$d := 4 \cdot 10^{-2} \text{ m} \quad a := \frac{0.5 \cdot 10^{-2}}{2} \text{ m}$$

$$f := 500 \cdot 10^6 \text{ Hz} \quad \omega := 2 \cdot \pi \cdot f$$

$$\sigma_{\text{cu}} := 5.8 \cdot 10^7 \text{ S/m} \quad \sigma_{\text{ins}} := 0.001 \text{ S/m}$$
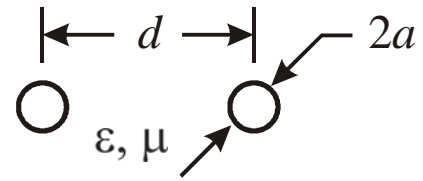
$$\epsilon_0 := 8.8541878 \cdot 10^{-12} \text{ F/m} \quad \epsilon_{\text{r,ins}} := 1.9$$



$$\mu_0 := 4 \cdot \pi \cdot 10^{-7} \text{ H/m}$$

**Calculate lossy transmission line parameters**

$$\delta := \frac{1}{\sqrt{\pi \cdot f \cdot \mu_0 \cdot \sigma_{\text{cu}}}} \quad \delta = 2.95543 \times 10^{-6} \text{ m, skin depth}$$

$$R := \frac{1}{\pi \cdot a \cdot \delta \cdot \sigma_{\text{cu}}} \quad R = 0.74278 \text{ } \Omega/\text{m, resistance-per-unit-length}$$

$$L := \frac{\mu_0}{\pi} \cdot \text{acosh}\left(\frac{d}{2 \cdot a}\right) \quad L = 1.10746 \times 10^{-6} \text{ H/m, inductance-per-unit-length}$$

$$G := \frac{\pi \cdot \sigma_{\text{ins}}}{\text{acosh}\left(\frac{d}{2 \cdot a}\right)} \quad G = 1.1347 \times 10^{-3} \text{ S/m, conductance-per-unit-length}$$

$$C := \frac{\pi \cdot \epsilon_{\text{r,ins}} \cdot \epsilon_0}{\text{acosh}\left(\frac{d}{2 \cdot a}\right)} \quad C = 1.9089 \times 10^{-11} \text{ F/m, capacitance-per-unit-length}$$


$$\gamma := \sqrt{(R + j \cdot \omega \cdot L) \cdot (G + j \cdot \omega \cdot C)} \quad \gamma = 0.13819 + 14.44525i \text{ 1/m, propagation constant}$$

$$\alpha := \text{Re}(\gamma) \quad \alpha = 0.1382 \text{ np/m, atten. constant or } 20 \log(e^\alpha) = 1.2 \text{ dB/m} \quad \beta := \text{Im}(\gamma)$$

$$\beta = 14.445 \text{ rad/m, phase constant} \quad u := \frac{\omega}{\beta} \quad u = 2.17483 \times 10^8 \text{ m/s, phase velocity}$$

$$\lambda := \frac{2 \cdot \pi}{\beta} \quad \lambda = 0.43497 \text{ m, wavelength}$$

$$Z_0 := \sqrt{\frac{(R + j \cdot \omega \cdot L)}{(G + j \cdot \omega \cdot C)}} \quad Z_0 = 240.8328 + 2.2525i \text{ } \Omega, \text{ characteristic impedance}$$

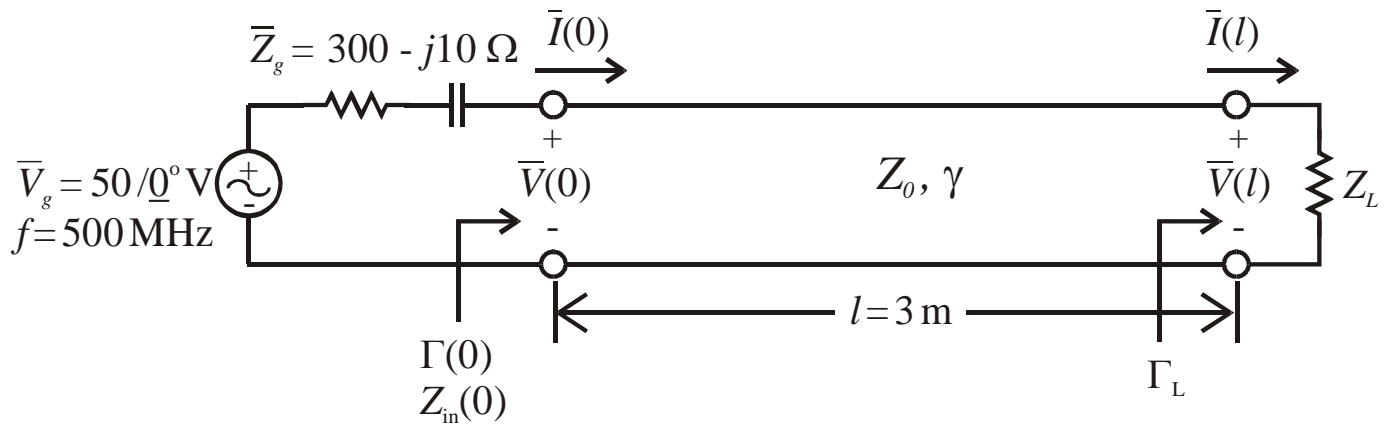**Lossy transmission line circuit**

$$Z_g := 300 - j \cdot 10 \quad \Omega \quad Z_L := 300 + j \cdot 0 \quad \Omega \quad l := 3.0 \quad \text{m} \quad V_g := 50 \quad \text{V}$$

$$\Gamma_L := \frac{Z_L - Z_0}{Z_L + Z_0} \quad \Gamma_g := \frac{Z_g - Z_0}{Z_g + Z_0}$$

$$\Gamma_L = 0.1094 - 4.6204i \times 10^{-3} \quad |\Gamma_L| = 0.1095 \quad \arg(\Gamma_L) \cdot \frac{180}{\pi} = -2.4188 \quad \text{deg}$$

$$\Gamma_g = 0.1097 - 0.0211i \quad |\Gamma_g| = 0.1117 \quad \arg(\Gamma_g) \cdot \frac{180}{\pi} = -10.8789 \quad \text{deg}$$

$$\Gamma_0 := \Gamma_L \cdot e^{-2 \cdot \gamma \cdot l} \quad Z_{in0} := Z_0 \cdot \frac{(1 + \Gamma_0)}{(1 - \Gamma_0)}$$

$$\Gamma_0 = 0.015 + 0.0454i \quad |\Gamma_0| = 0.0478 \quad \arg(\Gamma_0) \cdot \frac{180}{\pi} = 71.6711 \quad \text{deg}$$


$$Z_{in0} = 246.9354 + 24.7814i \quad \Omega \quad |Z_{in0}| = 248.1758 \quad \Omega \quad \arg(Z_{in0}) \cdot \frac{180}{\pi} = 5.73 \quad \text{deg}$$

**OR**

$$Z_{in} := Z_0 \cdot \frac{(Z_L + Z_0 \cdot \tanh(\gamma \cdot l))}{Z_0 + Z_L \cdot \tanh(\gamma \cdot l)} \quad Z_{in} = 246.9354 + 24.7814i \quad \Omega \quad \text{SAME!}$$

**Notice how  $Z_{in}$  is converging toward  $Z_0 = 240.83 + j2.25$  Ohms**

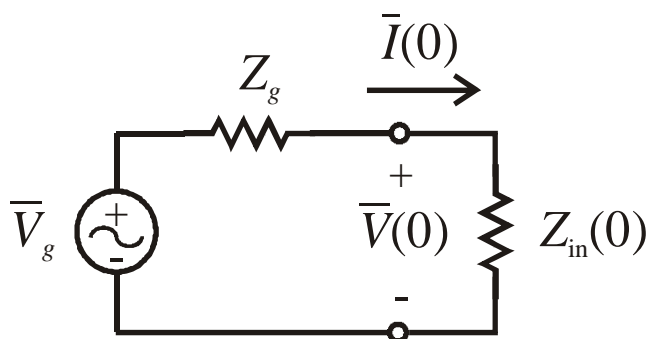**Now, we can draw the equivalent circuit seen by the generator.**



**Use simple circuit theory to calculate the input voltage, current, and power.**

$$I_0 := \frac{V_g}{Z_g + Z_{in}} \quad |I_0| = 0.0914 \text{ A} \quad \arg(I_0) \cdot \frac{180}{\pi} = -1.5481 \text{ deg}$$

$$V_0 := \frac{V_g \cdot Z_{in}}{Z_g + Z_{in}} \quad |V_0| = 22.6796 \text{ V} \quad \arg(V_0) \cdot \frac{180}{\pi} = 4.1827 \text{ deg}$$

$$P_0 := 0.5 \cdot \text{Re}(V_0 \cdot \bar{I}_0) \quad P_0 = 1.03111 \text{ W} \quad \text{Power into transmission line.}$$

**Next, we'll find how much power makes it to the load and how much is lost.**

$$I_L := \frac{V_g}{Z_0 + Z_g} \cdot e^{-\gamma \cdot l} \cdot \frac{1 - \Gamma_L}{1 - \Gamma_g \cdot \Gamma_L \cdot e^{-2\gamma \cdot l}} \quad |I_L| = 0.0545 \text{ A} \quad \arg(I_L) \cdot \frac{180}{\pi} = 38.431 \text{ deg}$$

$$V_L := \frac{V_g \cdot Z_0}{Z_0 + Z_g} \cdot e^{-\gamma \cdot l} \cdot \frac{1 + \Gamma_L}{1 - \Gamma_g \cdot \Gamma_L \cdot e^{-2\gamma \cdot l}} \quad |V_L| = 16.359 \text{ V} \quad \arg(V_L) \cdot \frac{180}{\pi} = 38.431 \text{ deg}$$

$$P_L := 0.5 \cdot \text{Re}(V_L \cdot \bar{I}_L) \quad P_L = 0.44604 \text{ W} \quad \text{Power delivered to load.}$$

$$P_{\text{lost}} := P_0 - P_L \quad P_{\text{lost}} = 0.58507 \text{ W} \quad \text{Power lost in transmission line.}$$

**Note that over half the power was lost in the transmission line.**

**OR, alternate methods to finding load current, voltage, & power**

$$V0\_fwd := \frac{V0}{1 + \Gamma0} \quad V0\_fwd = 22.31261 + 0.63268i \text{ V}$$

$$V0\_fwd2 := 0.5 \cdot (V0 + Z0 \cdot I0) \quad V0\_fwd2 = 22.31261 + 0.63268i \text{ V}$$

$$V0\_fwd3 := 0.5 \cdot (VL + Z0 \cdot IL) \cdot e^{\gamma \cdot l} \quad V0\_fwd3 = 22.31261 + 0.63268i \text{ V}$$

**ALL  
THE  
SAME!!**

$$\boxed{|V0\_fwd| = 22.3216} \text{ V}$$

$$\boxed{\arg(V0\_fwd) \cdot \frac{180}{\pi} = 1.6242} \text{ deg}$$

**Knowing the magnitude of the forward traveling wave, we can now use the phasor voltage and current equations, evaluated at  $z = l$ .**

$$IL2 := \frac{V0\_fwd}{Z0} \cdot e^{-\gamma \cdot l} \cdot (1 - \Gamma L) \quad \boxed{|IL2| = 0.0545} \text{ A} \quad \boxed{\arg(IL2) \cdot \frac{180}{\pi} = 38.431} \text{ deg}$$

$$VL2 := V0\_fwd \cdot e^{-\gamma \cdot l} \cdot (1 + \Gamma L) \quad \boxed{|VL2| = 16.359} \text{ V} \quad \boxed{\arg(VL2) \cdot \frac{180}{\pi} = 38.431} \text{ deg}$$

$$PL2 := 0.5 \cdot \text{Re}(VL2 \cdot \overline{IL2}) \quad \boxed{PL2 = 0.44604} \text{ W} \quad \textbf{SAME AS BEFORE!!}$$