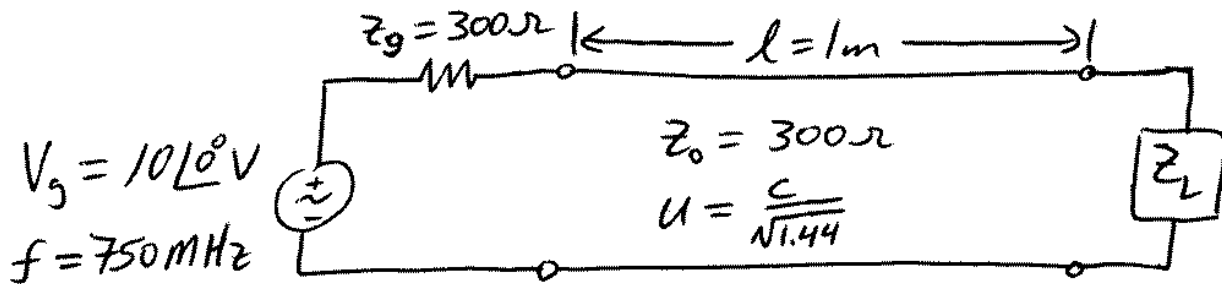


Matching load using a discrete parallel capacitor

Using a discrete capacitor placed in parallel w/ the transmission line, match the load $z_L = 150 - j600 \Omega$ to the transmission line and generator. Place the capacitor as close to the load as possible. How much power is delivered to the load?

$$y_L = \frac{z_L}{z_0} = \frac{150 - j600}{300} = 0.5 - j2 \text{ } \Omega^{-1}$$

→ plot y_L on Smith Chart

→ draw circle, centered on Smith Chart, thru y_L

→ rotate $1/4$ from y_L to $y_L = 0.11765 + j0.4706 \text{ } \Omega^{-1}$


→ Note location of match points (points where $|r|$ circle intersects $g = 1 \text{ } \Omega^{-1}$ circle).

$$y_{m1} = 1 + j3 \text{ } \Omega^{-1} \leftarrow \text{capacitive susceptance}$$

$$y_{m2} = 1 - j3 \text{ } \Omega^{-1} \leftarrow \text{inductive susceptance}$$

Simple Smith Chart

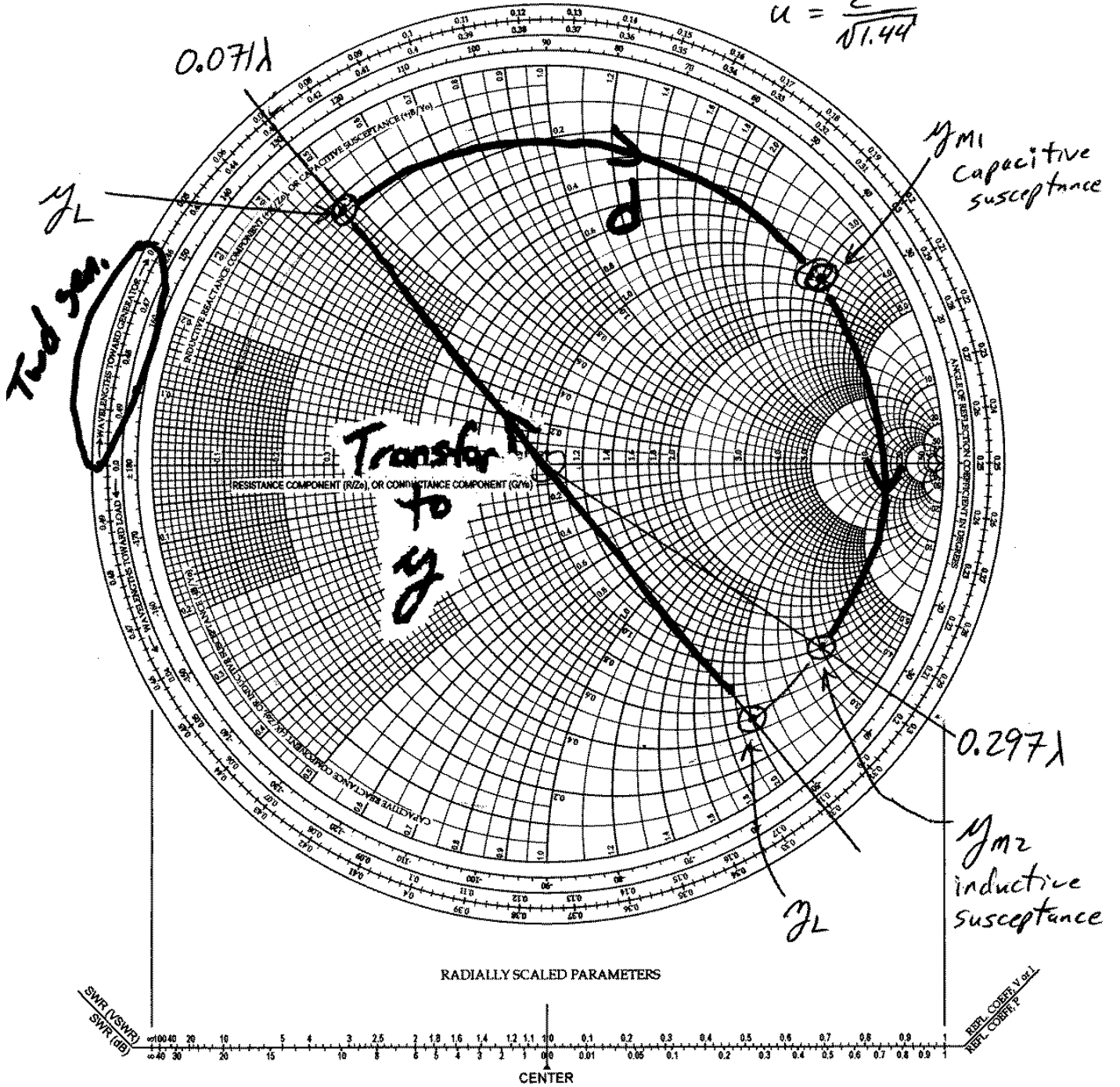$Z_0 = 300 \Omega$
 $f = 750 \text{ MHz}$
 $u = \frac{c}{\sqrt{1.44}}$



Normalized capacitive
susceptance $y_{cap} = (j\omega C) Z_0$

To use a discrete capacitor for matching, select
match point #2 and require

$$y_{m2} + y_{cap} = 1$$

$$(1 - j3) + j(2\pi)(750 \times 10^6) C (300) = 1$$

$$\hookrightarrow C = \frac{3}{2\pi (750 \times 10^6) (300)}$$


$$\underline{\underline{C = 2.122 \text{ pF}}}$$

Distance from load to y_{m2} location closest
to load? \leftarrow from "Toward Generator"
Scale

$$d = 0.297 \lambda - 0.071 \lambda = \underline{\underline{0.226 \lambda}}$$

$$d = 0.226 \left(\frac{3 \times 10^8 / \sqrt{1.44}}{750 \times 10^6} \right) = 0.0753 \bar{m}$$
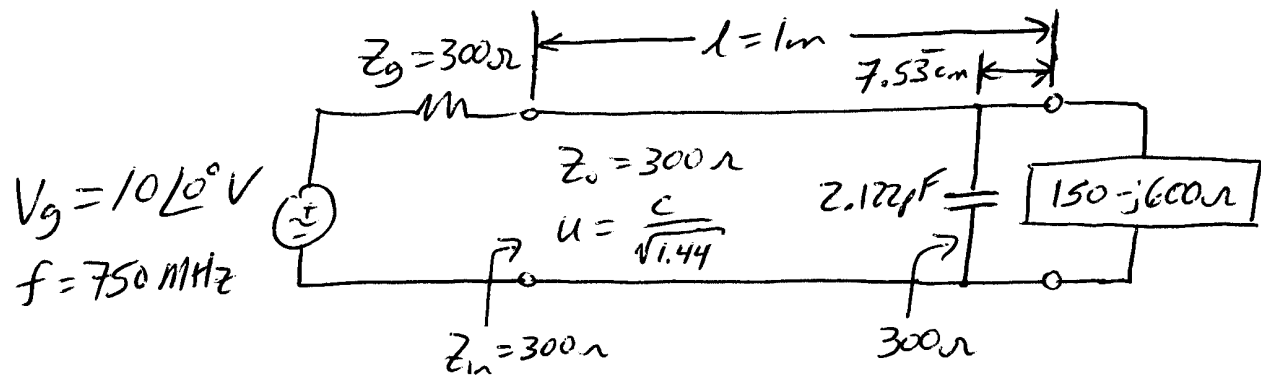
$$\underline{\underline{d = 7.53 \text{ cm}}}$$



$$I(0) = \frac{V_g}{Z_g + Z_{in}} = \frac{10 \angle 0^\circ}{300 + 300} = \frac{1}{60} \angle 0^\circ \text{ A}$$

$$P_{in} = \frac{1}{2} |I(0)|^2 R_{in} = \frac{1}{2} \left(\frac{1}{60}\right)^2 300 = \frac{|V_g|^2}{8 R_g}$$

$$P_{in} = \underline{41.6 \text{ mW}}$$

Since capacitors do not absorb real power and the transmission line is lossless,

$$P_L = P_{in} = \underline{41.6 \text{ mW}} \quad \text{w/ matching capacitor}$$

For comparison, w/out matching capacitor,

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{(150 - j600) - 300}{(150 - j600) + 300} = 0.8246 \angle -50.9^\circ$$

$$\Gamma_{in} = \Gamma_L e^{-j2\beta l} = (0.8246 \angle -50.9^\circ) e^{-j2 \frac{2\pi(750 \times 10^6)(1)}{c/\sqrt{1.44}}} = 0.8246 \angle -52.42^\circ$$

$$Z_{in} = Z_0 \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} = 300 \frac{1 + 0.825 \angle -52.4^\circ}{1 - 0.825 \angle -52.4^\circ} = 142.4 - j581.62 \Omega$$

$$I_0 = \frac{V_g}{Z_{in} + Z_g} = \frac{10 \angle 0^\circ \text{ V}}{142.4 - j581.6 + 300} = 0.01368455 \angle 52.74^\circ \text{ A}$$

$$P_{in, noc} = P_{L, noc} = \frac{1}{2} (0.01368)^2 142.4 = \underline{13.3 \text{ mW}} \quad \leftarrow 32\% \text{ of matched } P_L$$