

Matching load using a shorted single stub

Match a load of $Z_L = 30 - j75 \Omega$ connected to a 75Ω generator operating at 900 MHz using a lossless transmission line ($u = 2.1 \times 10^8$ m/s, 75Ω) and a **short circuit** single-stub tuner made of the same transmission line.

$$\lambda = \frac{u}{f} = 23.3 \text{ cm}$$

$$\gamma_L = \frac{30 - j75}{75} = 0.4 - j1 \quad \frac{S}{\Omega}$$

⇒ Plot on Smith Chart

⇒ Rotate 180° to get γ_L

$$\text{or use } \gamma_L = \frac{1}{\gamma_L} = 0.344 + j0.862 \frac{S}{\Omega}$$

⇒ Draw circle through $\gamma_L + \gamma_L$

⇒ Read off match points

$$\gamma_{m1} = 1 + j1.85 \frac{S}{\Omega} \quad \gamma_{m2} = 1 - j1.85 \frac{S}{\Omega}$$

⇒ Selecting γ_{m1} $\lambda_1 = 0.1835\lambda - 0.1195\lambda$

$$\underline{\underline{\lambda_1 = 0.064\lambda}}$$

⇒ Use short circuit terminated stub of length

$$\gamma_{sc} = \infty \quad \gamma_{in, stub} = -j1.85 \frac{S}{\Omega}$$


$$d_1 = 0.329\lambda - 0.25\lambda$$


$$\underline{\underline{d_1 = 0.079\lambda}}$$

Simple Smith Chart

$Z_0 = 75 \Omega$
 $f = 900 \text{ MHz}$
 $u = 2.1 \times 10^8 \text{ m/s}$

$l_1 = 0.064 \lambda$

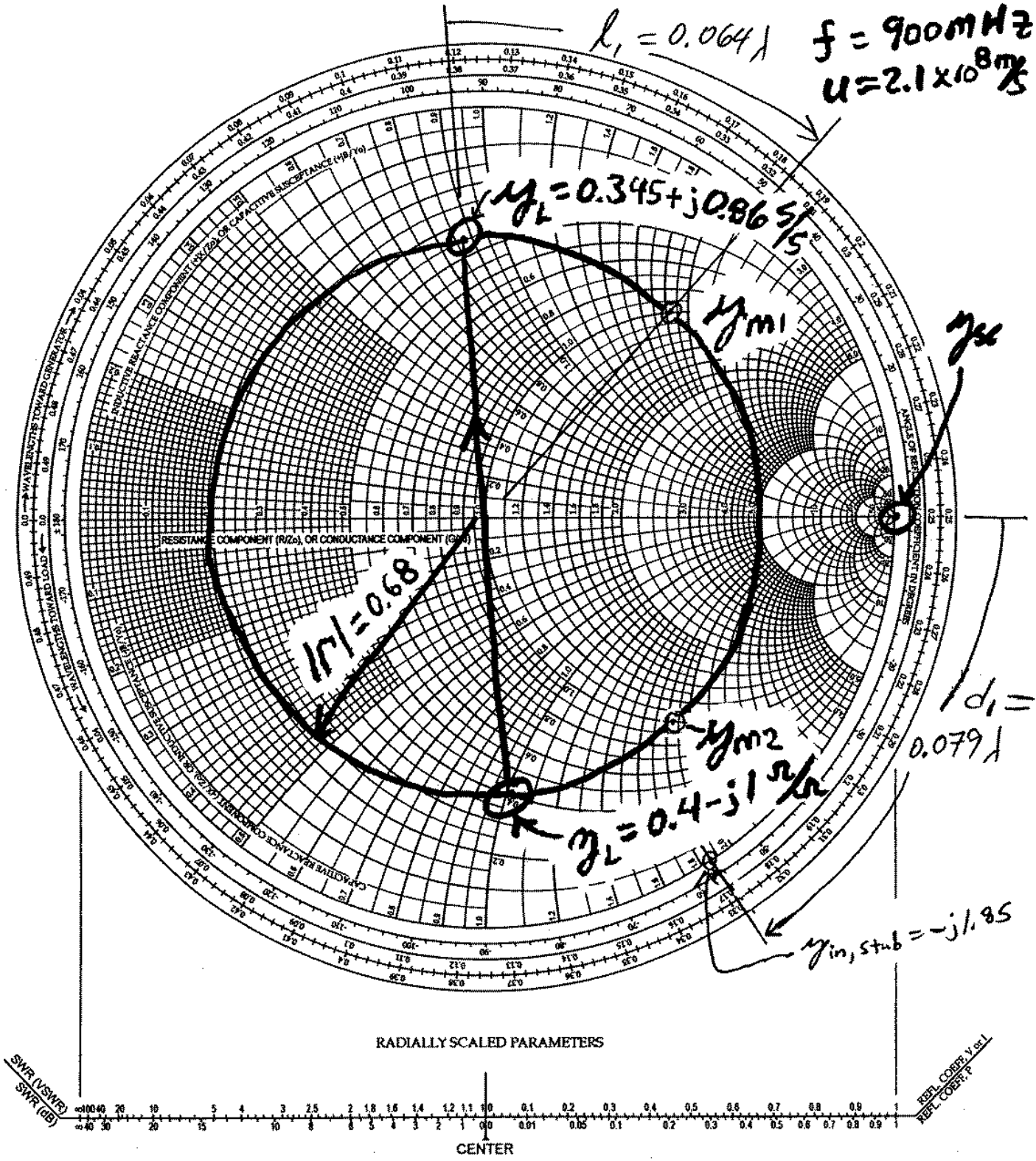

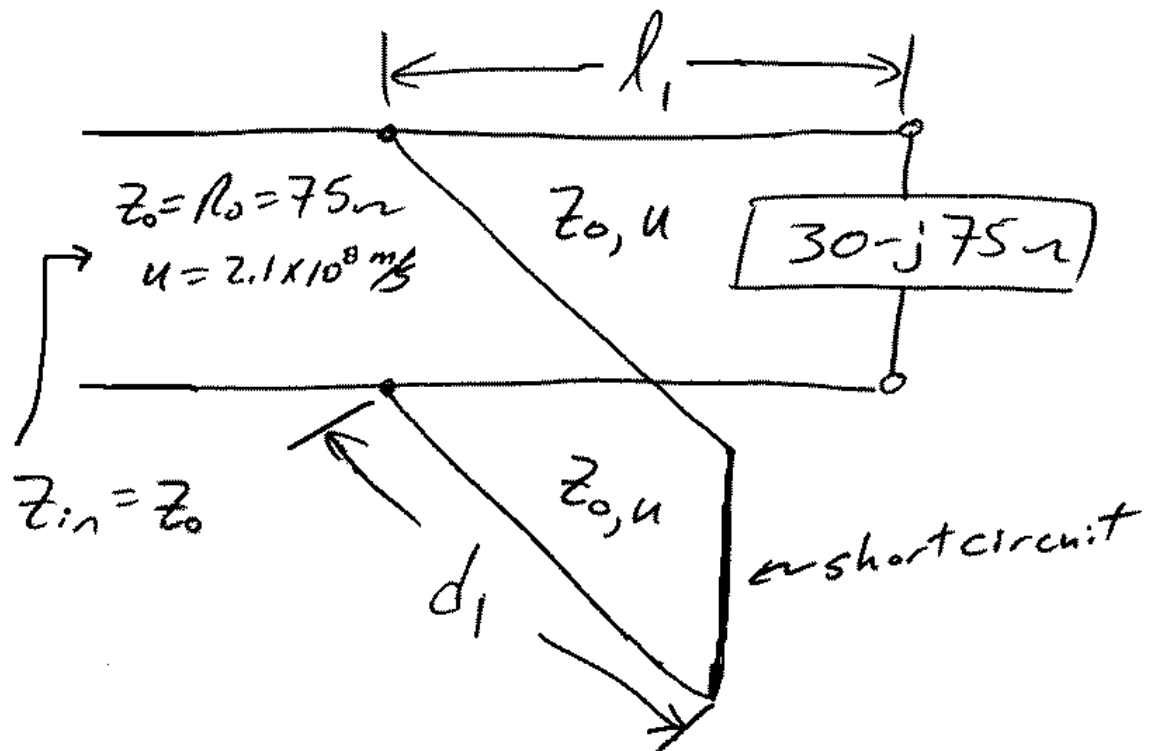

where

$$l_1 = 0.064 \lambda = \underline{\underline{1.4933 \text{ cm}}}$$

or

$$l_1 = 0.064 \lambda + n \frac{\lambda}{2} = \underline{\underline{1.4933 + n 11.666 \text{ cm}}}$$

$$d_1 = 0.079 \lambda = \underline{\underline{1.843 \text{ cm}}}$$

or

$$d_1 = 0.079 \lambda + n \frac{\lambda}{2} = \underline{\underline{1.843 + n 11.666 \text{ cm}}}$$