

$$z_o = 75 \Omega, \quad u = 1.5 \times 10^8 \text{ m/s}, \quad l = 600 \text{ m}$$

$$\Gamma_L = \frac{R_L - z_o}{R_L + z_o} = \frac{225 - 75}{225 + 75} = \underline{0.5}$$


$$\Gamma_g = \frac{z_g - z_o}{z_g + z_o} = \frac{25 - 75}{25 + 75} = \underline{-0.5}$$

$$T = \frac{l}{u} = \frac{600 \text{ m}}{1.5 \times 10^8 \text{ m/s}} = \underline{4 \mu\text{s}}$$

$$\text{Spatial length of pulse} = (1 \mu\text{s})(1.5 \times 10^8 \text{ m/s}) = \underline{150 \text{ m}}$$

a) At $t = 0^+$, the generator turns on and "sees" the generator and transmission line impedances.

Equiv. Ckt. ($t = 0^+$)

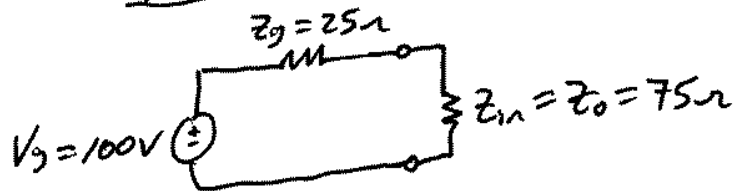


Still has same shape & PW as $V_g(t)$

$$V_{\text{init}} = V_1^+ = V_g \frac{z_{in}}{z_g + z_{in}} = 100 \left(\frac{75}{25 + 75} \right) = \underline{75 \text{ V}}$$


$$I_{\text{init}} = I_1^+ = \frac{V_g}{z_g + z_{in}} = \frac{100 \text{ V}}{(25 + 75) \Omega} = \underline{1 \text{ A}}$$

Now, we'll follow the pulse (voltage only) as it propagates on the transmission line.

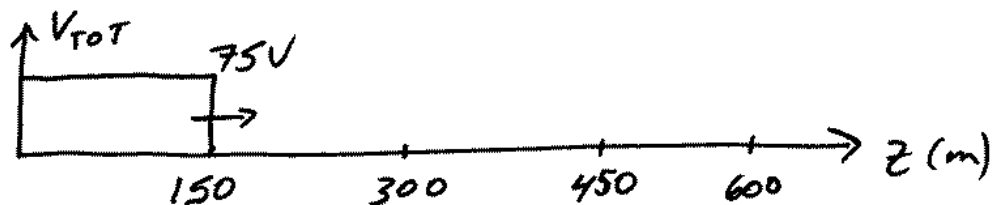b) At $t = 1 \mu s$, leading edge at $z = 1 \mu s (1.5 \times 10^8) = 150 m$



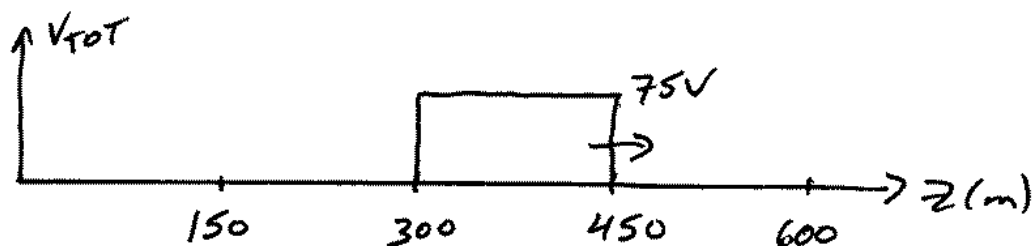c) At $t = 3 \mu s$, leading edge at $z = 3 \mu s (1.5 \times 10^8) = 450 m$




d) At $t = 4 \mu s = T$, the leading edge of the pulse arrives at the load and is partially absorbed/reflected

$$V_1^- = V_1^+ \Gamma_L = 75(0.5) = \underline{37.5 V} \leftarrow \begin{array}{l} \text{still same} \\ \text{shape \& duration} \end{array}$$

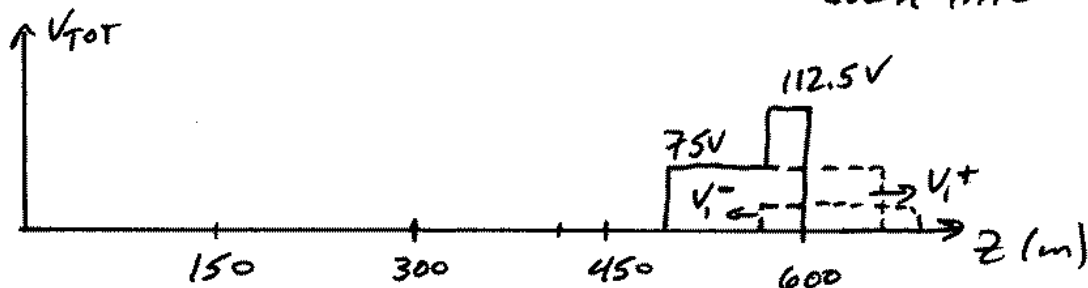
e) At $t = 4.25 \mu s$, V_1^+ and V_1^- are partially overlapped

$$\text{overlap: } V_{TOT} = V_1^+ + V_1^- = 75 + 37.5 = 112.5 V$$

leading edge $4.25 \mu s (1.5 \times 10^8) = 637.5 m \rightarrow 37.5 m$ back down line



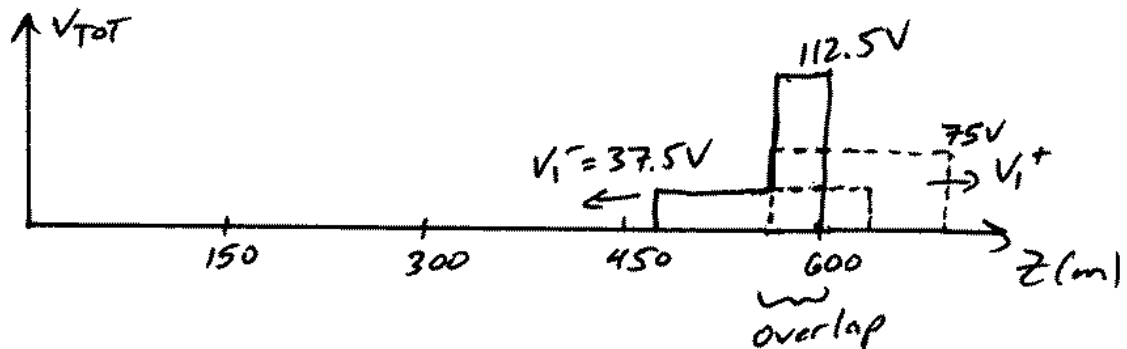- f) At $t = 4.75 \mu\text{s}$, V_1^+ and V_1^- are still partially overlapped. Leading edge is at $4.75 \mu\text{s} (1.5 \times 10^8 \text{ m/s}) = 712.5 \text{ m} \rightarrow 112.5 \text{ m}$ back down the line from the load




- g) At $t = 8 \mu\text{s}^+ = 2T^+$, the pulse initially reflected from the load (V_1^-) has its leading edge arrives at the generator and is partially reflected


$$V_2^+ = V_1^- \Gamma_g = 37.5(-0.5) = \underline{-18.75 \text{ V}}$$

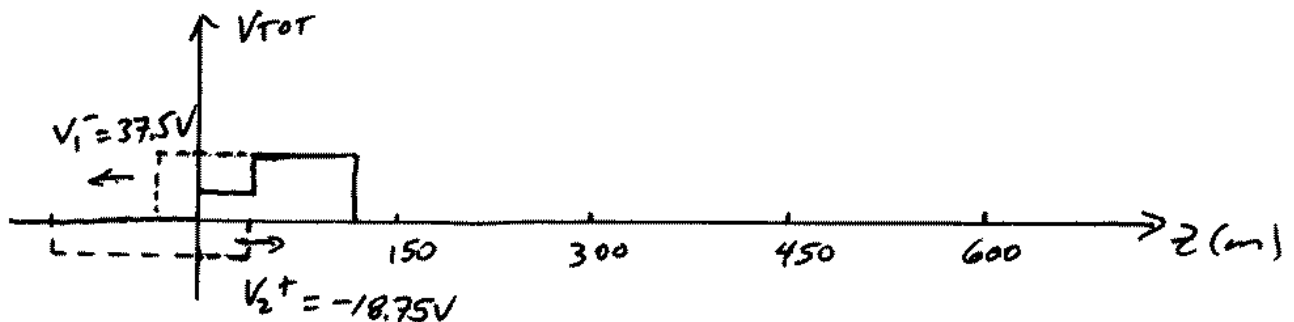- h) At $t = 8.25 \mu\text{s}$, the pulses V_1^- and V_2^+ are partially overlapped

$$V_{\text{TOT}} = V_1^- + V_2^+ = 37.5 + (-18.75) = \underline{18.75 \text{ V}}$$



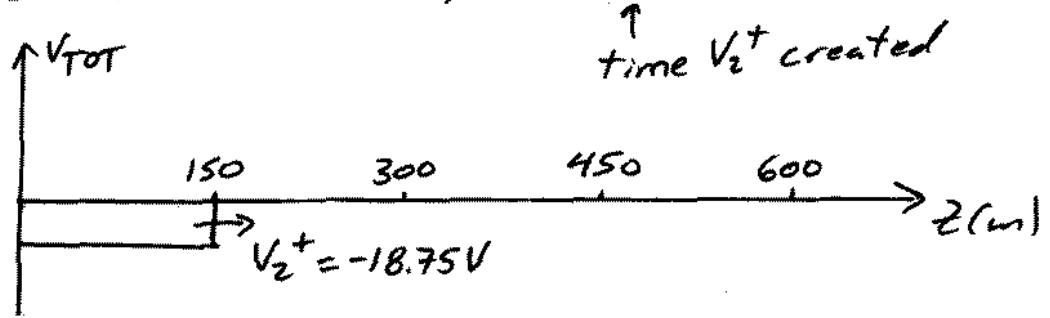i) At $t = 9 \mu s$, only the pulse reflected from the generator (V_2^+) remains, its leading edge is at $(9 \mu s - 8 \mu s)(1.5 \times 10^8) = 150 m$



→ Repeat steps c) – h)

Note: * So far, the voltage has been plotted as a function of position (i.e., versus z) at selected snapshots in time.

* However, the reality is that an oscilloscope measures total voltage as a function of time (i.e., versus t) at a fixed location.

For example, if I had an oscilloscope attached at the load ($z = l = 600 m$), I would see:

