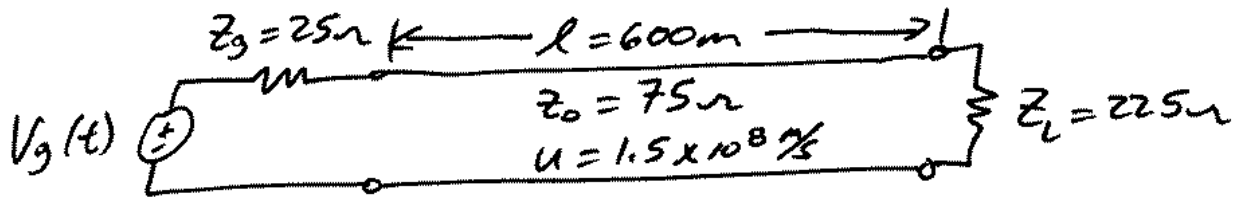


Step voltage input into transmission line \Rightarrow let $V_g(t) = 100 u(t)$ V

$$T = \frac{l}{u} = \frac{600 \text{ m}}{1.5 \times 10^8 \text{ m/s}} = \underline{4 \mu\text{s}}$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{225 - 75}{225 + 75} = \underline{0.5}$$

$$\Gamma_g = \frac{Z_g - Z_0}{Z_g + Z_0} = \frac{25 - 75}{25 + 75} = \underline{-0.5}$$

@ $Z=0$

$$V_{\text{init}}(t) = V_g(t) \frac{Z_0}{Z_g + Z_0} = 100 u(t) \frac{75}{25 + 75} = \underline{75 u(t) \text{ V} = V_1^+}$$

$$I_{\text{init}}(t) = \frac{V_g(t)}{Z_g + Z_0} = \frac{100 u(t)}{25 + 75} = \underline{1 u(t) \text{ A} = I_1^+}$$

@ S.S. ($t \rightarrow \infty$)

$$V_{SS} = V_g(t \rightarrow \infty) \frac{Z_L}{Z_g + Z_L} = 100 \frac{225}{25 + 225} = \underline{90 \text{ V}}$$

$$I_{SS} = \frac{V_g(t \rightarrow \infty)}{Z_g + Z_L} = \frac{100}{25 + 225} = \underline{0.4 \text{ A}}$$

answers should converge to these values

Find $V(z, t_1 = 3.5T) = V(z, 14\mu s)$


- Draw horizontal line on voltage bounce diagram at $3.5T = 14\mu s$.
- Draw vertical line from where the horizontal line crosses the bounce diagram down to the z -axis. This value of z is where there will be a discontinuity. Call it z_1 .

$$\underline{z_1 = 300\text{ m} = \frac{l}{2}}$$

- Add up voltage, on either side of z_1 , below the horizontal line

$$\begin{aligned} 0 \leq z < z_1 \quad V(z, 14\mu s) &= V_2^+ + V_1^- + V_1^+ \\ &= -18.75 + 37.5 + 75 \\ &= \underline{93.75\text{ V}} \end{aligned}$$
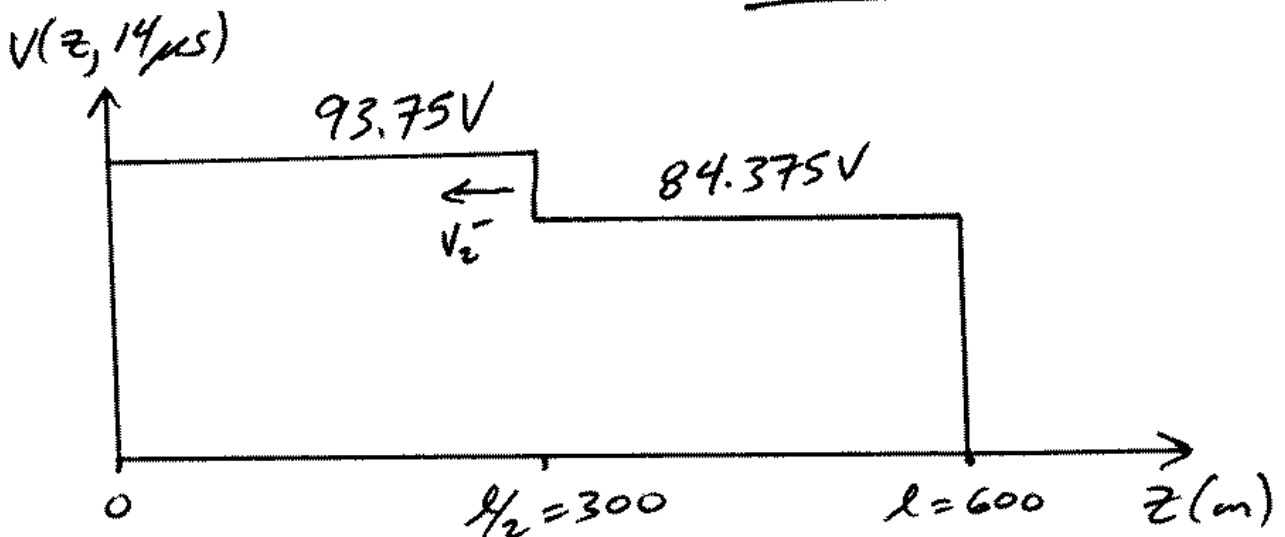
$$\begin{aligned} z_1 \leq z \leq l \quad V(z, 14\mu s) &= V_2^- + V_2^+ + V_1^- + V_1^+ \\ &= \underline{84.375\text{ V}} \end{aligned}$$



Find $i(z, t_2 = 4.75T) = i(z, 19\mu s)$


- Draw horizontal line at $t_2 = 4.75T = 19\mu s$ on the current bounce diagram
- Draw a vertical line from where the horizontal line crosses the bounce diagram down to the z -axis. This value of z is where there will be a discontinuity at

$$\underline{\underline{z_2 = 450\text{ m} = 3l/4}}$$

- Add up the currents on either side of z_2 below the horizontal line

$$\begin{aligned} 0 \leq z < z_2 \quad i(z, 19\mu s) &= I_3^+ + I_2^- + I_2^+ + I_1^- + I_1^+ \\ &= 0.0625 + 0.125 - 0.25 - 0.5 + 1 \\ &= \underline{\underline{0.4375\text{ A}}} \end{aligned}$$


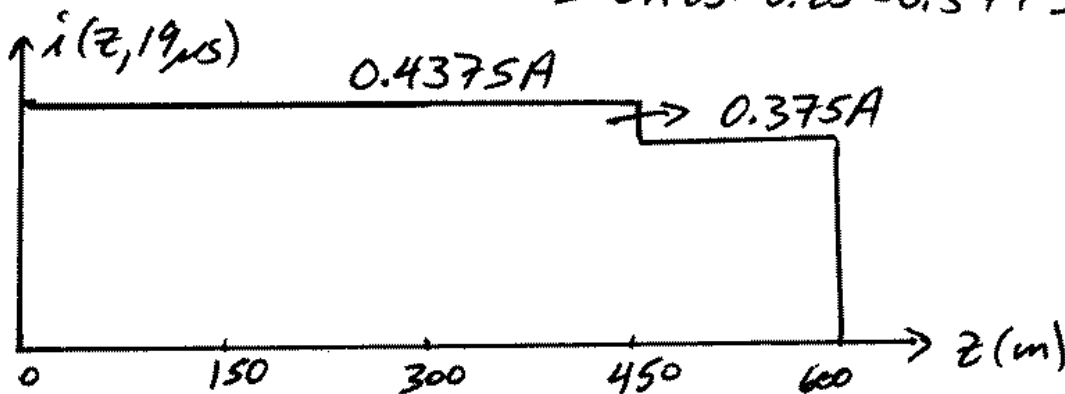
$$\begin{aligned} z_2 \leq z \leq l \quad i(z, 19\mu s) &= I_2^- + I_2^+ + I_1^- + I_1^+ \\ &= 0.125 - 0.25 - 0.5 + 1 = \underline{\underline{0.375\text{ A}}} \end{aligned}$$



Bounce diagrams

$V(z, t_1 = 3.5T = 14\mu s)$

$I(z, t_2 = 4.75T = 19\mu s)$

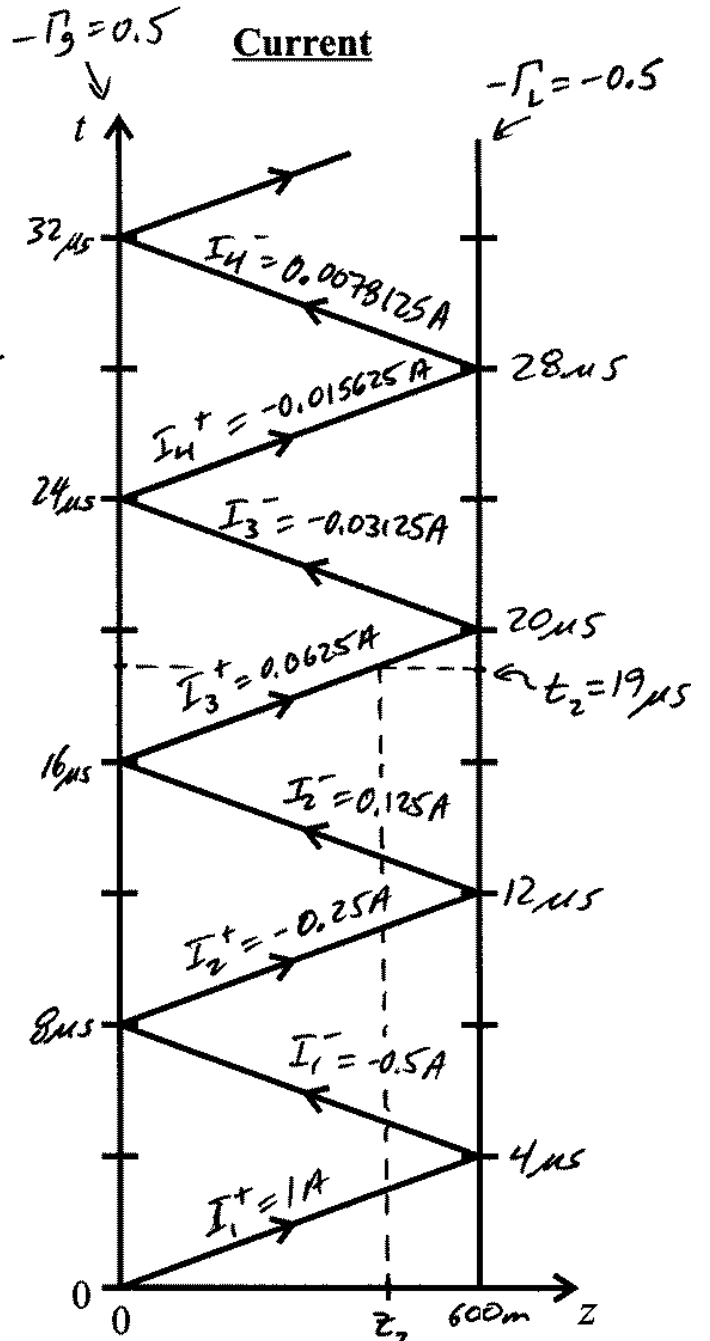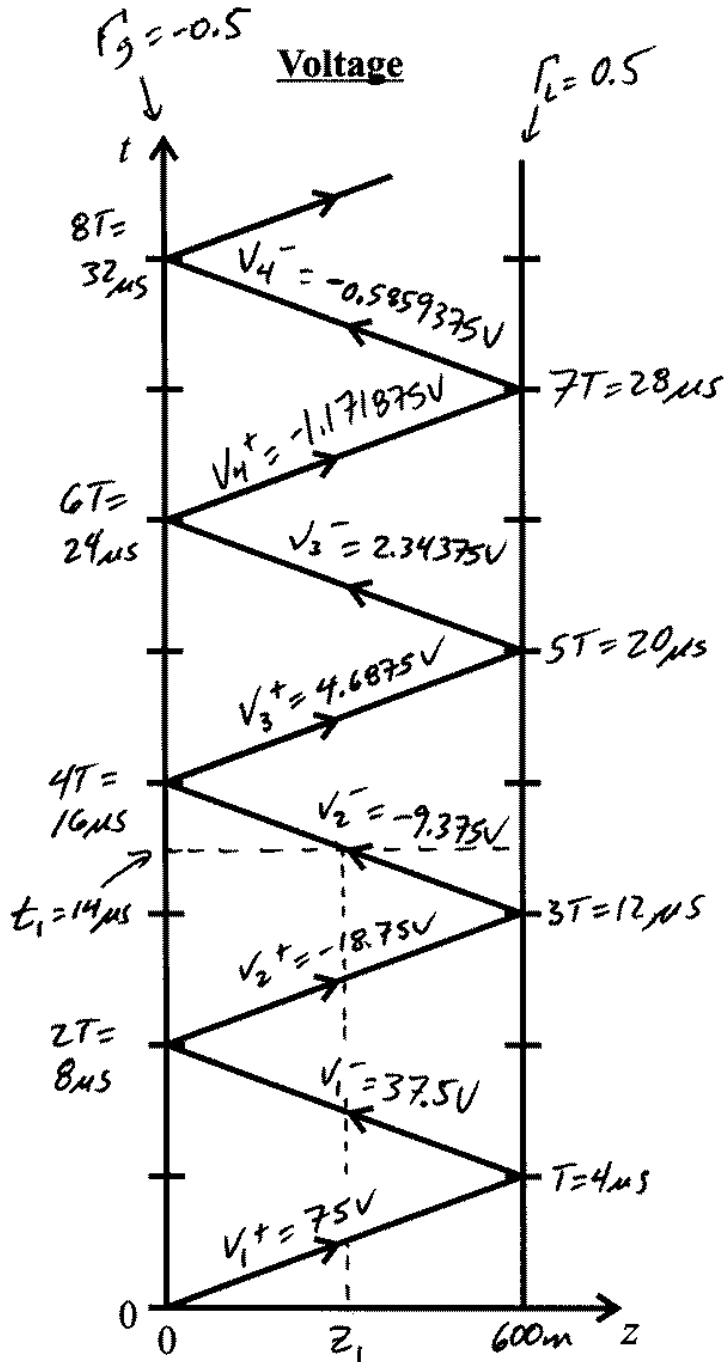

Find $V(z = \frac{1}{2}, t) = V(300\text{m}, t)$

→ Draw a vertical line up from $z = 300\text{m}$ on the voltage bounce diagram

→ add up voltages as the vertical line crosses the bounce diagram, draw horizontal lines over to the time axis to note times where voltage level changes

$$0 \leq t < 2\mu\text{s} \quad V(300, t) = 0$$

$$2\mu\text{s} \leq t < 6\mu\text{s} \quad V(300, t) = 75\text{V}$$

$$6\mu\text{s} \leq t < 10\mu\text{s} \quad V(300, t) = 75 + 37.5 = 112.5\text{V}$$


$$10\mu\text{s} \leq t < 14\mu\text{s} \quad V(300, t) = 112.5 + (-18.75) = 93.75\text{V}$$

$$14\mu\text{s} \leq t < 18\mu\text{s} \quad V(300, t) = 93.75 - 9.375 = 84.375\text{V}$$

$$18\mu\text{s} \leq t < 22\mu\text{s} \quad V(300, t) = 84.375 + 4.6875 = 89.0625\text{V}$$

$$22\mu\text{s} \leq t < 26\mu\text{s} \quad V(300, t) = 89.0625 + 2.34375 = 91.40625\text{V}$$

⋮

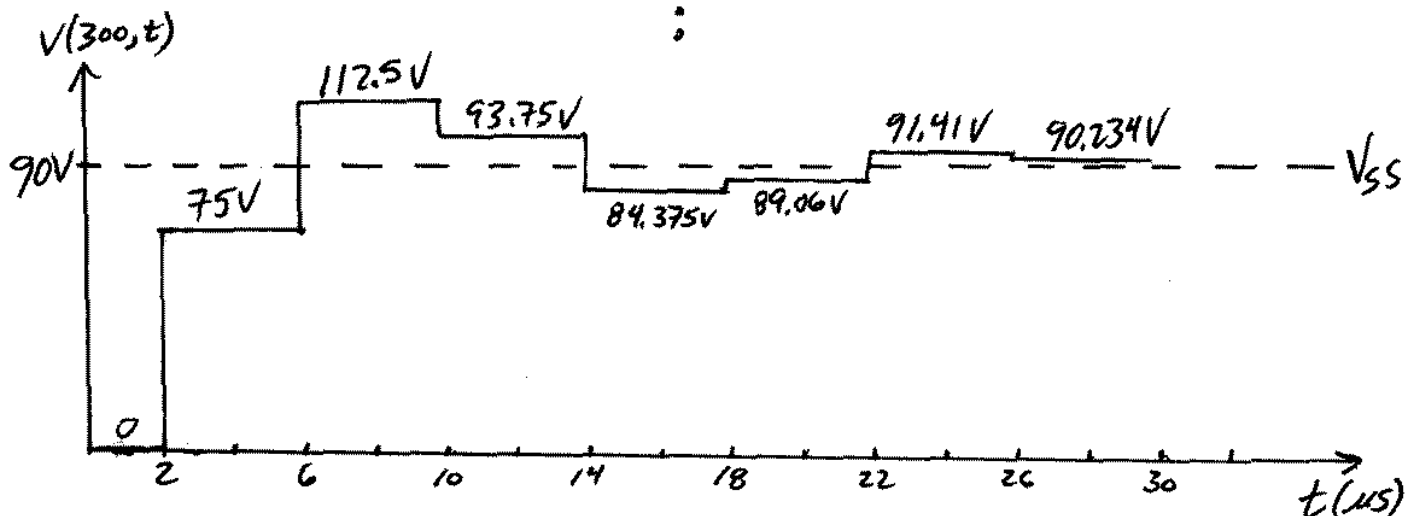

Find $i(z=l, t) = i(600m, t)$

→ use existing vertical line & time marks
on current bounce diagram

→ add up currents as the vertical line at $z=l$
contacts bounce diagram & note times


$$0 \leq t < 4\mu s \quad i(600, t) = 0$$

$$4\mu s \leq t < 12\mu s \quad i(600, t) = 1 + (-0.5) = \underline{0.5A}$$

$$12\mu s \leq t < 20\mu s \quad i(600, t) = 0.5 + (-0.25 + 0.125) = \underline{0.375A}$$

$$20\mu s \leq t < 28\mu s \quad i(600, t) = 0.375 + (0.0625 - 0.03125) \\ = \underline{0.40625A}$$
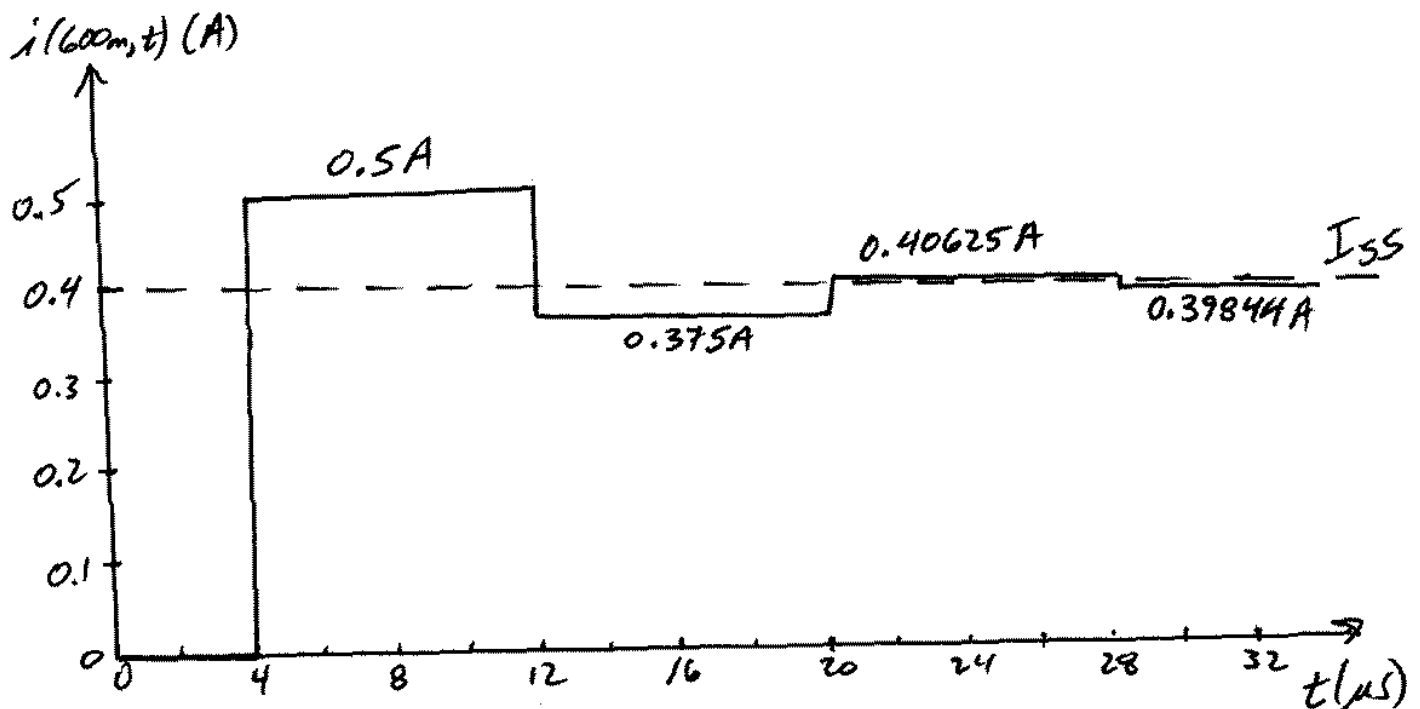
$$28\mu s \leq t < 36\mu s \quad i(600, t) = 0.40625 + (-0.015625 + 0.0078125) \\ = \underline{0.3984375A}$$



Bounce diagrams

$V(z=l/2=300m, t)$

$I(z=l=600m, t)$

