
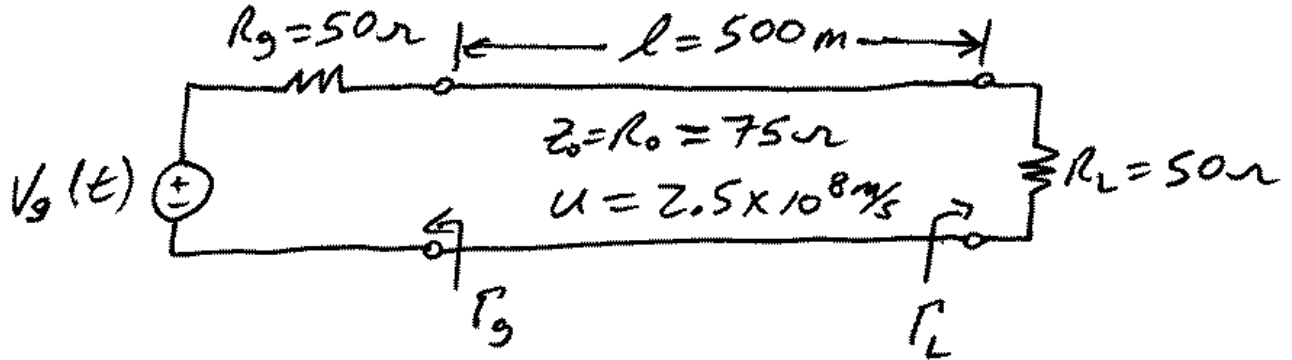


Voltage pulse input into transmission

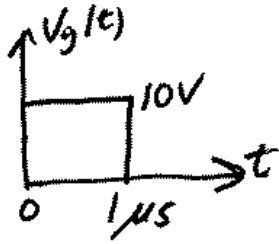
⇒ let $V_g(t) = 10 [u(t) - u(t - 1 \mu s)]$ V



$$\Gamma_g = \Gamma_L = \frac{50 - 75}{50 + 75} = \underline{-0.2}$$

$$T = \frac{l}{u} = \frac{500 \text{ m}}{2.5 \times 10^8 \text{ m/s}} = \underline{2 \mu\text{s}}$$

Equiv. CKT $t < 2T$

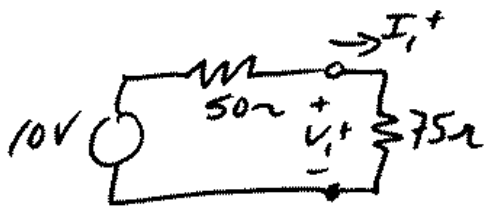

$$V_1^+ = V_{init} = 10V \left(\frac{75}{50+75} \right) = \underline{6V}$$

$$I_1^+ = I_{init} = \frac{10V}{(50+75)\Omega} = \underline{80 \text{ mA}}$$

$V_{SS} = 0V$ (finite-length input & $|\Gamma_g| = |\Gamma_L| < 1$)

$I_{SS} = 0A$

Draw Bounce Diagrams

Find $V(l, t) = V(500\text{m}, t)$ for $0 \leq t \leq 14\mu\text{s}$

→ use existing vertical line at $z = l = 500\text{m}$
and existing time dilineations (scale)

→ note values of voltage pulses as well
as times

$$0 \leq t < 2\mu\text{s} \quad V(l, t) = \underline{0}$$

$$2\mu\text{s} \leq t < 3\mu\text{s} \quad V(l, t) = 6 + (-1.2) = \underline{4.8\text{V}}$$

$$3\mu\text{s} \leq t < 6\mu\text{s} \quad V(l, t) = [6 + (-1.2)] + [-6 + 1.2] = \underline{0}$$


$$6\mu\text{s} \leq t < 7\mu\text{s} \quad V(l, t) = 0 + 0.24 - 0.048 = \underline{0.192\text{V}}$$

$$7\mu\text{s} \leq t < 10\mu\text{s} \quad V(l, t) = 0.192\text{V} + [-0.24 + 0.048] = \underline{0}$$

$$10\mu\text{s} \leq t < 11\mu\text{s} \quad V(l, t) = 0 + 0.0096 - 0.00192 = \underline{0.00768\text{V}}$$

$$11\mu\text{s} \leq t < 14\mu\text{s} \quad V(l, t) = 0.00768 + [-0.0096 + 0.00192] = \underline{0}$$

(see plot on next page)

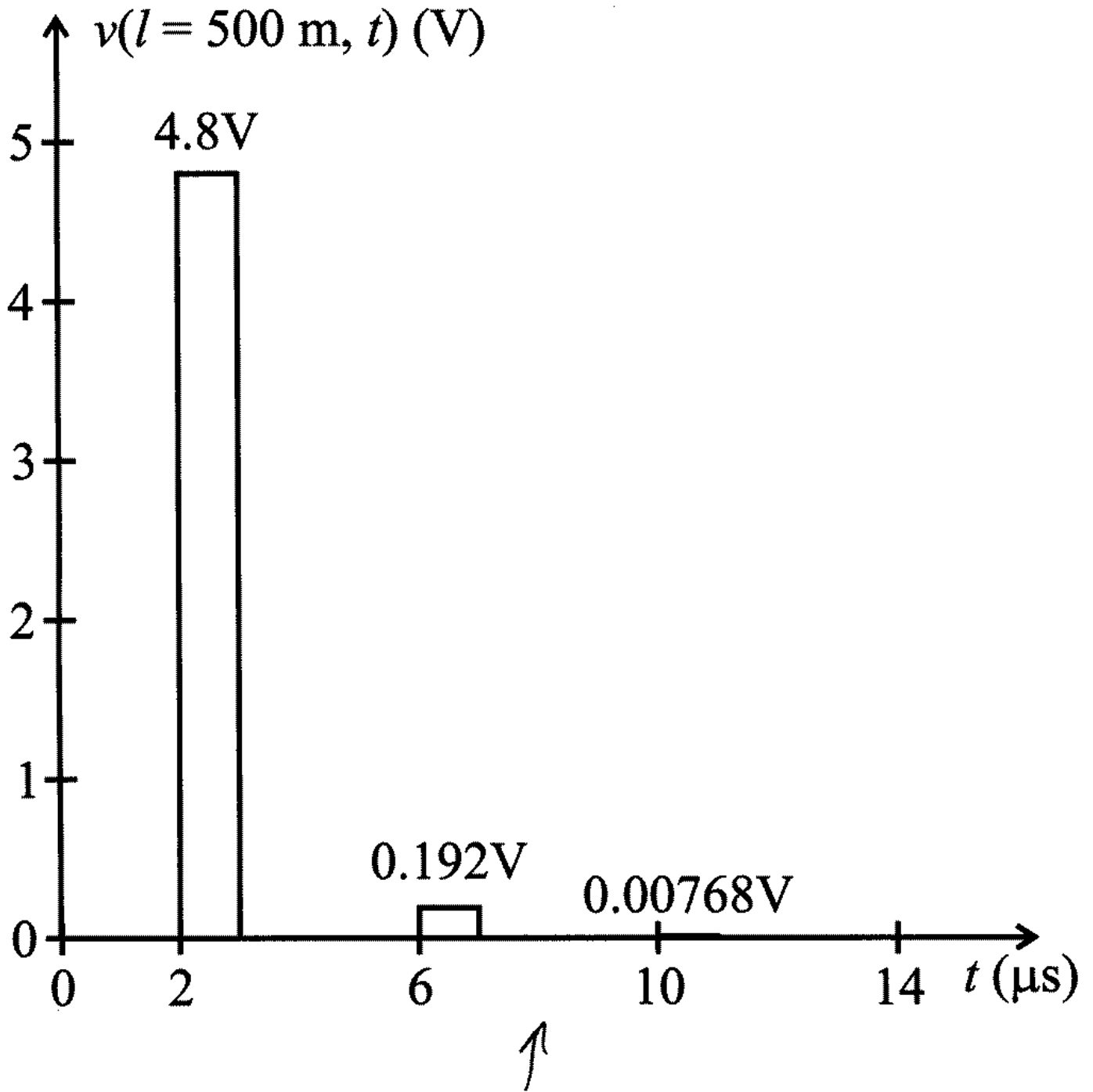

Note how quickly the pulse is dying out w/ moderate ($|r|=0.2$) mis-matches

Find $i(z, t = 1.75T) = i(z, 3.5\mu s)$

→ Draw horizontal line at $t = 3.5\mu s$ on the current bounce diagram

→ Draw vertical lines down from where the horizontal $t = 3.5\mu s$ line intersects the bounce diagram and note values of z


$$\underline{z_1 = 125m} \qquad \underline{z_2 = 375m}$$

→ add up current pulses below horizontal line


$$0 \leq z < z_1 \quad i(z, 3.5\mu s) = -80mA + 80mA = \underline{0}$$

$$z_1 \leq z < z_2 \quad i(z, 3.5\mu s) = 16mA - 80mA + 80mA = \underline{16mA}$$
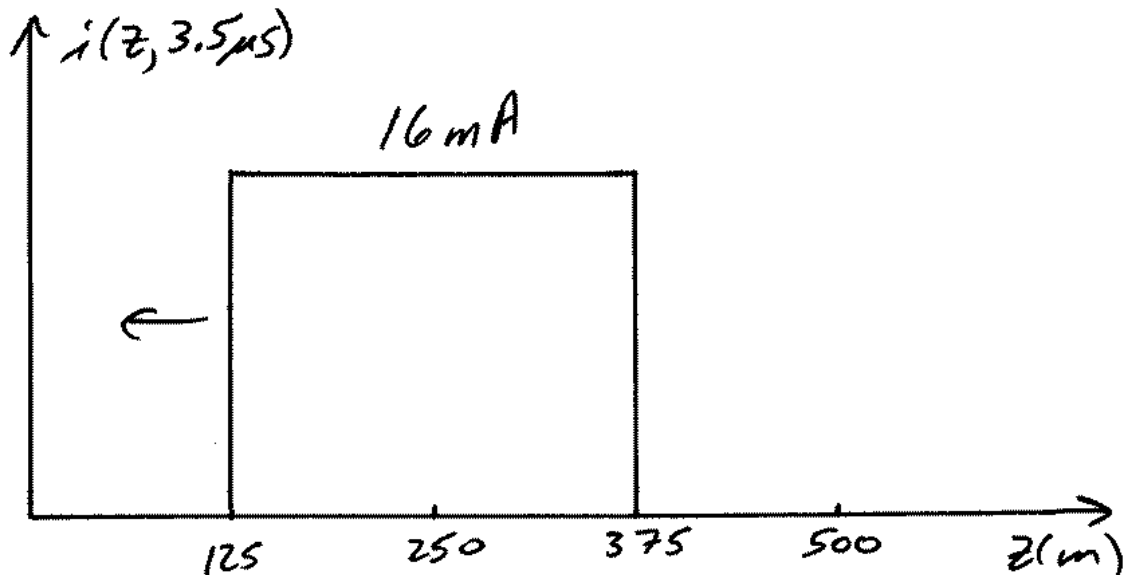
$$z_2 \leq z \leq l \quad i(z, 3.5\mu s) = -16 + 16 - 80 + 80 = \underline{0}$$



Voltage $V(l=500 \text{ m}, t)$

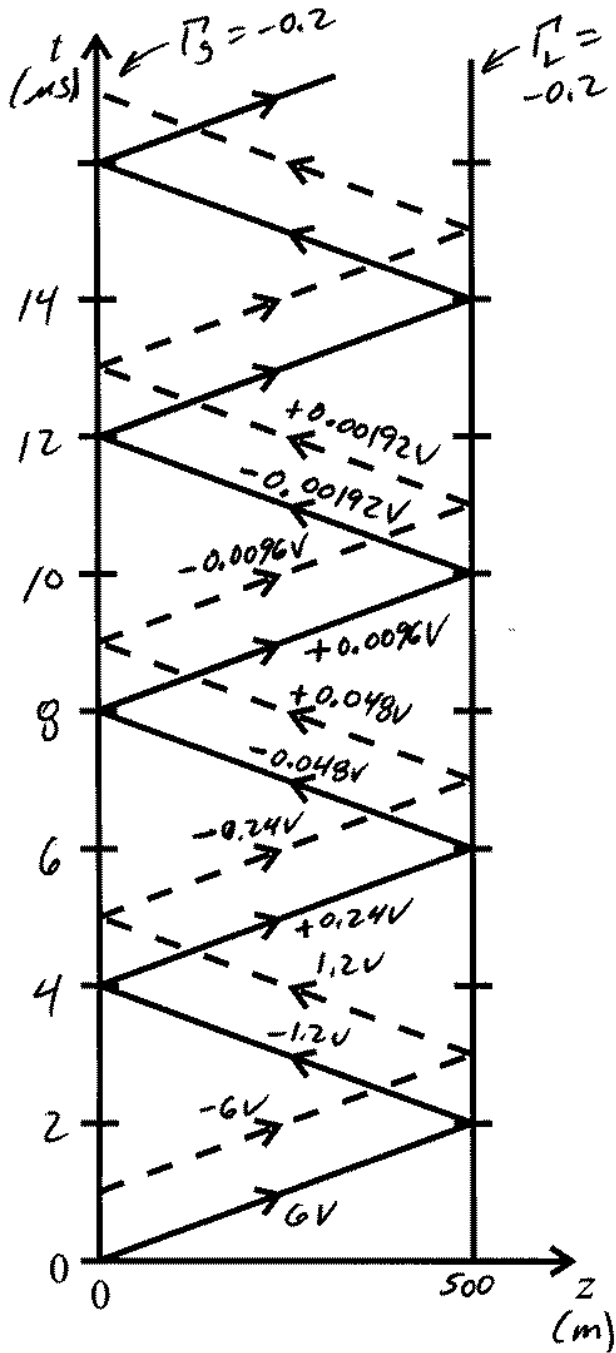

Current $I(z, t=1.75T=3.5 \mu\text{s})$

