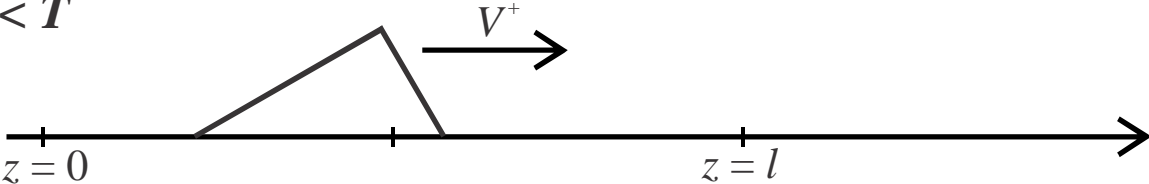


Define one-way transit time $\equiv T = l / u$




$0 < t < T$



Total voltage will be the sum of V^+ and V^-

$t = T + \Delta t$

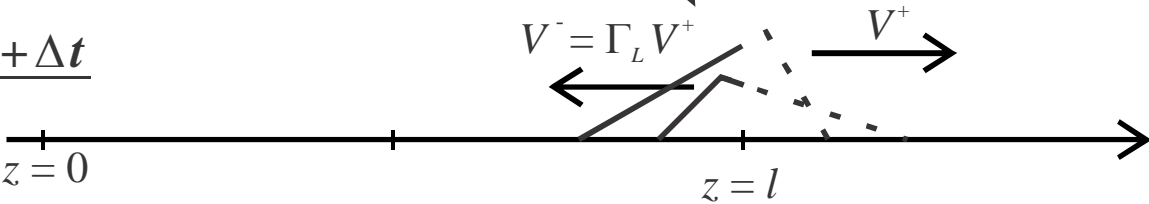

$T < t < 2T$

