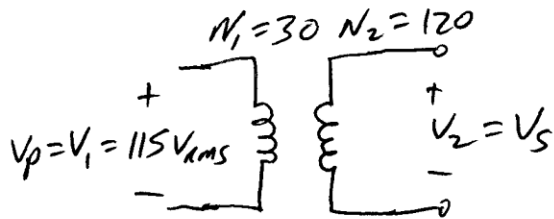


An ideal transformer has 30 turns on the primary and 120 turns on the secondary. (a) If the primary voltage is  $115 \text{ V}_{\text{rms}}$ , what is the secondary voltage if the secondary is assumed to be open-circuited? (b) Is this a step-up or step-down transformer? (c) If the secondary is now connected to a resistive load of  $1.5 \text{ k}\Omega$ , what are the currents in the primary and secondary windings?




a) From Dr. Whites Notes (lecture 9 Ideal Transformer)

$$\frac{V_1(t)}{V_2(t)} = \frac{N_1}{N_2} \Rightarrow V_2 = V_s = \frac{N_2}{N_1} V_1 = \frac{120}{30} (115)$$

$$\underline{V_2 = V_s = 460 \text{ V}_{\text{rms}}}$$

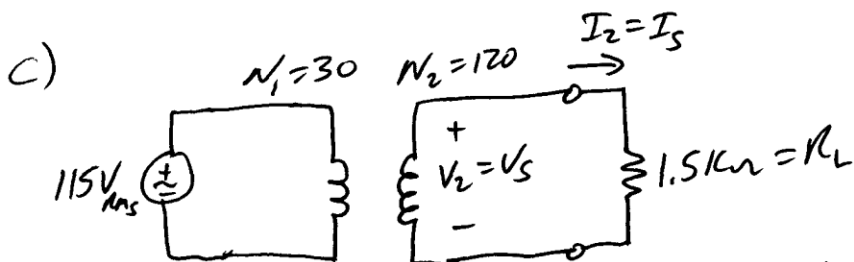b) Since  $V_2 = V_s > V_1 = V_p$ , this is a step-up transformer



By Ohm's Law,  $I_2 = I_s = \frac{V_2}{R_L} = \frac{460 \text{ V}_{\text{rms}}}{1500 \Omega}$

$$\underline{I_2 = I_s = 0.306 \text{ A}_{\text{rms}} = 306.6 \text{ mA}_{\text{rms}}}$$

From Dr. Whites notes,  $\frac{I_1(t)}{I_2(t)} = \frac{N_2}{N_1}$ .

$$I_1 = I_p = \frac{120}{30} (0.306 \text{ A}_{\text{rms}})$$

$$\underline{I_1 = I_p = 1.226 \text{ A}_{\text{rms}}}$$