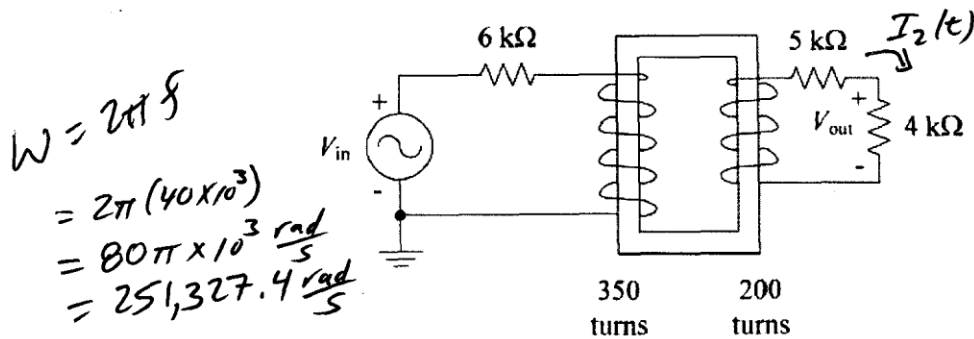


A voltage source $V_{in}(t) = 5 + 5\cos(2\pi ft)$ V is connected to an ideal transformer as shown in the figure below. If $f = 40$ kHz, find the output voltage $V_{out}(t)$.




$$\begin{aligned} \omega &= 2\pi f \\ &= 2\pi(40 \times 10^3) \\ &= 80\pi \times 10^3 \frac{\text{rad}}{\text{s}} \\ &= 251,327.4 \frac{\text{rad}}{\text{s}} \end{aligned}$$

⇒ Ignore DC component of $V_{in}(t)$ as it will NOT couple to the secondary side of the transformer

⇒ For the AC component, the primary side 'sees' an effective input resistance (see Dr. White's notes, Lecture 9 Ideal Transformer) of

$$\begin{aligned} R_{1, \text{eff}} &= \left(\frac{N_1}{N_2}\right)^2 R_L = \left(\frac{350}{200}\right)^2 (5000 + 4000) \\ &= 27562.5 \Omega \end{aligned}$$

Equivalent Primary Circuit (AC ONLY)

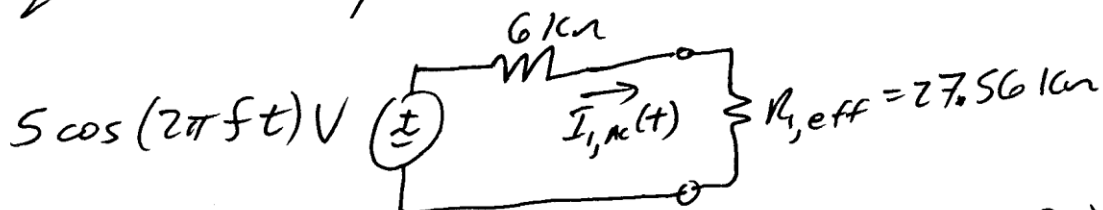

$$I_{1, \text{AC}}(t) = \frac{5 \cos(2\pi ft)}{6000 + 27562.5} = 1.49 \times 10^{-4} \cos(2\pi ft) \text{ A}$$

Per ideal transformer current relationship,

$$\frac{I_1(t)}{I_2(t)} = \frac{N_2}{N_1} \Rightarrow I_2(t) = \frac{N_1}{N_2} I_1(t) = \frac{350}{200} (1.49 \times 10^{-4} \cos(\))$$

$$V_{\text{out}}(t) = I_2(t) 4000 = 2.607 \times 10^{-4} \cos(\) 4000$$

$$\underline{\underline{V_{\text{out}}(t) = 1.0428 \cos(251,327.4t) \text{ V}}}$$