
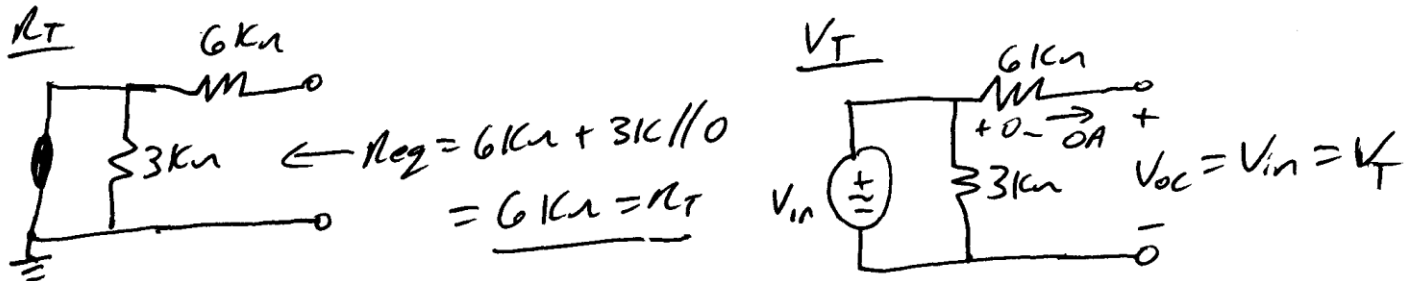


The source $V_{in}(t) = 10\cos(2\pi \cdot 3000t)$ V is connected to an ideal transformer as shown below. Design the transformer so that maximum power is delivered to the 4 k Ω load.

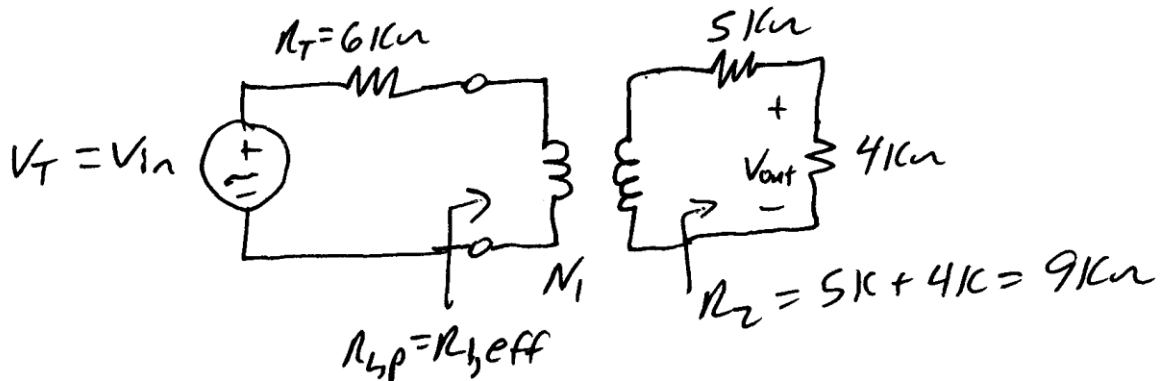Find Thevenin equiv. of primary side circuit



Simplified transformer circuit



For maximum power transfer to the secondary, set $R_{Lp} = R_{1,eff} = R_T = 6\text{ k}\Omega$. Per Dr. Whites notes (Lecture 9 Ideal Transformer)

$$R_{1,eff} = \left(\frac{N_1}{N_2}\right)^2 R_2 = \left(\frac{N_1}{N_2}\right)^2 9\text{ k}\Omega = 6\text{ k}\Omega$$

$$\hookrightarrow \frac{N_1}{N_2} = \sqrt{\frac{6}{9}} = 0.8165$$