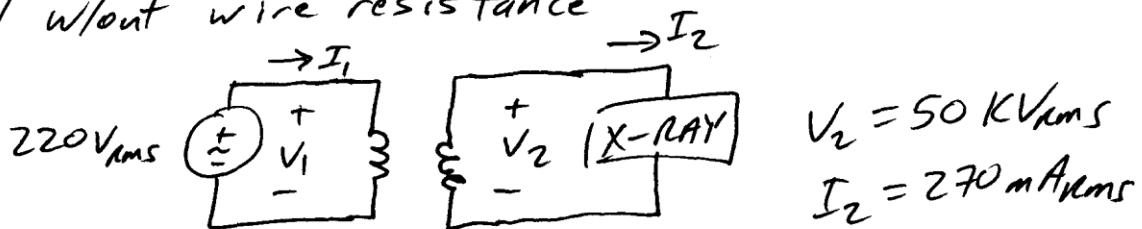


An ideal transformer was designed to run an X-ray machine at a voltage of $50 \text{ kV}_{\text{rms}}$ and $270 \text{ mA}_{\text{rms}}$ current. The transformer operates from a $220\text{-V}_{\text{rms}}$ power supply. However, the resistance in the wires connecting the power supply to the transformer was initially ignored. Upon installation, it was realized that the supply wires have a total resistance of 0.6Ω . By how much must the supply voltage be increased in order to maintain the same operating parameters at the transformer output?

Ideal w/out wire resistance




From Dr. Whites notes (Lecture 9 Ideal Transformer)

$$\frac{V_1(t)}{V_2(t)} = \frac{N_1}{N_2} = \frac{220}{50 \times 10^3} = 4.4 \times 10^{-3}$$

$$\frac{I_1(t)}{I_2(t)} = \frac{N_2}{N_1} \Rightarrow I_1 = \frac{1}{4.4 \times 10^{-3}} (0.27) = 61.36 \text{ A}_{\text{rms}}$$

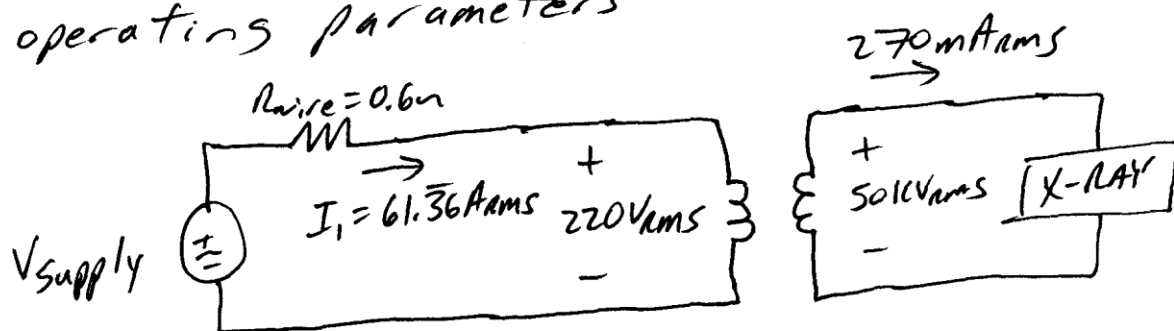Adding wire resistance and maintaining same operating parameters



Apply KVL around primary / supply side

$$-V_{\text{supply}} + 61.36(0.6) + 220 = 0$$

$$V_{\text{supply}} = 256.81 \text{ V}_{\text{rms}}$$

$$\text{Increase} = V_{\text{supply}} - 220 = \underline{\underline{36.81 \text{ V}_{\text{rms}}}}$$