

- 11.17 A distortionless line operating at 120 MHz has  $R = 20 \Omega/\text{m}$ ,  $L = 0.3 \mu\text{H}/\text{m}$ , and  $C = 63 \text{ pF}/\text{m}$ . (a) Determine  $\gamma$ ,  $u$ , and  $Z_0$ . (b) How far will a voltage wave travel before it is reduced to 20% of its initial magnitude? (c) How far will it travel to suffer a  $45^\circ$  phase shift?

$$a) \quad (11.22) \quad G = \frac{RC}{L} = \frac{(20)63 \times 10^{-12}}{0.3 \times 10^{-6}} = \underline{0.0042 \text{ S/m}}$$

$$(11.11) \quad \gamma = \sqrt{(R + j\omega L)(G + j\omega C)} = \sqrt{(20 + j2\pi(120 \times 10^6)0.3 \times 10^{-6})(0.0042 + j\omega 63 \times 10^{-12})}$$

$$\underline{\underline{\gamma = 0.28983 + j3.2779 \text{ m}^{-1}}}$$

$$(11.14) \quad u = \frac{\omega}{\beta} = \frac{2\pi(120 \times 10^6)}{3.2779} = \underline{\underline{2.3002 \times 10^8 \text{ m/s}}}$$

$$Z_0 = \sqrt{\frac{L}{C}} = \underline{\underline{69 \Omega}} \quad (11.23b)$$

$$b) \quad e^{-\alpha d} = 0.20 \quad (\text{exponential decay term})$$

$$d = -\frac{1}{\alpha} \ln 0.2 = -\frac{1}{0.28983} \ln 0.2$$

$$\underline{\underline{d = 5.55 \text{ m}}}$$

$$c) \quad \beta d = 45^\circ \text{ or } \pi/4 \quad (\text{phase shift term})$$

$$d = \frac{\pi/4}{3.2779} = \underline{\underline{0.2396 \text{ m}}}$$