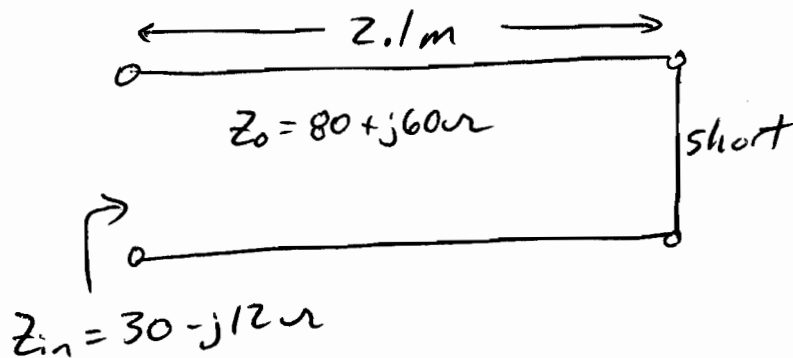


- 11.22 A lossy transmission line of length 2.1 m has characteristic impedance of $80 + j60 \Omega$. When the line is short-circuited, the input impedance is $30 - j12 \Omega$. (a) Determine α and β . (b) Find the input impedance when the short circuit is replaced by $Z_L = 40 + j30 \Omega$.



- a) Per (11.33), for a short circuit stub ($Z_L = 0$)

$$Z_{in,sc} = Z_0 \tanh(\gamma l)$$

$$30 - j12 = (80 + j60) \tanh(\gamma (2.1))$$

$$2.1 \gamma = \tanh^{-1} \left(\frac{30 - j12}{80 + j60} \right) = 0.1571 - j0.276176$$

$$\gamma = 0.07480544 - j0.1315125 \text{ m}^{-1}$$

$$\alpha = 0.074805 \text{ Np/m} \quad \& \quad \beta = 0.1315125 \text{ rad/m}$$

- b) Use (11.33) again

$$Z_{in} = Z_0 \left[\frac{Z_L + Z_0 \tanh \gamma l}{Z_0 + Z_L \tanh \gamma l} \right]$$

$$= (80 + j60) \left[\frac{(40 + j30) + (80 + j60) \left(\frac{30 - j12}{80 + j60} \right)}{(80 + j60) + (40 + j30) \left(\frac{30 - j12}{80 + j60} \right)} \right]$$

$$Z_{in} = 61.4655 + j24.4301 \Omega$$