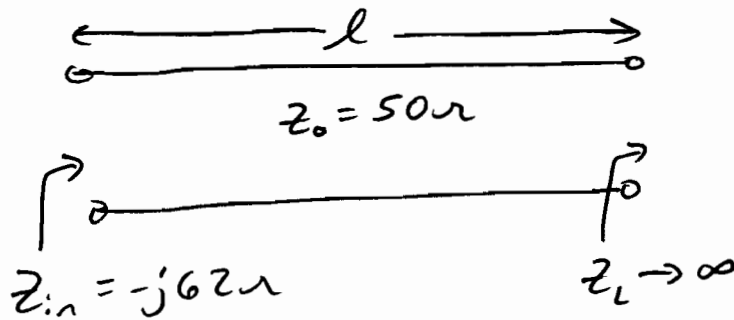


- 11.27 A  $50 \Omega$  transmission line of length  $\ell$  is open-circuited. If the input impedance is  $-j62 \Omega$ , determine  $\ell$  in terms of  $\lambda$ .



Normalize impedances and plot on Smith Chart

$$z_L = \frac{\infty}{50} \rightarrow \infty$$

$$z_{in} = \frac{-j62}{50} = -j1.24 \Omega/\Omega$$

looking at the "WAVELENGTHS TOWARD GENERATOR" scale

$$\ell = 0.3575 \lambda - 0.25 \lambda$$

$\uparrow$   $z_{in}$  location       $\uparrow$   $z_L = z_{oc}$  location

$$\underline{\underline{\ell = 0.1075 \lambda + n \frac{\lambda}{2}}}$$

can always  
add half wavelengths

Analytic Check

$$\Gamma_{in} = \frac{z_{in} - z_0}{z_{in} + z_0} = \frac{-j62 - 50}{-j62 + 50} = 1 \angle -77.77^\circ = 1 \angle -1.3573 \text{ rad}$$

Per Smith Chart

$$\Gamma_{in} = \Gamma_L e^{-j2\beta\ell} = (1) e^{-j2\left(\frac{2\pi}{\lambda}\right)(0.1075\lambda)} = 1 e^{-j1.3509} = 1 \angle -1.3509 \text{ rad}$$

fairly close!

# Simple Smith Chart

Problem 11.27

$$Z_0 = 50 \Omega$$

