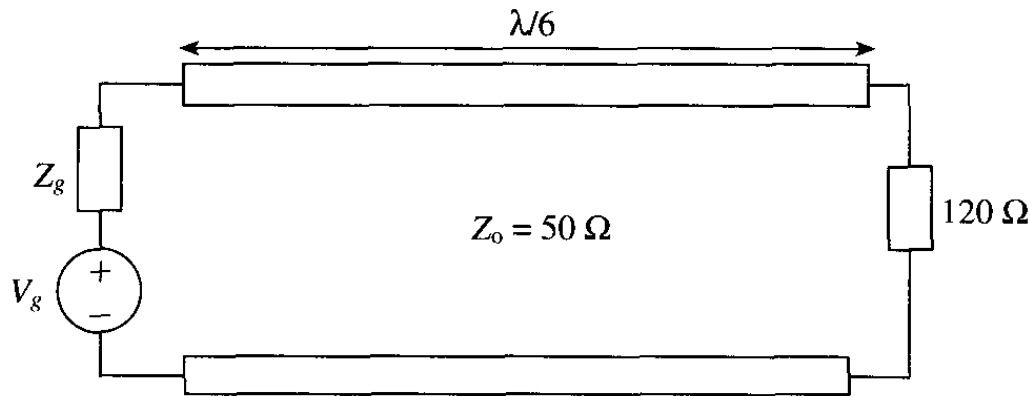


- 11.28 Refer to the lossless transmission line shown. (a) Find  $\Gamma$  and  $s$ .  
 (b) Determine  $Z_{in}$  at the generator.



- Find reflection coefficient at both load and input.

Plot  $z_L = \frac{Z_L}{Z_0} = \frac{120}{50} = 2.4 \text{ } \Omega$  on Smith Chart

a) Read off  $|\Gamma_L| = 0.41$   $\angle \Gamma_L = 0^\circ$

$$S = 2.4 = r_{max}$$

$$\underline{\underline{\Gamma_L = 0.41 \angle 0^\circ}}$$

b) Move  $\lambda/6$  "toward the generator" from  $z_L$  on an arc of constant radius to  $\Gamma_{in}$  +  $y_{in}$  point

$$y_{in} = 0.525 - j0.45 \text{ } \Omega \Rightarrow z_{in} = y_{in} Z_0$$

$$\underline{\underline{z_{in} = 26.25 - j22.5 \text{ } \Omega}}$$

$$|\Gamma_{in}| = 0.41 \quad \angle \Gamma_{in} = -120^\circ$$

$$\underline{\underline{\Gamma_{in} = 0.41 \angle -120^\circ}}$$

# Simple Smith Chart

$Z_0 = 50\Omega$

